

## 6. Attenuators and Switches

The state of the switch is controlled by some **digital logic**, and there is a different scattering matrix for each state.

[HO: Microwave Switches](#)

[HO: The Microwave Switch Spec Sheet](#)

We can **combine** fixed attenuators with microwave switches to create very important and useful devices—the **variable** (digital) attenuator.

[HO: Attenuators](#)


[HO: The Digital Attenuator Spec Sheet](#)

We typically make switches and voltage controlled attenuators with PIN diodes. **If** you are interested, you might check out the handout below (no, this handout below will **not** be on any exam!).

[HO: PIN Diodes](#)
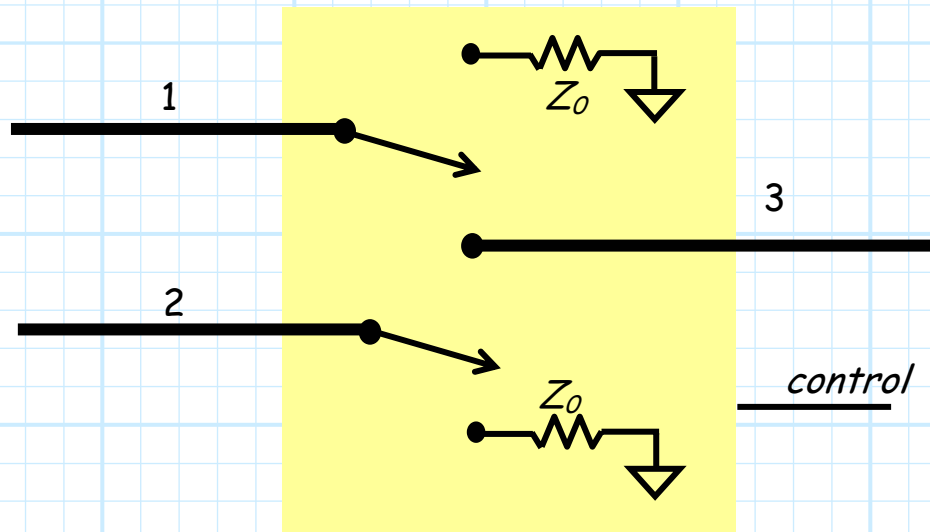
# Microwave Switches


Consider an **ideal** microwave SPDT switch.




The **scattering matrix** will have one of two forms:

$$\bar{\bar{\mathbf{S}}}_{13} = \begin{bmatrix} 0 & 0 & 1 \\ 0 & 0 & 0 \\ 1 & 0 & 0 \end{bmatrix} \quad \bar{\bar{\mathbf{S}}}_{23} = \begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & 1 \\ 0 & 1 & 0 \end{bmatrix}$$

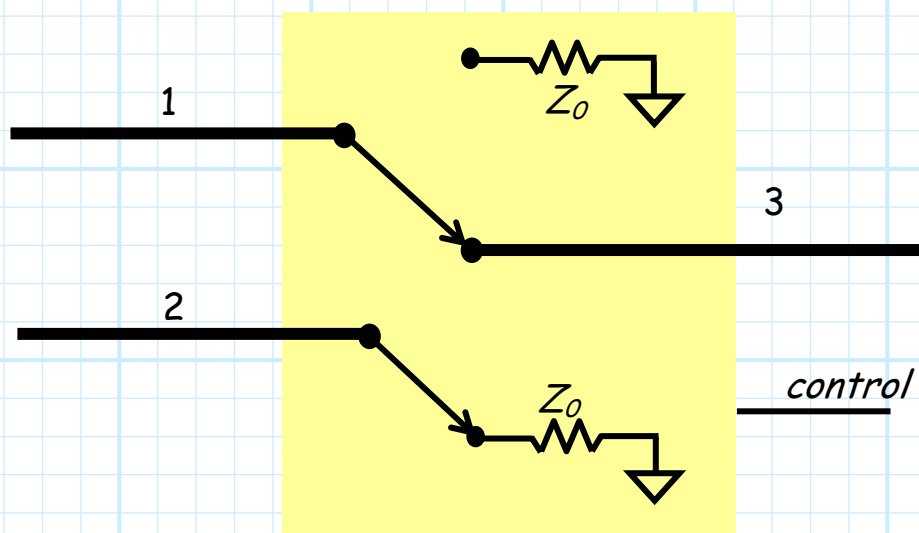where  $\bar{\bar{\mathbf{S}}}_{13}$  describes the device when port 1 is **connected** to port 3:



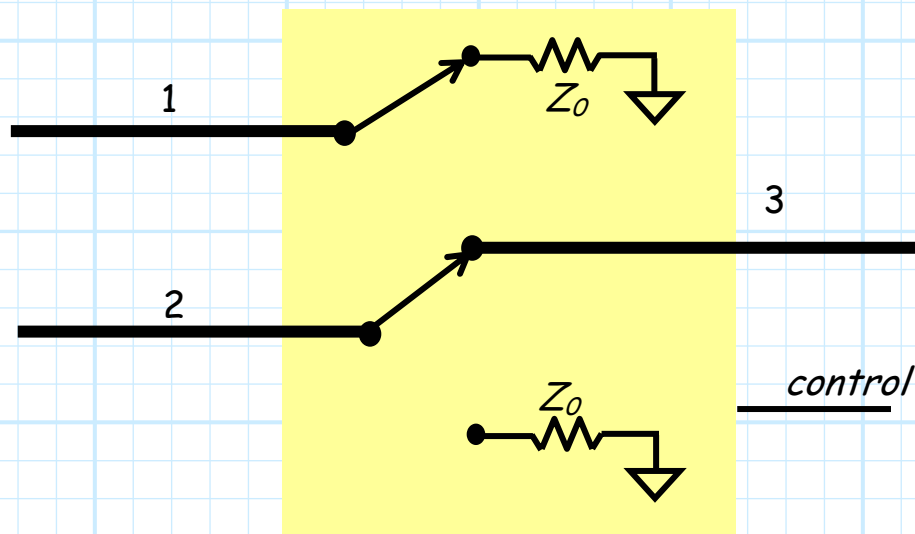and where  $\bar{\bar{S}}_{23}$  describes the device when port 2 is connected to port 3:




These ideal switches are called **matched**, or **absorptive switches**, as ports 1 and 2 remain matched, even when **not connected**.

This is in contrast to a **reflective switch**, where the disconnected port will be perfectly reflective, i.e.,

$$\bar{\bar{S}}_{13} = \begin{bmatrix} 0 & 0 & 1 \\ 0 & e^{j\phi} & 0 \\ 1 & 0 & 0 \end{bmatrix} \quad \bar{\bar{S}}_{23} = \begin{bmatrix} e^{j\phi} & 0 & 0 \\ 0 & 0 & 1 \\ 0 & 1 & 0 \end{bmatrix}$$

where of course  $|e^{j\phi}| = 1$ .

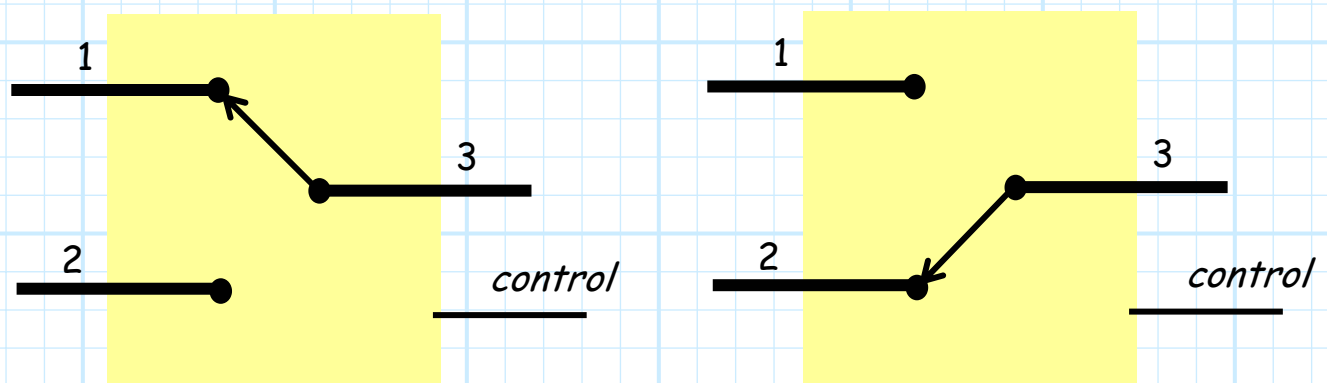

Of course, just as with **all** ideal components, the ideal switch does **not** exist!

Using the fact that switches are **reciprocal** devices, we can write for  $\bar{\bar{S}}_{13}$  for a non-ideal switch:

$$\bar{\bar{S}}_{13} = \begin{bmatrix} S_{11} & S_{21} & S_{31} \\ S_{21} & S_{22} & S_{32} \\ S_{31} & S_{32} & S_{33} \end{bmatrix}$$

We can therefore consider the following **parameters** for specifying switch performance.

### Insertion Loss

$$IL = -10 \log_{10} |S_{31}|^2$$

Insertion Loss indicates the loss encountered as a signal propagates **through** the switch. Ideally, this value is 0 dB. Typically, this value is around 1 dB.

### Isolation


$$Isolation = -10 \log_{10} |S_{32}|^2$$

Isolation is a measure of how much power "**leaks**" into the **disconnected** port. Ideally, this value would be very **large**—typical switch isolation is 30 - 50 dB.

## Return Loss

$$\text{Return Loss} = -10 \log_{10} |S_{11}|^2$$

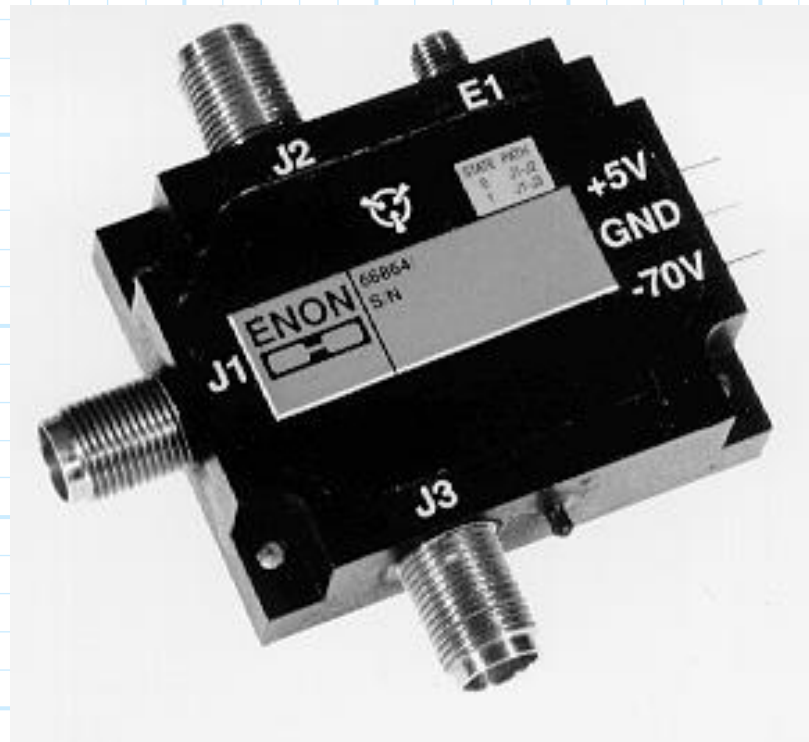Just as we have **always** defined it! We of course want this value to very high (typical values are 20 to 40 dB). However, we find for **reflective** switches, this value can be nearly 0 dB for the **disconnected** port!



# The Microwave Switch Specification Sheet

## Switch Type

A microwave switch is **either** absorptive or reflective, which refers to the input impedance of the disconnected port.

A microwave switch can have **multiple** ports (e.g., SPDT, SP4T)

## Bandwidth (Hz)

A switch, like all other devices, can effectively operate only within a finite **bandwidth** (e.g., 2-5 GHz or 300-400 MHz).

## Input Impedance ( $\Gamma$ , return loss, VSWR)

This of course is dependent on the **state** of the switch (i.e., whether a port is connected or disconnected).

## Insertion Loss (dB)

Typically this is 2 dB or less for good switches, but is somewhat dependent on frequency (insertion loss **increases** with frequency).

## Maximum Input power (dBm)

Switches have a **maximum** input power. Typical values range from 10 to 25 dBm.

## Switching Speed (seconds)

The state of a microwave switch **cannot** change instantaneously. It takes some small but non-zero amount of time to change from one state to another. Typical values range from 0.1 to 10.0  $\mu$ -seconds.

## Isolation (dB)

Typical values range from 20 to 50 dB.

## Switch Logic

Describes the control line values required to switch the port switch state. Typically **TTL** logic values are used—0 volts for one state and 5V for the other.


## DC Power

Switches are **not** passive devices! They require a D.C. voltage (5 or 15 V typical) and will draw some amount of D.C current. The product of the two of course is equal to the D.C. **power** delivered to the switch (typically  $\ll$  1W)
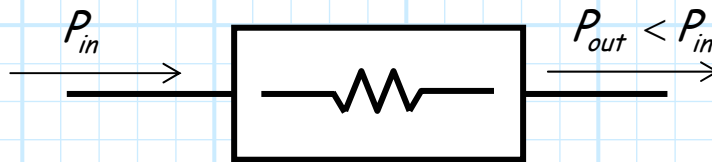
# Attenuators

Under certain situations, we may actually want to **reduce** signal power!

Thus, we need an inverse amplifier—an **attenuator**.



An **ideal** attenuator has a scattering matrix of the form:

$$\bar{\mathbf{S}} = \begin{bmatrix} 0 & \alpha \\ \alpha & 0 \end{bmatrix}$$

where  $|\alpha| < 1$ .

Thus, an attenuator is **matched** and **reciprocal**, but it is certainly **not** lossless.

The **attenuation** of an attenuator is defined as:

$$\text{Attenuation} = -10 \log_{10} |\alpha|^2$$


Typical values of **fixed** attenuators (sometimes called “pads”) are 3 dB, 6 dB, 10 dB, 20 dB and 30 dB.




For example, a 6 dB pad will attenuate as signal by 6 dB—the output power will be **one fourth** of the input power.

One **application** of **fixed** attenuators is to improve **return loss**.

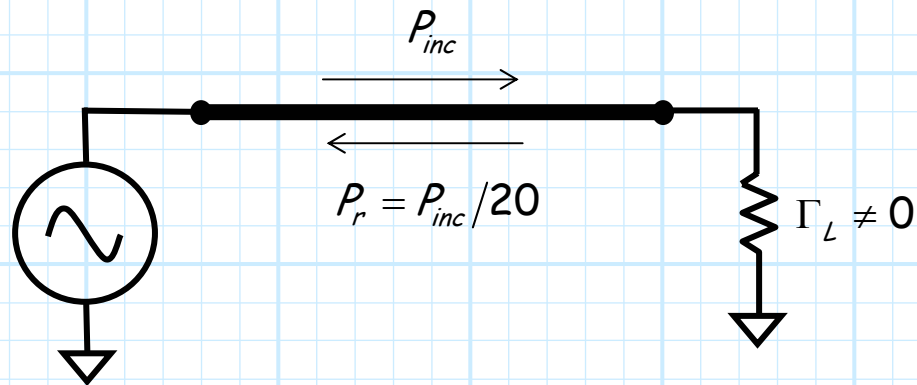For example, consider the case where the **return loss** of a mismatched load is 13 dB:



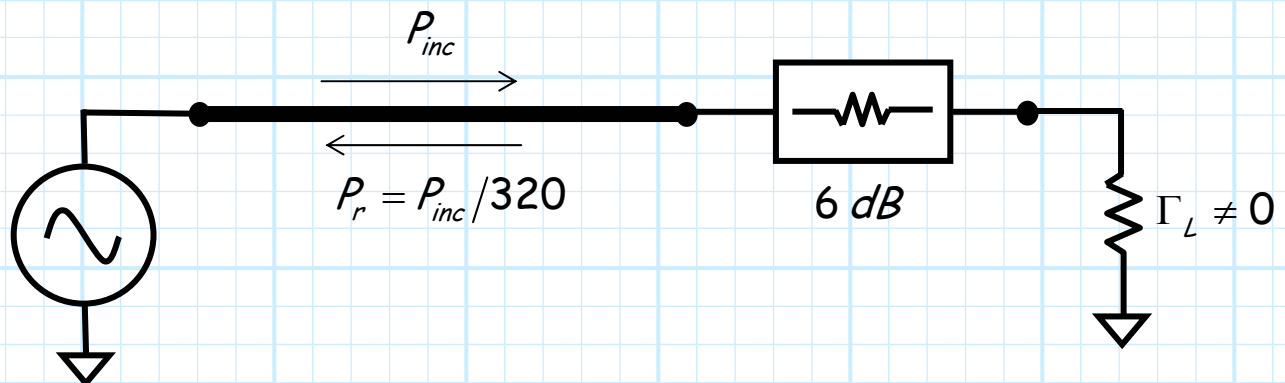Say we now add a **6 dB pad** between the source and the load—we find that the return loss has **improved** to 25 dB!



The reason that the return loss improves by 12 dB (as opposed to 6 dB) is that reflected power is attenuated **twice**—once as it travels toward the load, and again after it is reflected from it.

Note from the standpoint of the source, the load is much **better matched**. As a result, the effect of **pulling** is reduced.

However, there is a definite downside to "matching" with a **fixed** attenuator—the power **delivered** to the load is also **reduced** by 6 dB!



**Q:** *Why do you keep referring to these devices as **fixed** attenuators? Do you really think we would use a **broken** one?*

**A:** In addition to fixed attenuators, engineers often used **variable** attenuators in radio system designs. A variable attenuator is a device whose attenuation can be **adjusted** (i.e., varied).


There are two types of (electronically) adjustable attenuators: **digital** and **voltage controlled**.

### Digital Attenuators

As the name implies, digital attenuators are controlled with a set of **digital** (i.e., binary) **control lines**. As a result, the attenuator can be set to a specific number of **discrete** values.


For example, a 6-bit attenuator can be set to one of  $2^6 = 64$  **different** attenuation values!

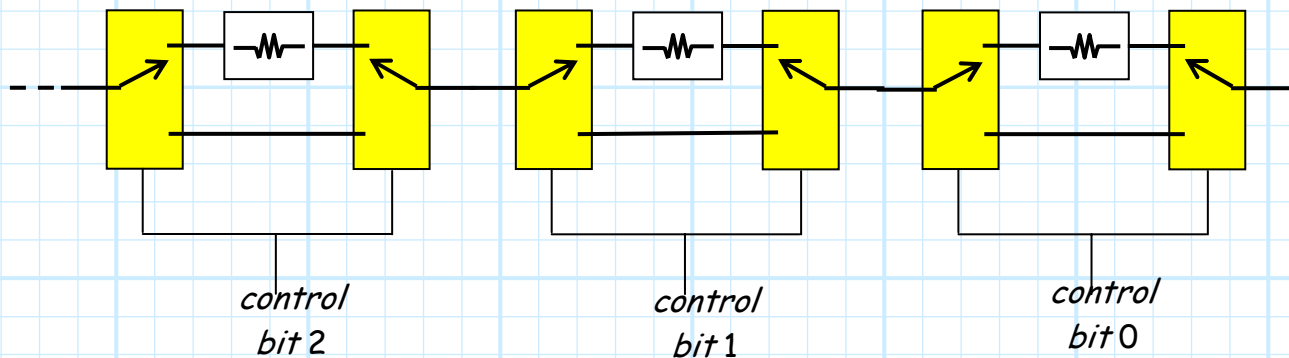Digital attenuators are typically made from **switches** and **fixed attenuators**, arranged in the following form:




Theoretically, we can construct a digital attenuator with as **many** sections as we wish. However, because of **switch insertion loss**, digital attenuators typically use no more than 8 to 10 bits (i.e., 8 to 10 sections).

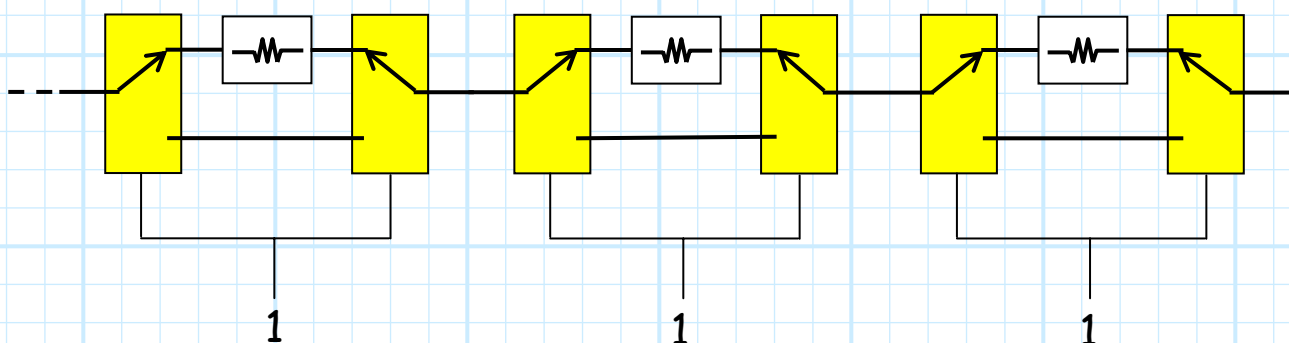
It is apparent from the schematic above that each section allows us to switch in its attenuator into the signal path (maximum attenuation):



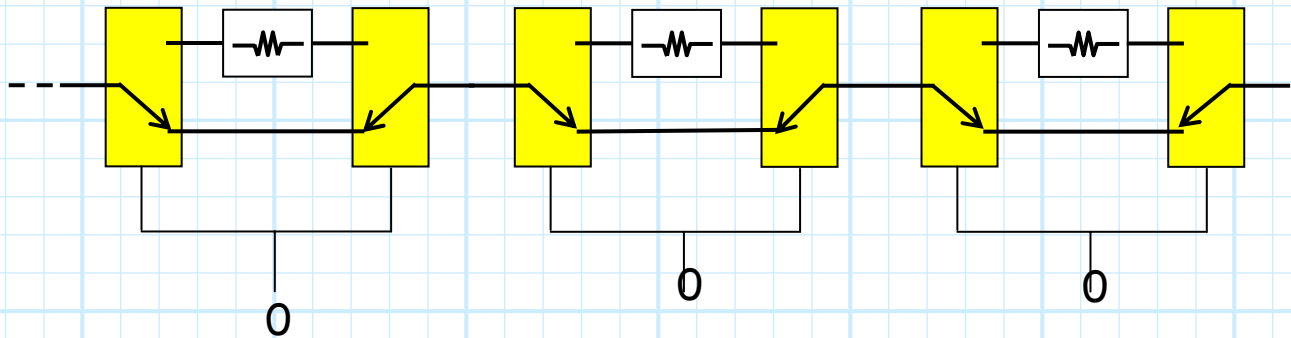Or we can **bypass** the attenuators, thus providing no attenuation (except for switch insertion loss!):



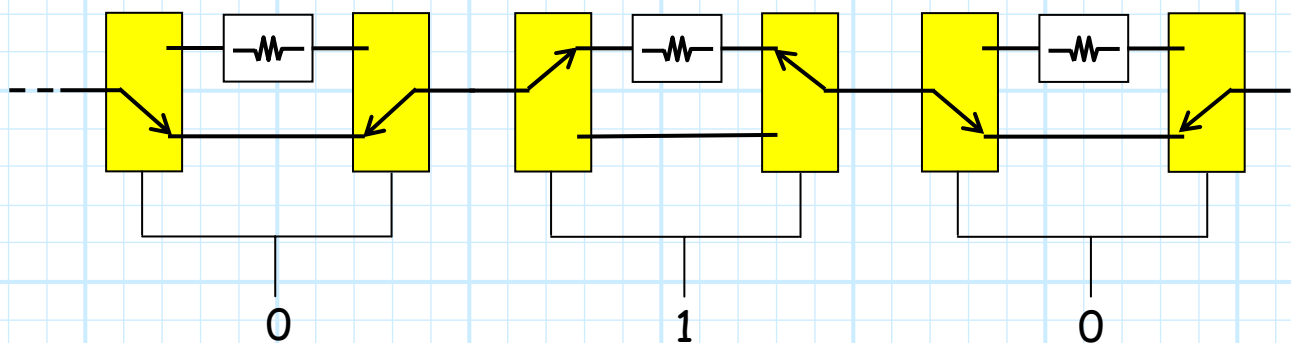Or we can select **some** attenuators and bypass **others**, thus setting the attenuation to be somewhere in between max and min!



For most digital attenuators, the attenuation of each section has a **different** value, and almost always are selected such that the values in dB are **binary**.

For example, consider a 6-bit digital attenuator. A typical design might use **these** attenuator values:

	bit 5	bit 4	bit 3	bit 2	bit 1	bit 0
attenuator	32 dB	16 dB	8 dB	4 dB	2 dB	1 dB

We note therefore, that by selecting the proper switches, we can select **any** attenuation between 0 dB and 63 dB, in **steps** of 1 dB.


For **example**, the 6-bit binary word 101101 would result in attenuation of:

$$32 + 8 + 4 + 1 = 45 \text{ dB}$$

Note also that 101101 is the **binary** representation of the **decimal** number 45—the binary control word **equals** the attenuation in dB!!
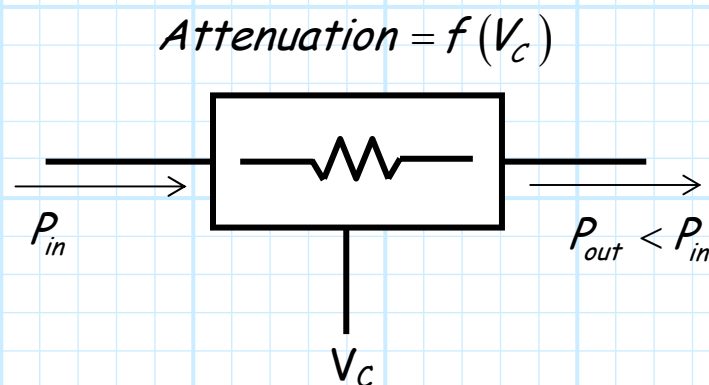
### Voltage Controlled Attenuators

Another adjustable attenuator is the **voltage-controlled attenuator**. This device uses a **single** control line, with the **voltage** at that control determining the attenuation of the device (an "analog" attenuator!):



Typical voltage control attenuators can provide attenuation from a **minimum** of a few dB to a **maximum** of as much as 50 dB.

Unlike the digital attenuator, this attenuation range is a **continuous** function of  $V_c$ , so that **any** and every attenuation between the minimum and maximum values can be selected.

Voltage controlled attenuators are typically **smaller**, simpler, and **cheaper** than their digital counterparts.



**Q:** *So why did you waste our time with digital attenuators? It sounds like voltage controlled attenuators are **always** the way to go!*

**A:** We have yet to discuss the **bad stuff** about voltage controlled attenuators!

- \* Voltage controlled attenuators are generally speaking **poorly matched**, with a return loss that varies with the control voltage  $V_c$ .
- \* Likewise, the phase delay, bandwidth, and just about every other device parameter also **changes** with  $V_c$ !
- \* Moreover, voltage controlled attenuators are notoriously **sensitive** to temperature, power supply variations, and load impedance.

Digital attenuators, on the other hand, generally exhibit **none** of the problems!

In addition, digital attenuators are ready made for integration with **digital controllers** or processors (i.e., computers).

However, digital attenuators do have a downside—they **can** be relatively large and **expensive**.

# The Digital Attenuator Specification Sheet

## Number of Sections

Equal to the number of bits.

## Bandwidth (Hz)

This device, like all other devices, can effectively operate only within a finite bandwidth (e.g., 2-5 GHz or 300-400 MHz).

## Port Impedance ( $\Gamma$ , return loss, VSWR)

## Insertion Loss (dB)

This is defined as the attenuation of the device in its **minimum** attenuation state (i.e., no attenuators are selected). Ideally, this would be 0 dB. However, the insertion loss of the **switches** makes this ideal value unachievable.

Typically, insertion loss will be equal to approximately 1 dB per bit. In other words a 6-bit attenuator will have an insertion loss of 6dB.

## DC Power

See microwave switch spec sheet.



### Maximum Attenuation (dB)

The attenuation of the device with **all** fixed attenuators selected. This value is therefore the sum (in dB) of every fixed attenuator, **plus** the insertion loss discussed above. Remember, the insertion loss of the switches is prevalent regardless of the attenuator state.

### Attenuation Step Size (dB)

The vast majority of digital attenuators have attenuation states that are separated by a **fixed** value (e.g., 0.5, 1.0, or 2 dB).

### Maximum Input power (dBm)

Digital attenuators have a **maximum** input power.

### Switching Speed (seconds)

The state of a microwave switch **cannot** change instantaneously. It takes some small but non-zero amount of time to change from one attenuation state to another. Typical values range from 0.1 to 20.0  $\mu$ seconds.

### Switch Logic

See microwave switch spec sheet.

# PIN Diodes

**Q:** *Just how do we **make switches and voltage controlled attenuators?***

**A:** Typically, they are constructed with **PIN diodes**.

A PIN diode is simply a *p-n* junction diode that is designed to have a very **small junction capacitance** (0.01 to 0.1 pf).

→ Sort of the **opposite** of the **varactor diode!**

To see why this is important, recall diode **small signal analysis** from your first electronics course.

In small signal analysis, the **total** diode voltage consists of a **D.C. bias voltage** ( $V_0$ ) and a **small, time-varying signal** ( $v_d$ ):

$$v_D(t) = V_0 + v_d(t)$$

For radio engineering applications, the small signal is a **microwave signal** !!! I.E.,:

$$v_D(t) = V_0 + v_{RF}(t)$$

Thus, we know that the **diode current**  $i_D$  is:

$$i_D = I_s \left( \exp \left[ \frac{V_0 + v_{RF}(t)}{nV_T} \right] - 1 \right)$$

Since  $v_{RF}$  is very **small**, we can **approximate** this diode current  $i_D(v_D)$  using a **Taylor Series** expansion around  $v_D = V_0$ :

$$\begin{aligned} i_D(v_D) &\approx i_D(v_D)\Big|_{v_D=V_0} + \frac{\partial i_D(v_D)}{\partial v_D}\Big|_{v_D=V_0} v_{RF}(t) \\ &= I_S \left( e^{V_0/nV_T} - 1 \right) + \frac{I_S e^{V_0/nV_T}}{nV_T} v_{RF}(t) \end{aligned}$$

We recognize that:

$$I_S \left( e^{V_0/nV_T} - 1 \right) = \text{D.C. Bias Current} \doteq I_0$$

and thus we can write our **small-signal approximation** as:

$$\begin{aligned} i_D &= I_0 + \frac{(I_0 + I_S)}{nV_T} v_{RF}(t) \\ &= I_0 + \frac{v_{RF}(t)}{r_d} \end{aligned}$$

where we have defined the diode **small-signal resistance**  $r_d$  as:

$$r_d = \frac{nV_T}{I_0 + I_S}$$

The diode small-signal resistance is also **often** referred to as the **junction** resistance  $R_j$  or the **series** resistance  $R_s$ .

We can further conclude that the total diode current  $i_D$  is the sum of the D.C. bias current  $I_0$ , and the **small-signal current**  $i_{RF}(t)$ , where:

$$i_{RF}(t) = \frac{v_{RF}(t)}{r_d}$$

→ Just like **Ohm's Law** !

To a small (i.e., low power) microwave signal, a diode "looks" like a **resistor**.


Moreover, we can **control** and **modify** the resistance of the diode by **changing** the D.C. bias.

→ Sort of a **voltage-controlled** resistor!

For example, if we put the diode into **forward** bias ( $V_0 \gg nV_T$ ), the bias current  $I_0$  will be positive and **big**, thus the junction resistance will be very **small** (e.g.,  $r_d =$  a few ohms).

→ A **forward** biased diode is very nearly a microwave **short circuit**!

$$r_d = \frac{nV_T}{I_0 + I_s}$$

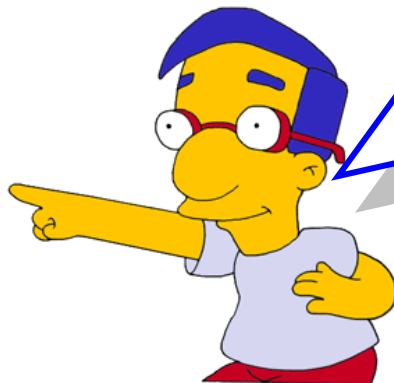


*I get it! If we **reverse** bias our diode, such that  $V_0 \ll -nV_T$ , the bias current  $I_0$  will be **nearly** equal to  $-I_s$ . As a result, the **series resistance** will be **hugemungous**!*

Not so fast! The small-signal **resistance** of a **reverse** biased diode is in fact **very large**. BUT, we must also consider the junction **capacitance**  $C_j$ !




Recall that in **reverse** bias, the junction capacitance of a diode can be **significant**, and in fact generally **increases** as the bias voltage becomes more negative!

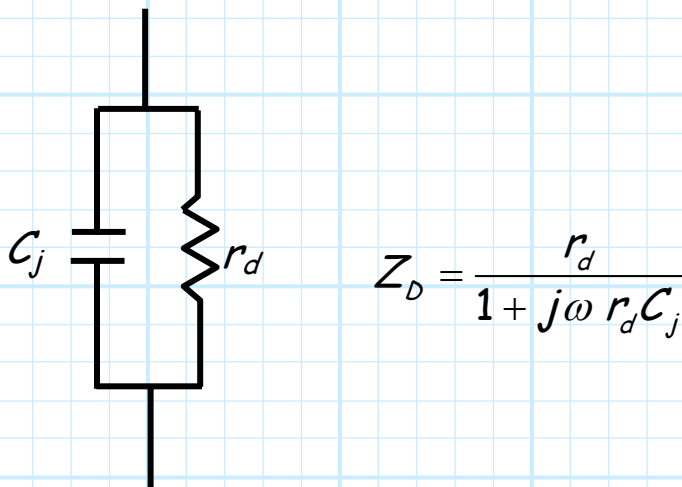As a result, a good microwave circuit **model** of a diode includes both the series resistance and junction capacitance:



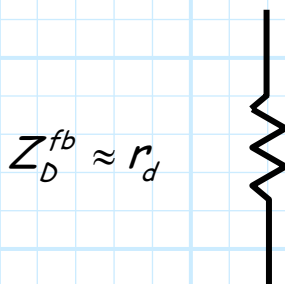For **forward** bias, where  $r_d$  is **very small**, we find that diode impedance  $Z_D$  is approximately equal to this **small series resistance** ( $Z_D \approx r_d$ )—a **short circuit** (approximately):



For reverse bias, where  $r_d$  is **very large**, we find that diode impedance  $Z_D$  is approximately equal to that of the junction capacitance  $C_j$ :

$$\begin{array}{c} | \\ | \\ \text{---} \\ | \\ | \\ | \end{array} \quad Z_D^{rb} = \frac{1}{j\omega C_j}$$

For low-frequencies (e.g., kHz), this impedance will be typically be **very large** and thus the diode can be approximate as an **open** circuit.

However, at microwave frequencies (where  $\omega$  is very large) the reverse bias impedance  $Z_D^{rb}$  may **not** be particularly large, and thus the reverse biased diode **cannot** be considered an open circuit.

In order for the impedance  $Z_D^{rb} = 1/j\omega C_j$  to be very **large** at **microwave** frequencies, the junction capacitance  $C_j$  must be **very, very small**.



***PIN** diodes! I bet that's why we use **PIN** diodes!*

That's **exactly** why! A PIN diode is **approximately** a (bias) **voltage controlled resistor** at microwave frequencies. We can select any value of  $r_d$  from a **short** to an **open**.

As a result, we can make **many** interesting devices!