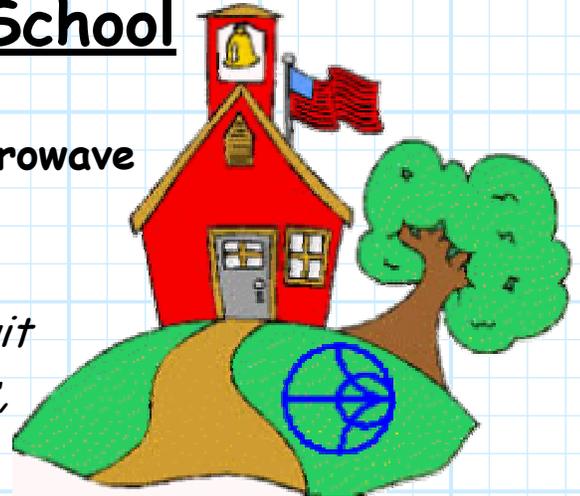


## 2. Microwave School

We design radio systems using **RF/microwave** components.

**Q:** *Why don't we use the "usual" circuit components (e.g., resistors, capacitors, op-amps, transistors) ??*



**A:** We **do** use these! But we require new devices because:

1. Our circuits are generally  $> \lambda$  in **size** !
2. We require **new** functions that "non-RF" devices cannot provide.

### **A. Transmission Line Theory**

The most important fact about microwave devices is that they are connected together using transmission lines.

**Q:** *So just what is a transmission line?*

**A:** A passive, linear, two port device that allows bounded E. M. energy to flow from one device to another.

→ Sort of an "electromagnetic pipe" !

**Q:** *Oh, so it's simply a conducting wire, right?*



**A:** NO! At high frequencies, things get much more complicated!

### HO: The Telegraphers Equations

### HO: Time-Harmonic Solutions for Linear Circuits

**Q:** *So, what complex functions  $I(z)$  and  $V(z)$  do satisfy both telegrapher equations?*

**A:** The solutions to the transmission line wave equations!

### HO: The Transmission Line Wave Equations

**Q:** *Are the solutions for  $I(z)$  and  $V(z)$  completely independent, or are they related in any way?*

**A:** The two solutions are related by the transmission line characteristic impedance.

### HO: The Transmission Line Characteristic Impedance

**Q:** *So what is the significance of the constant  $\beta$ ? What does it tell us?*

**A:** It describes the propagation of each wave along the transmission line.

### HO: The Propagation Constant

**Q:** *Is characteristic impedance  $Z_0$  the same as the concept of impedance I learned about in circuits class?*

**A:** **NO!** The  $Z_0$  is a **wave impedance**. However, we can also define **line impedance**, which is the same as that used in circuits.

### HO: Line Impedance


**Q:** *These wave functions  $V^+(z)$  and  $V^-(z)$  seem to be important. How are they related?*

**A:** They are in fact **very** important! They are related by a function called the **reflection coefficient**.

### HO: The Reflection Coefficient

# The Telegrapher Equations

Consider a section of "wire":

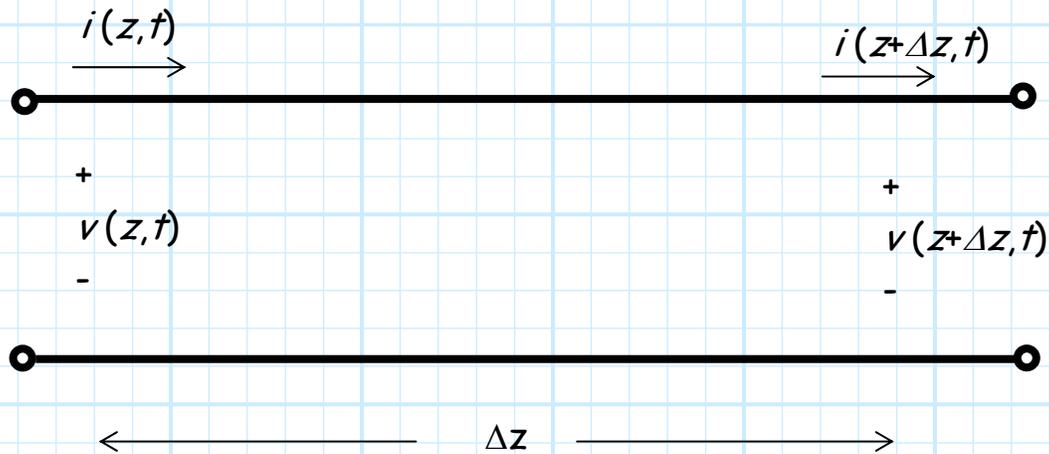


**Q:** Huh ?! Current  $i$  and voltage  $v$  are a function of position  $z$  ??  
Shouldn't  $i(z,t) = i(z + \Delta z,t)$  and  $v(z,t) = v(z + \Delta z,t)$  ?

**A:** NO ! Because a wire is never a **perfect** conductor.

A "wire" will have:

- 1) Inductance
- 2) Resistance
- 3) Capacitance
- 4) Conductance

i.e.,

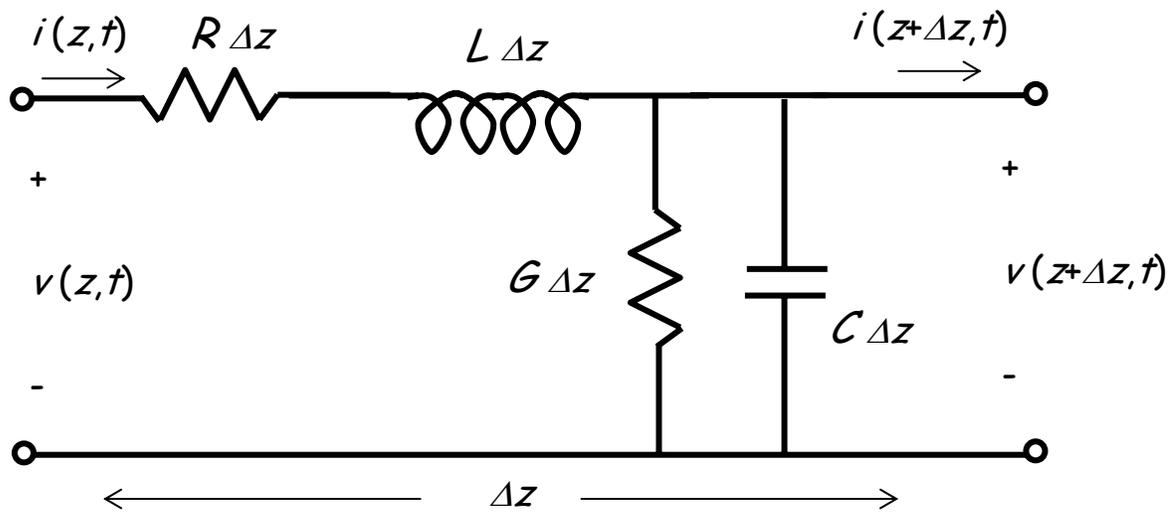

Where:

$R$  = resistance/unit length

$L$  = inductance/unit length

$C$  = capacitance/unit length

$G$  = conductance/unit length

$\therefore$  resistance of wire length  $\Delta z$  is  $R\Delta z$ .

Using KVL, we find:

$$v(z + \Delta z, t) - v(z, t) = -R\Delta z i(z, t) - L\Delta z \frac{\partial i(z, t)}{\partial t}$$

and from KCL:

$$i(z + \Delta z, t) - i(z, t) = -G\Delta z v(z, t) - C\Delta z \frac{\partial v(z, t)}{\partial t}$$

Dividing the first equation by  $\Delta z$ , and then taking the limit as  $\Delta z \rightarrow 0$ :

$$\lim_{\Delta z \rightarrow 0} \frac{v(z + \Delta z, t) - v(z, t)}{\Delta z} = -R i(z, t) - L \frac{\partial i(z, t)}{\partial t}$$

which, by definition of the derivative, becomes:

$$\frac{\partial v(z, t)}{\partial z} = -R i(z, t) - L \frac{\partial i(z, t)}{\partial t}$$

Similarly, the KCL equation becomes:

$$\frac{\partial i(z, t)}{\partial z} = -G v(z, t) - C \frac{\partial v(z, t)}{\partial t}$$

These equations are known as the **telegrapher's equations** !

$$\frac{\partial v(z, t)}{\partial z} = -R i(z, t) - L \frac{\partial i(z, t)}{\partial t}$$

$$\frac{\partial i(z, t)}{\partial z} = -G v(z, t) - C \frac{\partial v(z, t)}{\partial t}$$


# Time-Harmonic Solutions for Linear Circuits

There are an unaccountably **infinite** number of solutions  $v(z,t)$  and  $i(z,t)$  for the telegrapher's equations! However, we can simplify the problem by assuming that the function of time is **time harmonic** (i.e., sinusoidal), oscillating at some **radial frequency**  $\omega$  (e.g.,  $\cos \omega t$ ).

**Q:** *Why on earth would we assume a **sinusoidal** function of time? Why not a **square wave**, or **triangle wave**, or a "sawtooth" function?*

**A:** We assume **sinusoids** because they have a **very special** property!

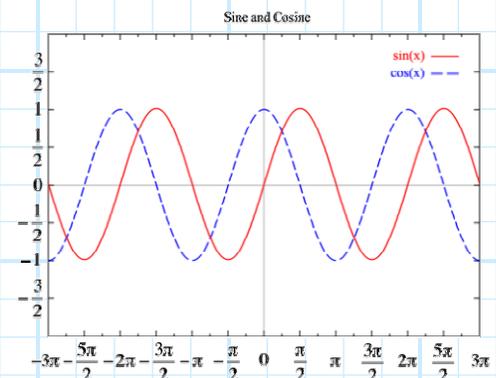Sinusoidal time functions—and **only** a sinusoidal time functions—are the **eigen functions** of **linear, time-invariant** systems.




**Q:** ???

**A:** If a sinusoidal voltage source with frequency  $\omega$  is used to excite a linear, time-invariant circuit (and a transmission line is **both** linear and time invariant!), then the voltage at each

and **every** point with the circuit will likewise vary sinusoidally—at the same frequency  $\omega$ !

**Q:** *So what? Isn't that obvious?*

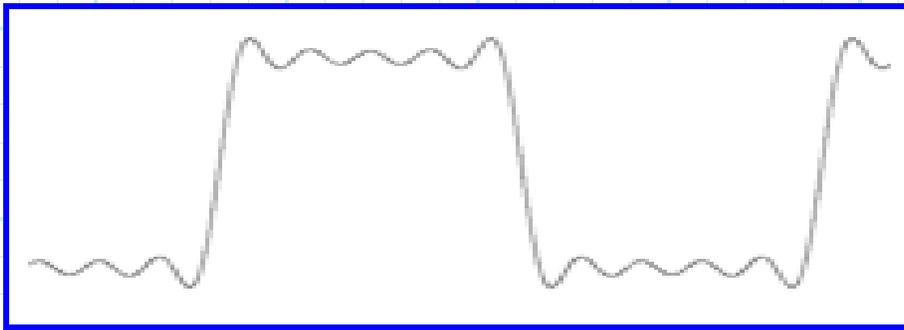**A:** Not at all! If you were to excite a linear circuit with a **square wave**, or **triangle wave**, or **sawtooth**, you would find that—generally speaking—**nowhere** else in the circuit is the voltage a perfect square wave, triangle wave, or sawtooth. The linear circuit will effectively **distort** the input signal into something **else**!



**Q:** *Into what function will the input signal be distorted?*

**A:** It depends—both on the original form of the **input signal**, and the parameters of the **linear circuit**. At **different** points within the circuit we will discover **different** functions of time—**unless**, of course, we use a **sinusoidal** input. Again, for a sinusoidal excitation, we find at **every** point within circuit an **undistorted** sinusoidal function!

**Q:** *So, the sinusoidal function at every point in the circuit is exactly the same as the input sinusoid?*

**A:** Not quite **exactly** the same. Although at every point within the circuit the voltage will be precisely sinusoidal (with frequency  $\omega$ ), the **magnitude** and **relative phase** of the sinusoid will generally be different at each and every point within the circuit.

Thus, the voltage along a transmission line—when excited by a sinusoidal source—**must** have the form:

$$v(z, t) = v(z) \cos(\omega t + \varphi(z))$$

Thus, at some arbitrary location  $z$  along the transmission line, we **must** find a time-harmonic oscillation of **magnitude**  $v(z)$  and **relative phase**  $\varphi(z)$ .

Now, consider Euler's equation, which states:

$$e^{j\psi} = \cos \psi + j \sin \psi$$

Thus, it is apparent that:

$$\operatorname{Re}\{e^{j\psi}\} = \cos \psi$$

and so we conclude that the voltage on a transmission line can be expressed as:

$$\begin{aligned} v(z, t) &= v(z) \cos(\omega t + \varphi(z)) \\ &= \operatorname{Re}\{v(z) e^{j(\omega t + \varphi(z))}\} \\ &= \operatorname{Re}\{v(z) e^{+j\varphi(z)} e^{j\omega t}\} \end{aligned}$$

Thus, we can specify the time-harmonic voltage at each an every location  $z$  along a transmission line with the **complex** function  $V(z)$ :

$$V(z) = v(z)e^{-j\varphi(z)}$$

where the **magnitude** of the complex function is the **magnitude** of the sinusoid:

$$v(z) = |V(z)|$$

and the phase of the complex function is the relative phase of the sinusoid :

$$\varphi(z) = \arg\{V(z)\}$$

**Q:** *Hey wait a minute! What happened to the time-harmonic function  $e^{j\omega t}$  ??*

**A:** There really is no reason to **explicitly** write the complex function  $e^{j\omega t}$ , since we know in fact (being the eigen function of linear systems and all) that if this is the time function at any **one** location (such as at the excitation source) then this must be time function at **all** transmission line locations  $z$ !

The only **unknown** is the **complex** function  $V(z)$ . Once we determine  $V(z)$ , we can always (if we so desire) "recover" the **real** function  $v(z,t)$  as:

$$v(z,t) = \operatorname{Re}\{V(z)e^{j\omega t}\}$$

Thus, if we assume a **time-harmonic source**, finding the transmission line solution  $v(z, t)$  reduces to solving for the **complex function**  $V(z)$ .

# The Transmission Line Wave Equation

Let's assume that  $v(z,t)$  and  $i(z,t)$  each have the time-harmonic form:

$$v(z,t) = \text{Re}\{V(z)e^{j\omega t}\} \quad \text{and} \quad i(z,t) = \text{Re}\{I(z)e^{j\omega t}\}$$

The time-derivative of these functions are:

$$\frac{\partial v(z,t)}{\partial t} = \text{Re}\left\{V(z)\frac{\partial e^{j\omega t}}{\partial t}\right\} = \text{Re}\{j\omega V(z)e^{j\omega t}\}$$

$$\frac{\partial i(z,t)}{\partial t} = \text{Re}\left\{I(z)\frac{\partial e^{j\omega t}}{\partial t}\right\} = \text{Re}\{j\omega I(z)e^{j\omega t}\}$$

The telegrapher's equations thus become:

$$\text{Re}\left\{\frac{\partial V(z)}{\partial z} e^{j\omega t}\right\} = \text{Re}\{-(R + j\omega L)I(z)e^{j\omega t}\}$$

$$\text{Re}\left\{\frac{\partial I(z)}{\partial z} e^{j\omega t}\right\} = \text{Re}\{-(G + j\omega C)V(z)e^{j\omega t}\}$$

And then simplifying, we have the **complex** form of **telegrapher's equations**:

$$\frac{\partial V(z)}{\partial z} = -(R + j\omega L)I(z)$$

$$\frac{\partial I(z)}{\partial z} = -(\mathcal{G} + j\omega \mathcal{C})V(z)$$

Note that these complex differential equations are **not** a function of time  $t$ !

- \* The functions  $I(z)$  and  $V(z)$  are **complex**, where the **magnitude** and **phase** of the complex functions describe the **magnitude** and **phase** of the sinusoidal time function  $e^{j\omega t}$ .
- \* Thus,  $I(z)$  and  $V(z)$  describe the current and voltage along the transmission line, as a function as position  $z$ .
- \* **Remember**, not just **any** function  $I(z)$  and  $V(z)$  can exist on a transmission line, but rather **only** those functions that satisfy the **telegraphers equations**.



Our task, therefore, is to **solve** the telegrapher equations and find **all** solutions  $I(z)$  and  $V(z)$ !

**Q:** So, what functions  $I(z)$  and  $V(z)$  do satisfy both telegrapher's equations??

**A:** To make this easier, we will combine the telegrapher equations to form **one** differential equation for  $V(z)$  and **another** for  $I(z)$ .

First, take the **derivative** with respect to  $z$  of the **first** telegrapher equation:

$$\frac{\partial}{\partial z} \left\{ \frac{\partial V(z)}{\partial z} = -(R + j\omega L) I(z) \right\}$$

$$= \frac{\partial^2 V(z)}{\partial z^2} = -(R + j\omega L) \frac{\partial I(z)}{\partial z}$$

Note that the **second** telegrapher equation expresses the derivative of  $I(z)$  in terms of  $V(z)$ :

$$\frac{\partial I(z)}{\partial z} = -(G + j\omega C) V(z)$$

Combining these two equations, we get an equation involving  $V(z)$  **only**:

$$\frac{\partial^2 V(z)}{\partial z^2} = (R + j\omega L)(G + j\omega C) V(z)$$

Now, we find at high frequencies that:

$$R \ll j\omega L \quad \text{and} \quad G \ll j\omega C$$

and so we can **approximate** the differential equation as:

$$\frac{\partial^2 V(z)}{\partial z^2} = (j\omega L)(j\omega C)V(z) = \omega^2 LC V(z) = \beta^2 V(z)$$

where it is apparent that:

$$\beta^2 \doteq \omega^2 LC$$

In a **similar** manner (i.e., begin by taking the derivative of the **second** telegrapher equation), we can derive the differential equation:

$$\frac{\partial^2 I(z)}{\partial z^2} = \beta^2 I(z)$$

We have **decoupled** the telegrapher's equations, such that we now have **two** equations involving **one** function only:

$$\frac{\partial^2 V(z)}{\partial z^2} = \beta^2 V(z)$$

$$\frac{\partial^2 I(z)}{\partial z^2} = \beta^2 I(z)$$

These are known as the **transmission line wave equations**.

Note only **special** functions satisfy these equations: if we take the double derivative of the function, the result is the **original function** (to within a constant)!



**Q:** *Yeah right! Every function that I know is **changed** after a double differentiation. What kind of "magical" function could possibly satisfy this differential equation?*

**A:** Such functions **do** exist !

For example, the functions  $V(z) = e^{-j\beta z}$  and  $V(z) = e^{+j\beta z}$  each satisfy this transmission line wave equation (insert these into the differential equation and see for **yourself!**).

Likewise, since the transmission line wave equation is a **linear** differential equation, a weighted **superposition** of the two solutions is **also a solution** (again, insert this solution to and see for **yourself!**):

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

In fact, it turns out that **any** and **all** possible solutions to the differential equations can be expressed in **this** simple form!

Therefore, the **general** solution to these wave equations (and thus the telegrapher equations) are:

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

$$I(z) = I_0^+ e^{-j\beta z} + I_0^- e^{+j\beta z}$$

where  $V_0^+$ ,  $V_0^-$ ,  $I_0^+$ , and  $I_0^-$  are **complex constants**.

→ It is **unfathomably** important that **you** understand what this result means!

It means that the functions  $V(z)$  and  $I(z)$ , describing the current and voltage at **all** points  $z$  along a transmission line, can **always** be **completely** specified with just **four complex constants** ( $V_0^+$ ,  $V_0^-$ ,  $I_0^+$ ,  $I_0^-$ )!!

We can **alternatively** write these solutions as:

$$V(z) = V^+(z) + V^-(z)$$

$$I(z) = I^+(z) + I^-(z)$$

where:


$$V^+(z) \doteq V_0^+ e^{-j\beta z}$$

$$V^-(z) \doteq V_0^- e^{+j\beta z}$$

$$I^+(z) \doteq I_0^+ e^{-j\beta z}$$

$$I^-(z) \doteq I_0^- e^{+j\beta z}$$

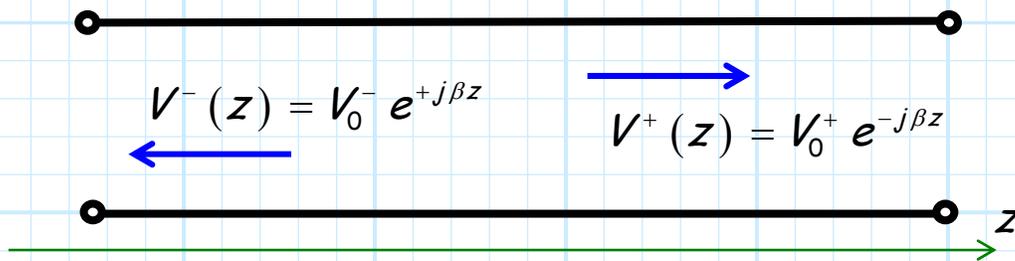The two terms in each solution describe **two waves** propagating in the transmission line, **one wave** ( $V^+(z)$  or  $I^+(z)$ ) propagating in one direction ( $+z$ ) and the **other wave** ( $V^-(z)$  or  $I^-(z)$ ) propagating in the **opposite** direction ( $-z$ ).



**Q:** So just what **are** the complex values  $V_0^+$ ,  $V_0^-$ ,  $I_0^+$ ,  $I_0^-$  ?

**A:** Consider the wave solutions at **one** specific point on the transmission line—the point  $z = 0$ . For example, we find that:

$$\begin{aligned} V^+(z=0) &= V_0^+ e^{-j\beta(z=0)} \\ &= V_0^+ e^{-(0)} \\ &= V_0^+ (1) \\ &= V_0^+ \end{aligned}$$

In other words,  $V_0^+$  is simply the **complex** value of the wave function  $V^+(z)$  at the point  $z=0$  on the transmission line!

Likewise, we find:

$$V_0^- = V^-(z = 0)$$


$$I_0^+ = I^+(z = 0)$$

$$I_0^- = I^-(z = 0)$$

Again, the four complex values  $V_0^+$ ,  $I_0^+$ ,  $V_0^-$ ,  $I_0^-$  are **all** that is needed to determine the voltage and current at any and all points on the transmission line.

More specifically, **each** of these four complex constants completely specifies **one** of the four transmission line wave functions  $V^+(z)$ ,  $I^+(z)$ ,  $V^-(z)$ ,  $I^-(z)$ .

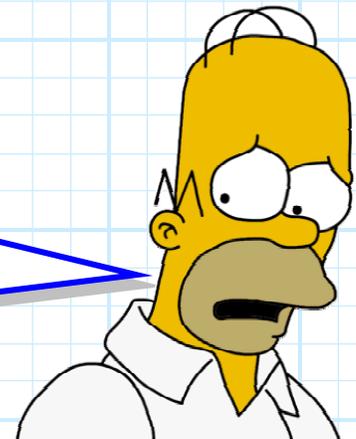**Q:** *But what **determines** these wave functions? How do we **find** the values of constants  $V_0^+$ ,  $I_0^+$ ,  $V_0^-$ ,  $I_0^-$ ?*



**A:** As you might expect, the voltage and current on a transmission line is determined by the devices **attached** to it on either end (e.g., active sources and/or passive loads)!

The precise values of  $V_0^+$ ,  $I_0^+$ ,  $V_0^-$ ,  $I_0^-$  are therefore determined by satisfying the **boundary conditions** applied at **each end** of the transmission line—much more on this **later!**

# The Characteristic Impedance of a Transmission Line

So, from the telegrapher's differential equations, we know that the complex current  $I(z)$  and voltage  $V(z)$  must have the form:

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

$$I(z) = I_0^+ e^{-j\beta z} + I_0^- e^{+j\beta z}$$

Let's insert the expression for  $V(z)$  into the first telegrapher's equation, and **see what happens!**

$$\frac{dV(z)}{dz} = -j\beta V_0^+ e^{-j\beta z} + j\beta V_0^- e^{+j\beta z} = -j\omega L I(z)$$


Therefore, rearranging,  $I(z)$  must be:

$$I(z) = \frac{\beta}{\omega L} (V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z})$$

**Q:** *But wait! I thought we already knew current  $I(z)$ . Isn't it:*

$$I(z) = I_0^+ e^{-j\beta z} + I_0^- e^{+j\beta z} \quad ??$$

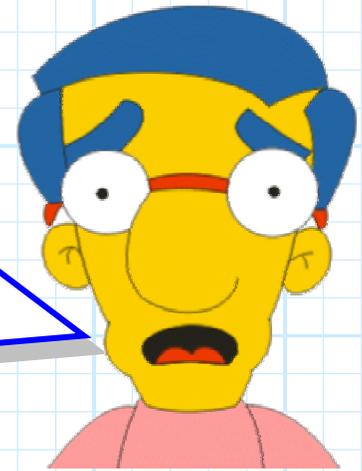*How can both expressions for  $I(z)$  be true??*



**A:** Easy! Both expressions for current are **equal** to each other.

$$I(z) = I_0^+ e^{-j\beta z} + I_0^- e^{+j\beta z} = \frac{\beta}{\omega L} (V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z})$$

For the above equation to be true for **all**  $z$ ,  $I_0$  and  $V_0$  must be related as:

$$I_0^+ e^{-\gamma z} = \left( \frac{\beta}{\omega L} \right) V_0^+ e^{-\gamma z} \quad \text{and} \quad I_0^- e^{+\gamma z} = \left( \frac{-\beta}{\omega L} \right) V_0^- e^{+\gamma z}$$

Or—recalling that  $V_0^+ e^{-j\beta z} = V^+(z)$  (etc.)—we can express this in terms of the **two propagating waves**:

$$I^+(z) = \left( \frac{\beta}{\omega L} \right) V^+(z) \quad \text{and} \quad I^-(z) = \left( \frac{-\beta}{\omega L} \right) V^-(z)$$

Now, we note that since:

$$\beta = \omega \sqrt{LC}$$

We find that:

$$\frac{\beta}{\omega L} = \frac{\omega\sqrt{LC}}{\omega L} = \sqrt{\frac{C}{L}}$$

Thus, we come to the **startling** conclusion that:

$$\frac{V^+(z)}{I^+(z)} = \sqrt{\frac{L}{C}} \quad \text{and} \quad \frac{-V^-(z)}{I^-(z)} = \sqrt{\frac{L}{C}}$$

**Q:** *What's so startling about **this** conclusion?*

**A:** Note that although the magnitude and phase of each propagating wave is a **function** of transmission line **position**  $z$  (e.g.,  $V^+(z)$  and  $I^+(z)$ ), the **ratio** of the voltage and current of **each wave** is independent of position—a **constant** with respect to position  $z$ !

Although  $V_0^\pm$  and  $I_0^\pm$  are determined by **boundary conditions** (i.e., what's connected to either end of the transmission line), the **ratio**  $V_0^\pm/I_0^\pm$  is determined by the parameters of the transmission line **only** ( $R, L, G, C$ ).

→ This ratio is an important **characteristic** of a transmission line, called its **Characteristic Impedance**  $Z_0$ .

$$Z_0 \doteq \frac{V_0^+}{I_0^+} = \frac{-V_0^-}{I_0^-} = \sqrt{\frac{L}{C}}$$

We can therefore describe the current and voltage along a transmission line as:

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{+j\beta z}$$

or equivalently:

$$V(z) = Z_0 I_0^+ e^{-j\beta z} - Z_0 I_0^- e^{+j\beta z}$$

$$I(z) = I_0^+ e^{-j\beta z} + I_0^- e^{+j\beta z}$$

Note that instead of characterizing a transmission line with **real** parameters  $L$  and  $C$ , we can (and typically do!) describe a lossless transmission line using real parameters  $Z_0$  and  $\beta$ .

# The Propagation Constant $\beta$

Recall that the activity along a transmission line can be expressed in terms of two functions, functions that we have described as **wave functions**:

$$V^+(z) = V_0^+ e^{-j\beta z}$$

$$V^-(z) = V_0^- e^{+j\beta z}$$

where  $\beta$  is a real constant with value:

$$\beta = \omega\sqrt{LC}$$

**Q:** *What is this constant  $\beta$ ? What does it **physically** represent?*

**A:** Remember, a complex function can be expressed in terms of its **magnitude** and **phase**:

$$f(z) = |f(z)| e^{j\phi_f(z)}$$

Thus:

$$|V^+(z)| = |V_0^+| \quad \phi^+(z) = -\beta z + \phi_0^+$$

$$|V^-(z)| = |V_0^-| \quad \phi^-(z) = +\beta z + \phi_0^-$$

Therefore,  $-\beta z + \phi_0^+$  represents the relative **phase** of wave  $V^+(z)$ ; a **function** of transmission line **position**  $z$ . Since phase  $\phi$  is expressed in **radians**, and  $z$  is distance (in meters), the value  $\beta$  must have **units** of:

$$\beta = \frac{\phi}{z} \quad \frac{\text{radians}}{\text{meter}}$$

The **wavelength**  $\lambda$  of the propagating wave is defined as the **distance**  $\Delta z_{2\pi}$  over which the relative phase changes by  $2\pi$  **radians**. So:

$$2\pi = \phi(z + \Delta z_{2\pi}) - \phi(z) = \beta \Delta z_{2\pi} = \beta \lambda$$

or, rearranging:

$$\beta = \frac{2\pi}{\lambda}$$

Thus, the value  $\beta$  is thus essentially a **spatial frequency**, in the same way that  $\omega$  is a temporal frequency:

$$\omega = \frac{2\pi}{T}$$

where  $T$  is the **time** required for the phase of the oscillating signal to change by a value of  $2\pi$  radians, i.e.:

$$\omega T = 2\pi$$

Note that this time is the **period** of a sinewave, and related to its **frequency** in Hertz (cycles/second) as:

$$T = \frac{2\pi}{\omega} = \frac{1}{f}$$

**Q:** *So, just how fast does this wave propagate down a transmission line?*

We describe wave velocity in terms of its **phase velocity**—in other words, how **fast** does a specific value of absolute phase  $\phi$  seem to **propagate** down the transmission line.

Since velocity is change in distance with respect to **time**, we need to first express our propagating wave in its real form:

$$\begin{aligned} v^+(z, t) &= \text{Re} \{ V^+(z) e^{-j\omega t} \} \\ &= |V_0^+| \cos(\omega t - \beta z + \phi_0^+) \end{aligned}$$

Thus, the absolute phase is a function of **both** time and frequency:

$$\phi^+(z, t) = \omega t - \beta z + \phi_0^+$$

Now let's set this phase to some **arbitrary** value of  $\phi_c$  radians.

$$\omega t - \beta z + \phi_0^+ = \phi_c$$

For **every** time  $t$ , there is **some** location  $z$  on a transmission line that has this phase value  $\phi_c$ . That location is evidently:

$$z = \frac{\omega t + \phi_0^+ - \phi_c}{\beta}$$

Note as **time increases**, so too does the **location**  $z$  on the line where  $\phi^+(z, t) = \phi_c$ .

The **velocity**  $v_p$  at which this phase point moves down the line can be determined as:

$$v_p = \frac{dz}{dt} = \frac{d\left(\frac{\omega t + \phi_0^+ - \phi_c}{\beta}\right)}{dt} = \frac{\omega}{\beta}$$

This wave velocity is the **velocity of the propagating wave!**

Note that the value:

$$\frac{v_p}{\lambda} = \frac{\omega}{\beta} \frac{\beta}{2\pi} = \frac{\omega}{2\pi} = f$$

and thus we can conclude that:

$$v_p = f\lambda$$

as well as:

$$\beta = \frac{\omega}{v_p}$$

**Q:** *But these results were derived for the  $V^+(z)$  wave; what about the **other** wave ( $V^-(z)$ )?*

**A:** The results are essentially the **same**, as each wave depends on the same value  $\beta$ .

The only **subtle difference** comes when we evaluate the phase velocity. For the wave  $V^-(z)$ , we find:

$$\phi^-(z, t) = \omega t + \beta z + \phi_0^-$$

Note the **plus sign** associated with  $\beta z$ !

We thus find that some arbitrary phase value will be located at location:

$$z = \frac{-\phi_0^- + \phi_c - \omega t}{\beta}$$

Note now that an **increasing time** will result in a **decreasing** value of **position**  $z$ . In other words this wave is propagating in the direction of decreasing position  $z$ —in the **opposite** direction of the  $V^+(z)$  wave!

This is **further** verified by the derivative:


$$v_p = \frac{dz}{dt} = \frac{d\left(\frac{-\phi_0^- + \phi_c - \omega t}{\beta}\right)}{dt} = -\frac{\omega}{\beta}$$

Where the **minus sign** merely means that the wave propagates in the  $-z$  direction. Otherwise, the **wavelength** and **velocity** of the two waves are **precisely** the same!

# Line Impedance

Now let's define **line impedance**  $Z(z)$ , a **complex** function which is simply the ratio of the complex line **voltage** and complex line **current**:

$$Z(z) = \frac{V(z)}{I(z)}$$

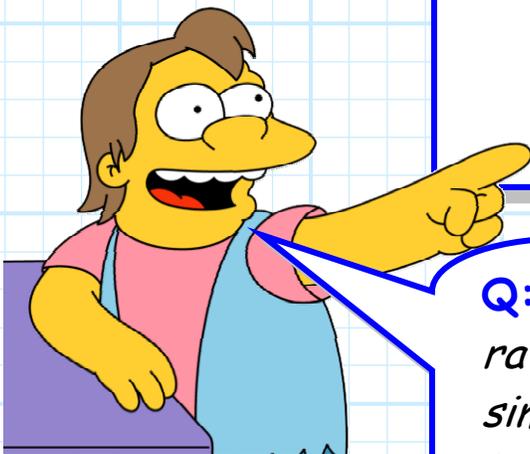

**Q:** *Hey! I know what this is! The ratio of the voltage to current is simply the **characteristic impedance**  $Z_0$ , right ???*

**A:** **NO!** The line impedance  $Z(z)$  is (generally speaking) **NOT** the transmission line **characteristic impedance**  $Z_0$ !!!

→ It is **unfathomably important** that you understand this!!!!

To see why, recall that:

$$V(z) = V^+(z) + V^-(z)$$

And that:

$$I(z) = \frac{V^+(z) - V^-(z)}{Z_0}$$

Therefore:


$$Z(z) = \frac{V(z)}{I(z)} = Z_0 \left( \frac{V^+(z) + V^-(z)}{V^+(z) - V^-(z)} \right) \neq Z_0$$

Or, more specifically, we can write:

$$Z(z) = Z_0 \left( \frac{V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}}{V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z}} \right)$$

**Q:** *I'm confused! Isn't:*

$$V^+(z)/I^+(z) = Z_0 ???$$

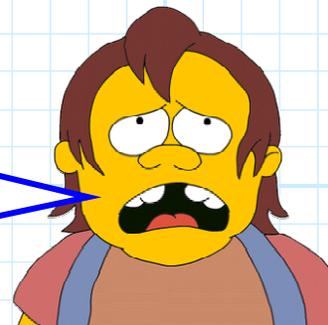

**A:** Yes! That is true! The ratio of the voltage to current for **each** of the two propagating waves is  $\pm Z_0$ . However, the ratio of the **sum** of the two voltages to the **sum** of the two currents is **not** equal to  $Z_0$  (generally speaking)!

This is actually confirmed by the equation above. Say that  $V^-(z) = 0$ , so that only **one** wave ( $V^+(z)$ ) is propagating on the line.

In this case, the ratio of the **total** voltage to the total current is simply the ratio of the voltage and current of the **one** remaining wave—the **characteristic impedance**  $Z_0$ !

$$Z(z) = \frac{V(z)}{I(z)} = Z_0 \left( \frac{V^+(z)}{I^+(z)} \right) = \frac{V^+(z)}{I^+(z)} = Z_0 \quad (\text{when } V^-(z) = 0)$$

**Q:** *So, it appears to me that characteristic impedance  $Z_0$  is a **transmission line parameter**, depending **only** on the transmission line values  $L$  and  $C$ .*

*Whereas **line impedance** is  $Z(z)$  depends the magnitude and phase of the two propagating waves  $V^+(z)$  and  $V^-(z)$  --values that depend **not only** on the transmission line, but also on the two things **attached** to either **end** of the transmission line!*

*Right !?*



**A:** **Exactly!** Moreover, note that characteristic impedance  $Z_0$  is simply a **number**, whereas line impedance  $Z(z)$  is a **function** of position ( $z$ ) on the transmission line.

# The Reflection Coefficient

So, we know that the transmission line **voltage**  $V(z)$  and the transmission line **current**  $I(z)$  can be related by the **line impedance**  $Z(z)$ :

$$V(z) = Z(z) I(z)$$

or equivalently:

$$I(z) = \frac{V(z)}{Z(z)}$$

**Q:** *Piece of cake! I fully understand the concepts of voltage, current and impedance from my circuits classes. Let's move on to something more important (or, at the very least, more interesting).*



Expressing the "activity" on a transmission line in terms of **voltage, current and impedance** is of course **perfectly valid**.


However, let us look **closer** at the expression for each of these quantities:

$$V(z) = V^+(z) + V^-(z)$$

$$I(z) = \frac{V^+(z) - V^-(z)}{Z_0}$$

$$Z(z) = Z_0 \left( \frac{V^+(z) + V^-(z)}{V^+(z) - V^-(z)} \right)$$

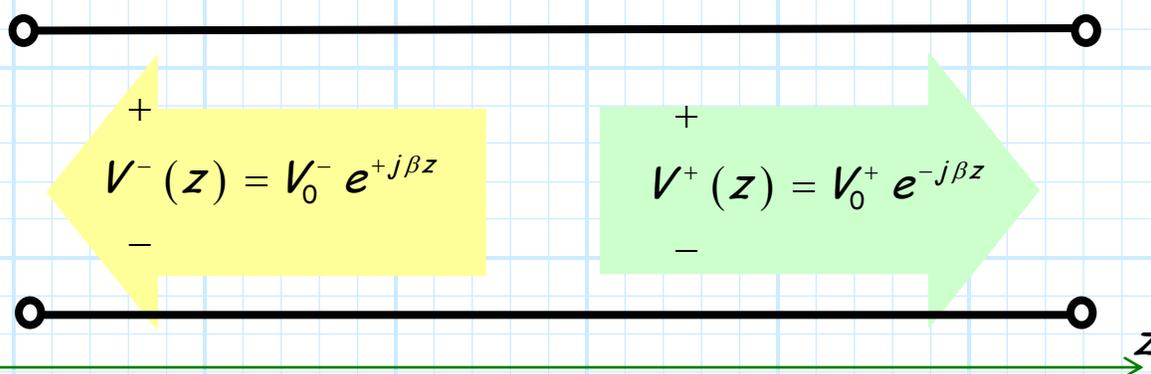It is evident that we can **alternatively** express all "activity" on the transmission line in terms of the two transmission line waves  $V^+(z)$  and  $V^-(z)$ .



**Q:** I know  $V(z)$  and  $I(z)$  are related by line impedance  $Z(z)$ :

$$Z(z) = \frac{V(z)}{I(z)}$$

But how are  $V^+(z)$  and  $V^-(z)$  related?

**A:** Similar to line impedance, we can define a new parameter—the **reflection coefficient**  $\Gamma(z)$ —as the **ratio** of the two quantities:

$$\Gamma(z) \doteq \frac{V^-(z)}{V^+(z)} \Rightarrow V^-(z) = \Gamma(z)V^+(z)$$

More specifically, we can express  $\Gamma(z)$  as:

$$\Gamma(z) = \frac{V_0^- e^{+j\beta z}}{V_0^+ e^{-j\beta z}} = \frac{V_0^-}{V_0^+} e^{+j2\beta z}$$

Note then, the value of the reflection coefficient at  $z=0$  is:

$$\Gamma(z=0) = \frac{V^-(z=0)}{V^+(z=0)} e^{+j2\beta(0)} = \frac{V_0^-}{V_0^+}$$

We define this value as  $\Gamma_0$ , where:

$$\Gamma_0 \doteq \Gamma(z=0) = \frac{V_0^-}{V_0^+}$$

Note then that we can alternatively write  $\Gamma(z)$  as:

$$\Gamma(z) = \Gamma_0 e^{+j2\beta z}$$

So now we have **two different** but equivalent ways to describe transmission line activity!

We can use (total) **voltage** and **current**, related by **line impedance**:

$$Z(z) = \frac{V(z)}{I(z)} \quad \therefore \quad V(z) = Z(z) I(z)$$

Or, we can use the two propagating **voltage waves**, related by the **reflection coefficient**:

$$\Gamma(z) = \frac{V^-(z)}{V^+(z)} \quad \therefore \quad V^-(z) = \Gamma(z) V^+(z)$$

These are **equivalent** relationships—we can use **either** when describing a transmission line.



*Based on your **circuits** experience, you might well be **tempted** to always use the **first** relationship. However, we will find it useful (as well as simple) indeed to describe activity on a transmission line in terms of the **second** relationship—in terms of the **two** propagating transmission line **waves**!*