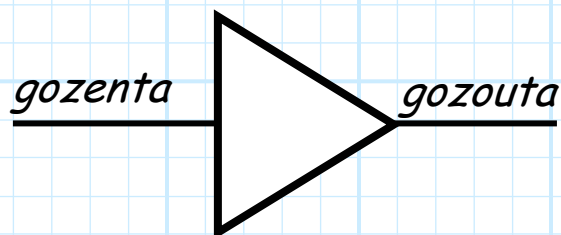


E. Microwave Network Theory

Note that a passive load is a one-port device—a device that can be characterized (at one frequency) by impedance Z_L or load reflection coefficient Γ_L .

However, many microwave devices have **multiple** ports!

Most common are **two-port devices** (e.g., amplifiers and filters), devices with both a gozenta and a gozouta.



Note that a transmission line is also two-port device!

Q: *Are there any known ways to characterize a **multi-port** device?*

A: Yes! **Two** methods are:

1. The **impedance** matrix—a multi-port equivalent of Z_L
2. The **scattering** matrix—a multi-port equivalent of Γ_L

HO: The Impedance Matrix

Q: You say that the impedance matrix characterizes a **multi-port** device. But is this characterization **helpful**? Can we actually use it to **solve** real problems?

A: Example: Using the Impedance Matrix

Q: The **impedance** matrix relates the quantities $I(z)$ and $V(z)$, is there an **equivalent** matrix that relates $V^+(z)$ and $V^-(z)$?

A: Yes! The **scattering** matrix relates the t.l. **waves** entering and exiting a multi-port device!

HO: The Scattering Matrix

Q: Can the scattering matrix likewise be used to solve real problems?

A: Of course!

Example: The Scattering Matrix

Example: Scattering Parameters


Q: But, can the scattering matrix by itself tell us anything about the device it characterizes?

A: Yes! It can tell us if the device is **matched**, or **lossless**, or **reciprocal**.

HO: Matched, Lossless, Reciprocal

The Impedance Matrix

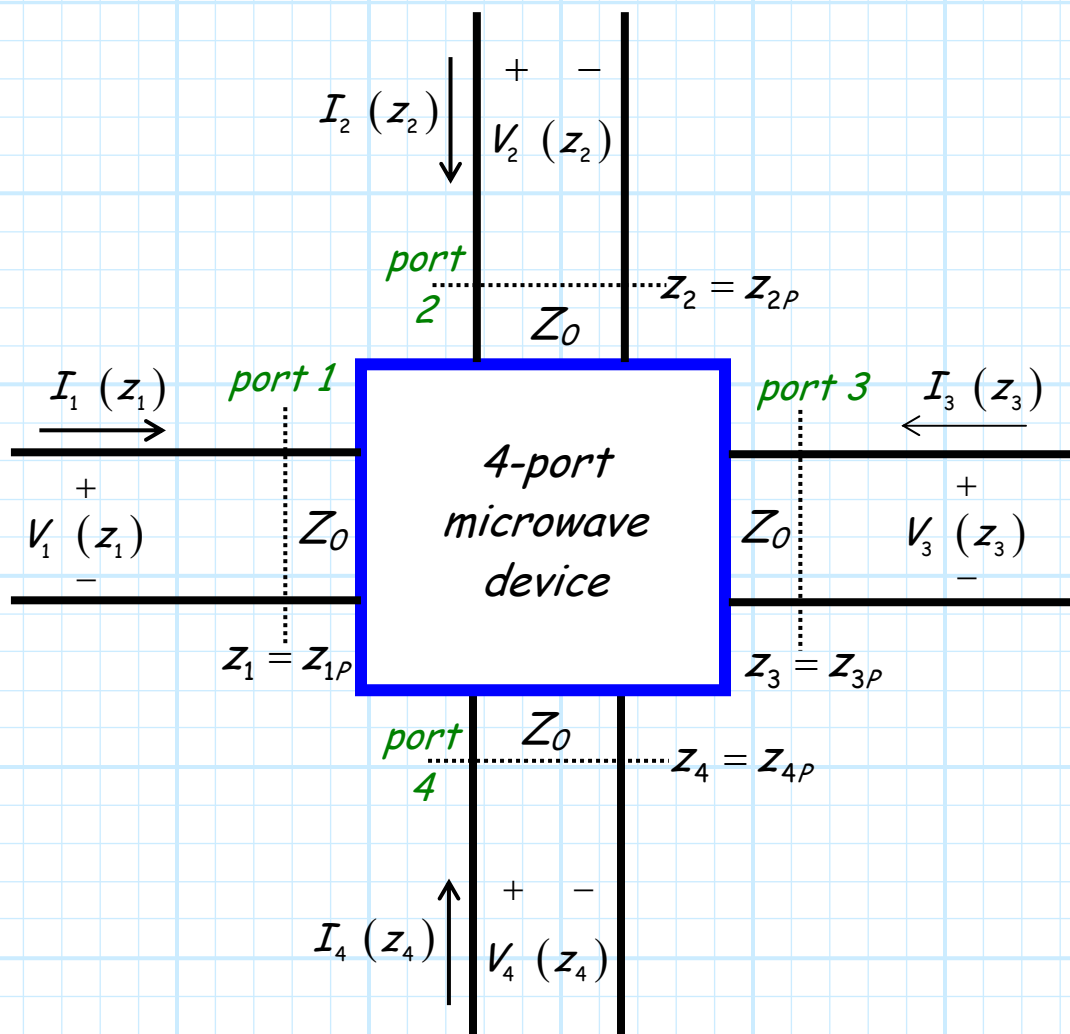Consider the **4-port** microwave device shown below:



Note in this example, there are four **identical** transmission lines connected to the same "box". Inside this box there may be a very **simple** linear device/circuit, or it might contain a very large and **complex** linear microwave system.

→ Either way, the "box" can be fully characterized by its **impedance matrix!**

First, note that each transmission line has a specific **location** that effectively defines the **input** to the device (i.e., z_{1P} , z_{2P} , z_{3P} , z_{4P}). These often arbitrary positions are known as the **port locations**, or **port planes** of the device.

Thus, the **voltage** and **current** at port n is:

$$V_n(z_n = z_{nP}) \quad I_n(z_n = z_{nP})$$

We can **simplify** this cumbersome notation by simply **defining** port n current and voltage as I_n and V_n :

$$V_n = V_n(z_n = z_{nP}) \quad I_n = I_n(z_n = z_{nP})$$

For **example**, the current at port **3** would be $I_3 = I_3(z_3 = z_{3P})$.

Now, say there exists a non-zero current at **port 1** (i.e., $I_1 \neq 0$), while the current at all **other** ports are known to be **zero** (i.e., $I_2 = I_3 = I_4 = 0$).

Say we measure/determine the **current** at port **1** (i.e., determine I_1), and we then measure/determine the **voltage** at the port **2** plane (i.e., determine V_2).

The complex ratio between V_2 and I_1 is known as the **trans-impedance parameter** Z_{21} :

$$Z_{21} = \frac{V_2}{I_1}$$

Likewise, the trans-impedance parameters Z_{31} and Z_{41} are:

$$Z_{31} = \frac{V_3}{I_1} \quad \text{and} \quad Z_{41} = \frac{V_4}{I_1}$$

We of course could **also** define, say, trans-impedance parameter Z_{34} as the ratio between the complex values I_4 (the current into port 4) and V_3 (the voltage at port 3), given that the current at all other ports (1, 2, and 3) are zero.


Thus, more **generally**, the ratio of the current into port n and the voltage at port m is:

$$Z_{mn} = \frac{V_m}{I_n} \quad (\text{given that } I_k = 0 \text{ for all } k \neq n)$$

Q: But how do we ensure that all but *one* port current is zero?



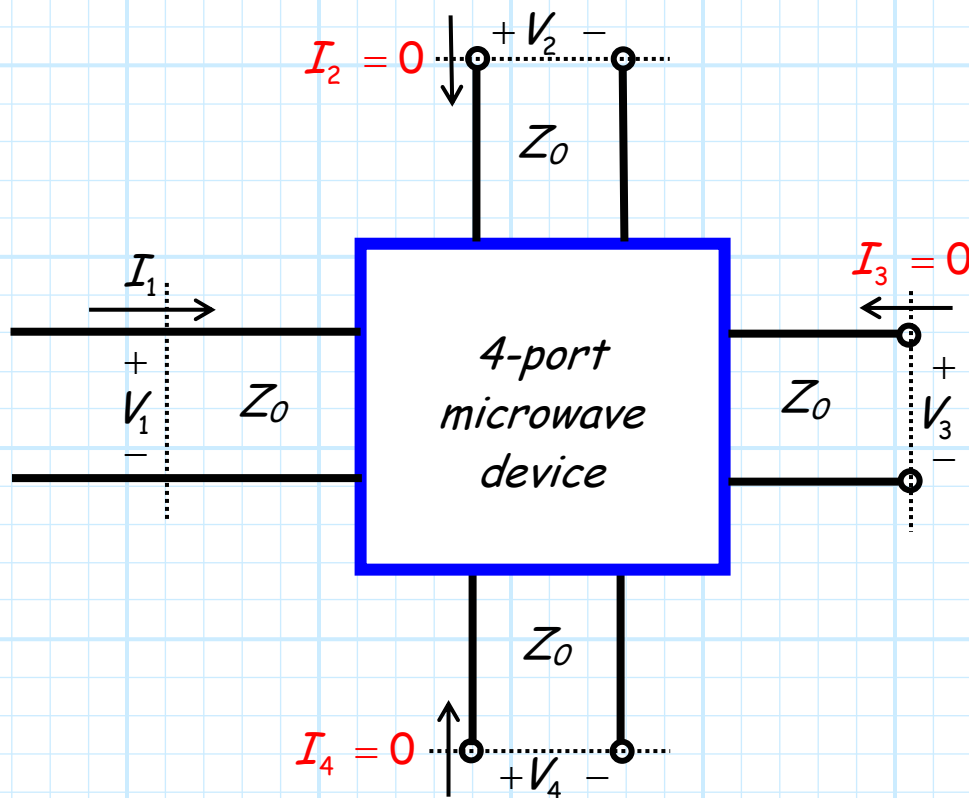
A: Place an **open circuit** at those ports!



Placing an **open** at a port (and it must be **at the port!**) enforces the condition that $I = 0$.

Now, we can thus **equivalently** state the definition of trans-impedance as:
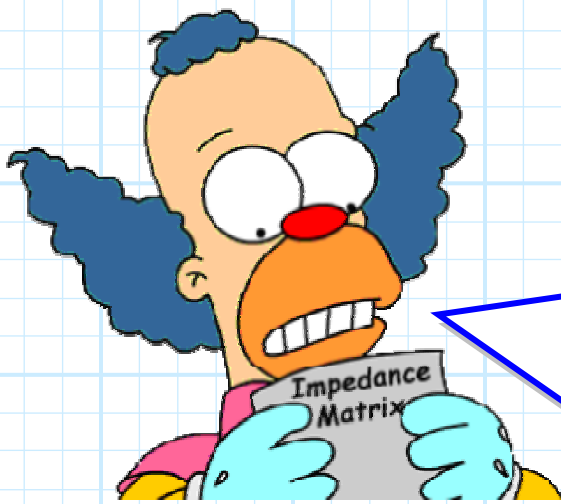
$$Z_{mn} = \frac{V_m}{I_n} \quad (\text{given that all ports } k \neq n \text{ are open})$$



Q: *As impossible as it sounds, this handout is even more **boring** and **pointless** than any of your previous efforts. **Why** are we studying this? After all, what is the likelihood that a device will have an **open** circuit on **all** but one of its ports?!*

A: OK, say that **none** of our ports are **open-circuited**, such that we have currents **simultaneously** on **each** of the **four** ports of our device.

Since the device is **linear**, the voltage at any **one** port due to **all** the port currents is simply the coherent **sum** of the voltage at that port due to **each** of the currents!

For example, the voltage at port 3 can be determined by:

$$V_3 = Z_{34} I_4 + Z_{33} I_3 + Z_{32} I_2 + Z_{31} I_1$$

More generally, the voltage at port m of an N -port device is:

$$V_m = \sum_{n=1}^N Z_{mn} I_n$$

This expression can be written in **matrix** form as:

$$\mathbf{V} = \mathbf{Z} \mathbf{I}$$

Where \mathbf{I} is the **vector**:

$$\mathbf{I} = [I_1, I_2, I_3, \dots, I_N]^T$$

and \mathbf{V} is the vector:

$$\mathbf{V} = [V_1, V_2, V_3, \dots, V_N]^T$$

And the matrix \mathbf{Z} is called the **impedance matrix**:

$$\mathbf{Z} = \begin{bmatrix} Z_{11} & \dots & Z_{1n} \\ \vdots & \ddots & \vdots \\ Z_{m1} & \dots & Z_{mn} \end{bmatrix}$$

The impedance matrix is a N by N matrix that **completely characterizes** a linear, N -port device. Effectively, the impedance matrix describes a multi-port device the way that Z_L describes a single-port device (e.g., a load)!




But **beware!** The values of the impedance matrix for a particular device or network, just like Z_L , are **frequency dependent!** Thus, it may be more instructive to **explicitly** write:

$$\mathbf{Z}(\omega) = \begin{bmatrix} Z_{11}(\omega) & \cdots & Z_{1n}(\omega) \\ \vdots & \ddots & \vdots \\ Z_{m1}(\omega) & \cdots & Z_{mn}(\omega) \end{bmatrix}$$

Example: Using the Impedance Matrix

Consider the following circuit:

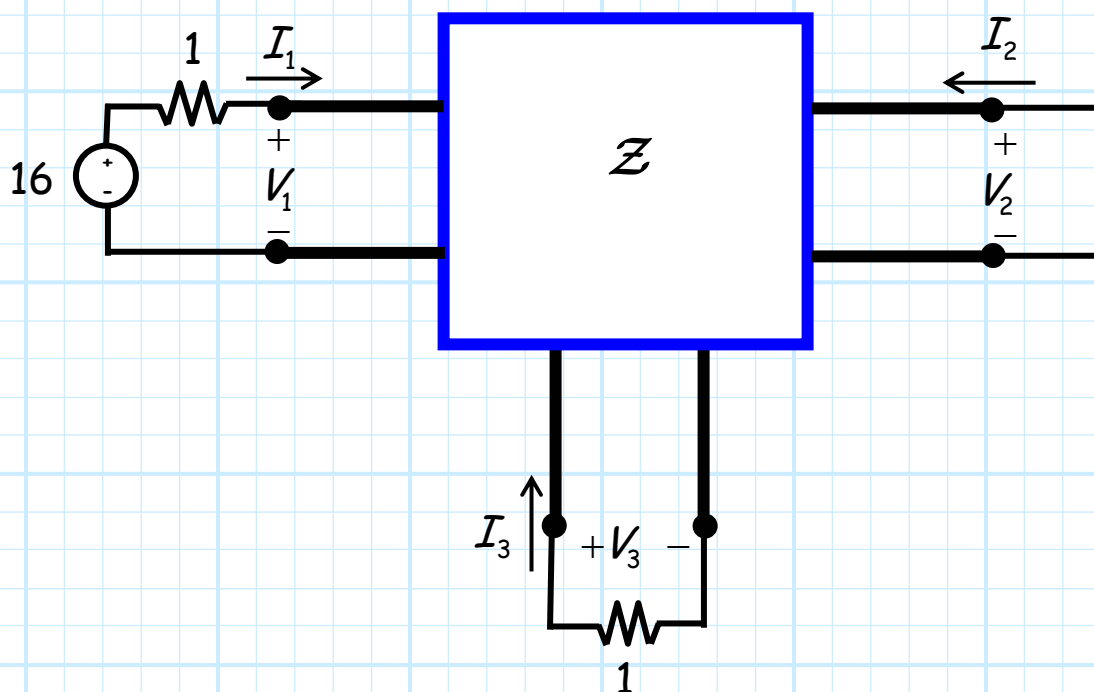

Where the 3-port **device** is characterized by the **impedance matrix**:

$$\mathbf{Z} = \begin{bmatrix} 2 & 1 & 2 \\ 1 & 1 & 4 \\ 2 & 4 & 1 \end{bmatrix}$$

Let's now determine all port **voltages** V_1, V_2, V_3 and all **currents** I_1, I_2, I_3 .



Q: *How can we do that—we **don't** know what the device is made of! What's inside that box?*

A: We **don't** need to know what's inside that box! We know its impedance matrix, and that **completely** characterizes the device (or, at least, characterizes it at **one** frequency).

Thus, we have enough information to solve this problem. From the impedance matrix we know:

$$V_1 = 2 I_1 + I_2 + 2 I_3$$

$$V_2 = I_1 + I_2 + 4 I_3$$

$$V_3 = 2 I_1 + 4 I_2 + I_3$$



Q: *Wait! There are only **3** equations here, yet there are **6** unknowns!?*

A: True! The impedance matrix describes the device in the box, but it does **not** describe the devices **attached** to it. We require **more** equations to describe them.

1. The **source** at port 1 is described by the equation:

$$V_1 = 16.0 - (1)I_1$$

2. The **short** circuit on port 2 means that:

$$V_2 = 0$$

3. While the **load** on port 3 leads to:

$$V_3 = -(1)I_3 \quad (\text{note the minus sign!})$$

Now we have **6** equations and **6** unknowns! Combining equations, we find:

$$V_1 = 16 - I_1 = 2I_1 + I_2 + 2I_3$$

$$\therefore 16 = 3I_1 + I_2 + 2I_3$$

$$V_2 = 0 = I_1 + I_2 + 4I_3$$

$$\therefore 0 = I_1 + I_2 + 4I_3$$

$$V_3 = -I_3 = 2I_1 + 4I_2 + I_3$$

$$\therefore 0 = 2I_1 + 4I_2 + 2I_3$$

Solving, we find (I'll let you do the algebraic details!):

$$I_1 = 7.0$$

$$I_2 = -3.0$$

$$I_3 = -1.0$$

$$V_1 = 9.0$$

$$V_2 = 0.0$$

$$V_3 = 1.0$$

The Scattering Matrix

At “**low**” frequencies, we can completely characterize a **linear** device or network using an **impedance** matrix, which relates the currents and voltages at **each** device terminal to the currents and voltages at **all** other terminals.


But, at microwave frequencies, it is **difficult** to measure total currents and voltages!



- * Instead, we can measure the **magnitude** and **phase** of each of the two transmission line **waves** $V^+(z)$ and $V^-(z)$.
- * In other words, we can determine the relationship between the incident and reflected wave at **each** device terminal to the incident and reflected waves at **all** other terminals.

These relationships are completely represented by the **scattering matrix**. It **completely** describes the behavior of a linear, multi-port device at a **given frequency** ω , and a given line impedance Z_0 .

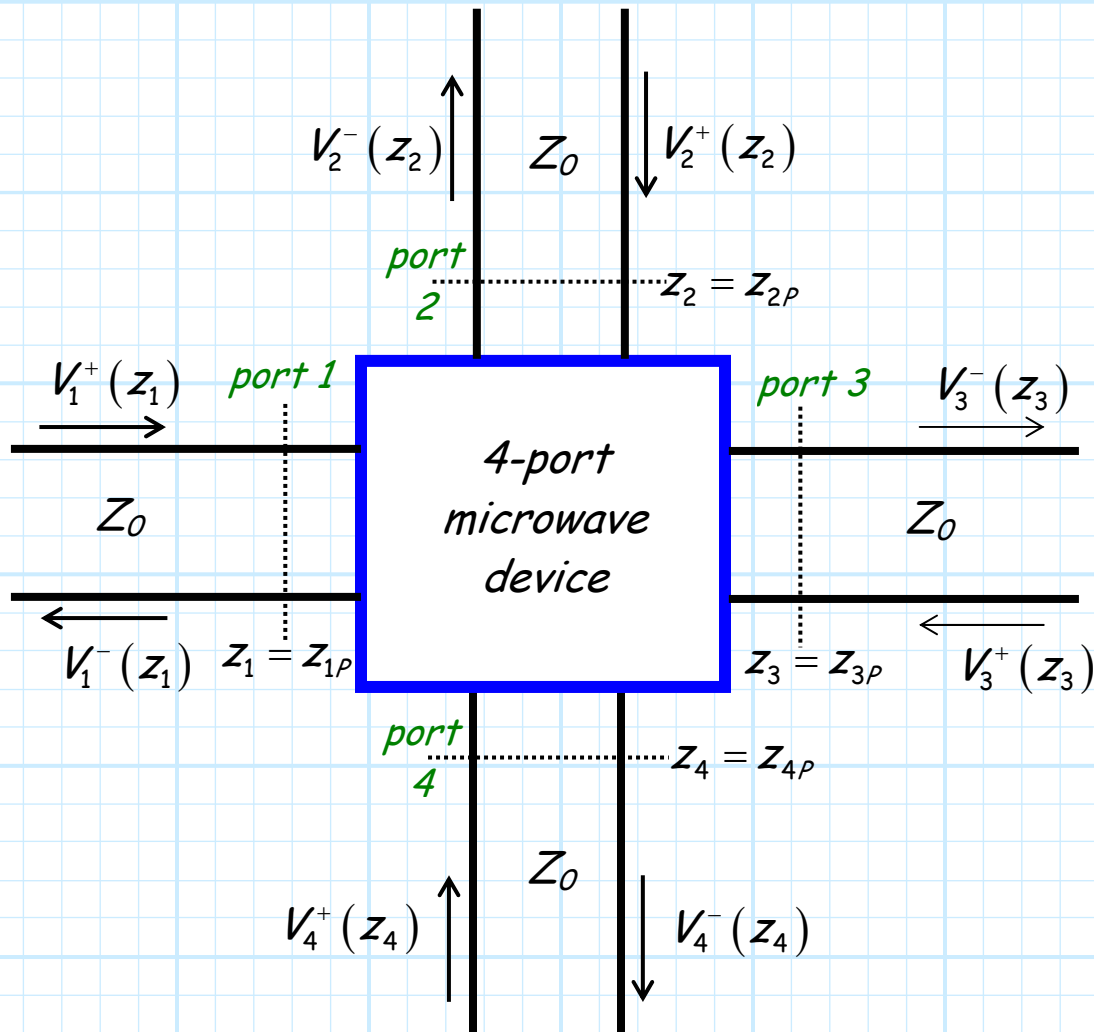
Consider now the **4-port** microwave device shown below:



Note that we have now characterized transmission line activity in terms of incident and "reflected" waves. Note the negative going "reflected" waves can be viewed as the waves **exiting** the multi-port network or device.


→ Viewing transmission line activity this way, we can fully characterize a multi-port device by its **scattering parameters!**

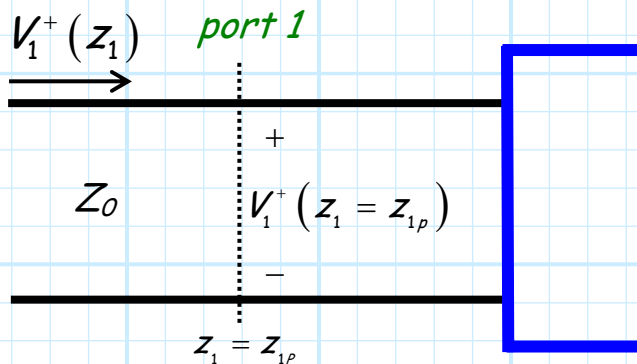Say there exists an **incident wave on port 1** (i.e., $V_1^+(z_1) \neq 0$), while the incident waves on all other ports are known to be **zero** (i.e., $V_2^+(z_2) = V_3^+(z_3) = V_4^+(z_4) = 0$).



Say we measure/determine the voltage of the wave flowing **into port 1**, at the port 1 **plane** (i.e., determine $V_1^+(z_1 = z_{1\rho})$).

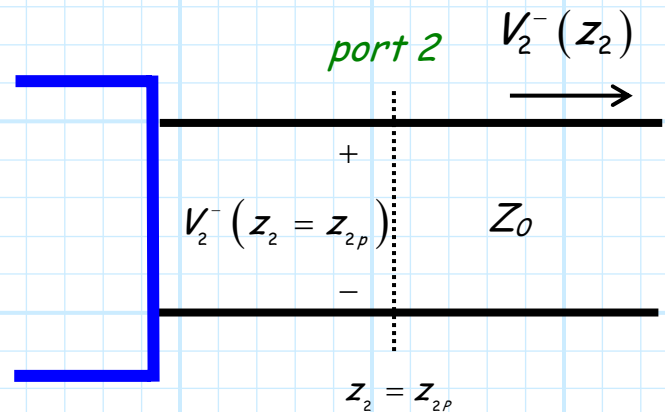Say we then measure/determine the voltage of the wave flowing **out of port 2**, at the port 2 plane (i.e., determine $V_2^-(z_2 = z_{2\rho})$).



The complex ratio between $V_1^+(z_1 = z_{1\rho})$ and $V_2^-(z_2 = z_{2\rho})$ is known as the **scattering parameter** S_{21} :

$$S_{21} = \frac{V_2^-(z_2 = z_{2\rho})}{V_1^+(z_1 = z_{1\rho})} = \frac{V_{02}^- e^{+j\beta z_{2\rho}}}{V_{01}^+ e^{-j\beta z_{1\rho}}} = \frac{V_{02}^-}{V_{01}^+} e^{+j\beta(z_{2\rho} + z_{1\rho})}$$

Likewise, the scattering parameters S_{31} and S_{41} are:

$$S_{31} = \frac{V_3^-(z_3 = z_{3\rho})}{V_1^+(z_1 = z_{1\rho})} \quad \text{and} \quad S_{41} = \frac{V_4^-(z_4 = z_{4\rho})}{V_1^+(z_1 = z_{1\rho})}$$

We of course could **also** define, say, scattering parameter S_{34} as the ratio between the complex values $V_4^+(z_4 = z_{4p})$ (the wave **into** port 4) and $V_3^-(z_3 = z_{3p})$ (the wave **out of** port 3), given that the input to all other ports (1,2, and 3) are zero.


Thus, more **generally**, the ratio of the wave incident on port n to the wave emerging from port m is:

$$S_{mn} = \frac{V_m^-(z_m = z_{mp})}{V_n^+(z_n = z_{np})} \quad (\text{given that } V_k^+(z_k) = 0 \text{ for all } k \neq n)$$

Note that frequently the port positions are assigned a **zero** value (e.g., $z_{1p} = 0, z_{2p} = 0$). This of course **simplifies** the scattering parameter calculation:

$$S_{mn} = \frac{V_m^-(z_m = 0)}{V_n^+(z_n = 0)} = \frac{V_{0m}^- e^{+j\beta 0}}{V_{0n}^+ e^{-j\beta 0}} = \frac{V_{0m}^-}{V_{0n}^+}$$

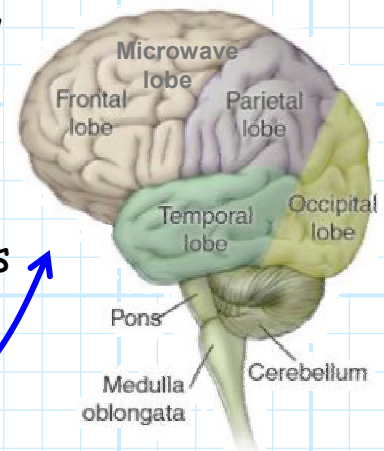
We will **generally assume** that the port locations are defined as $z_{np} = 0$, and thus use the **above** notation. But **remember** where this expression came from!






Q: *But how do we ensure that only one incident wave is non-zero?*

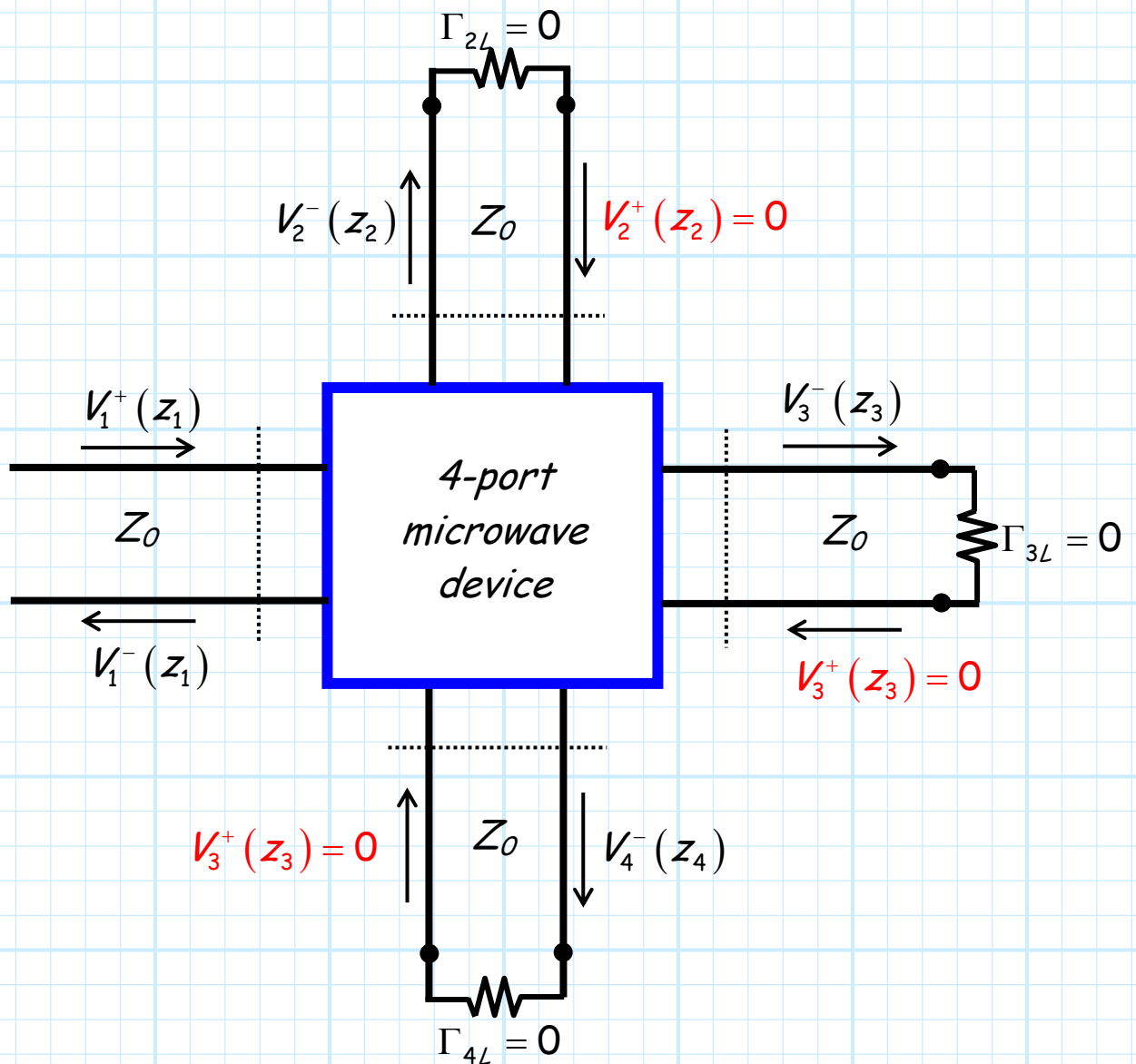A: **Terminate all other ports with a matched load!**



Note that if the ports are terminated in a **matched load** (i.e., $Z_L = Z_0$), then $\Gamma_{nL} = 0$ and therefore:

$$V_n^+(z_n) = 0$$

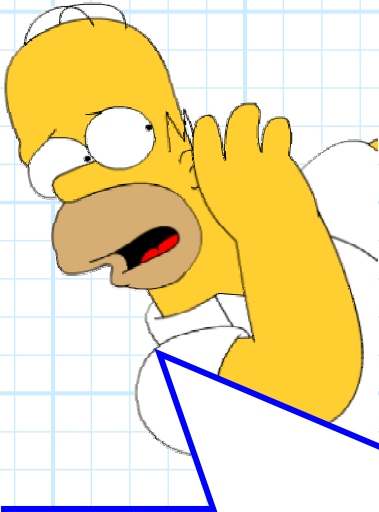

In other words, terminating a port ensures that there will be **no signal** incident on that port!

Q: *Just between you and me, I think you've messed this up! In all previous handouts you said that if $\Gamma_L = 0$, the wave in the **minus** direction would be zero:*

$$V^-(z) = 0 \quad \text{if} \quad \Gamma_L = 0$$


*but just **now** you said that the wave in the **positive** direction would be zero:*

$$V^+(z) = 0 \quad \text{if} \quad \Gamma_L = 0$$

*Of course, there is **no way** that **both** statements can be correct!*


A: Actually, **both** statements are correct! You must be careful to understand the **physical definitions** of the plus and minus directions—in other words, the propagation directions of waves $V_n^+(z_n)$ and $V_n^-(z_n)$!

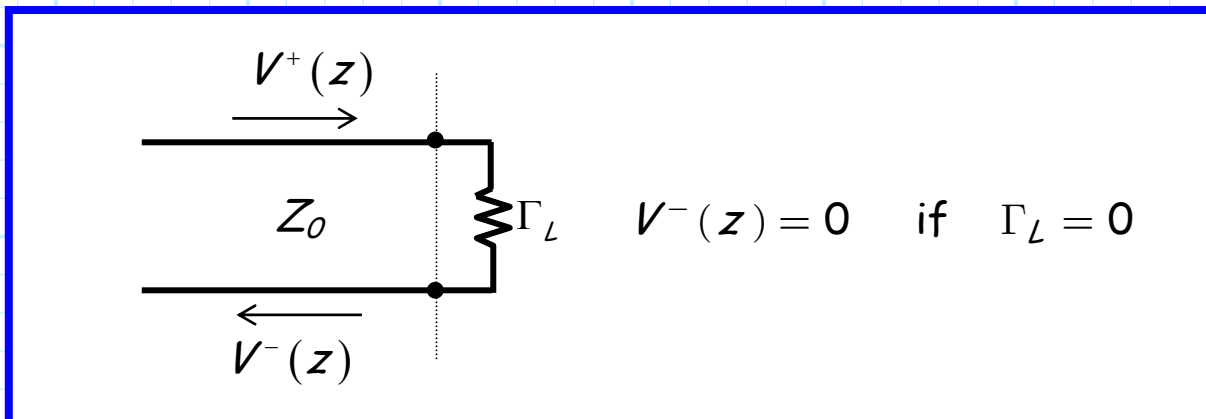For example, we **originally** analyzed this case:



In this original case, the wave **incident** on the load is $V^+(z)$ (**plus** direction), while the **reflected** wave is $V^-(z)$ (**minus** direction).

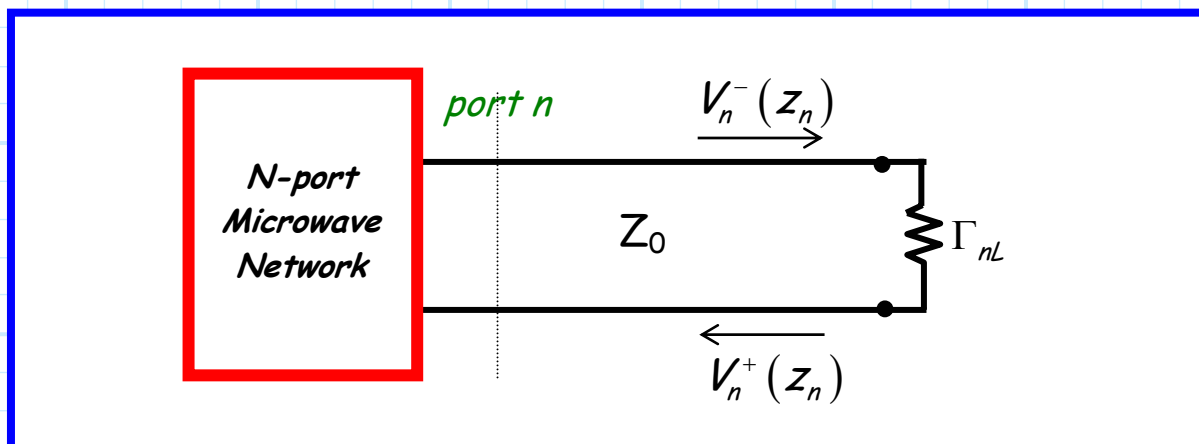Contrast this with the case we are **now** considering:




For this current case, the situation is **reversed**. The wave incident on the load is **now** denoted as $V_n^-(z_n)$ (coming **out** of port n), while the wave reflected off the load is **now** denoted as $V_n^+(z_n)$ (going **into** port n).

As a result, $V_n^+(z_n) = 0$ when $\Gamma_{nL} = 0$!

Perhaps we could more **generally** state that for some load Γ_L :
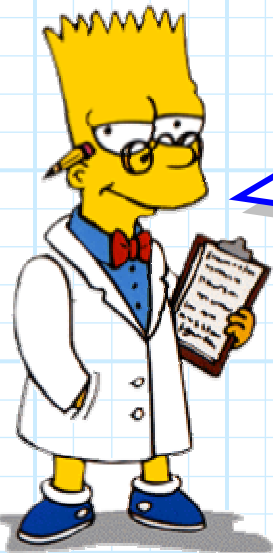
$$V^{\text{reflected}}(z = z_L) = \Gamma_L V^{\text{incident}}(z = z_L)$$



*For each case, you must be able to correctly identify the mathematical statement describing the wave **incident** on, and **reflected** from, some passive load.*

*Like most equations in engineering, the **variable names** can change, but the **physics** described by the mathematics will **not**!*

Now, **back** to our discussion of **S-parameters**. We found that if $z_{np} = 0$ for all ports n , the scattering parameters could be directly written in terms of wave **amplitudes** V_{0n}^+ and V_{0m}^- .

$$S_{mn} = \frac{V_{0m}^-}{V_{0n}^+} \quad (\text{when } V_k^+(z_k) = 0 \text{ for all } k \neq n)$$

Which we can now **equivalently** state as:

$$S_{mn} = \frac{V_{0m}^-}{V_{0n}^+} \quad (\text{when all ports, except port } n, \text{ are terminated in **matched loads**)}$$

We can use the scattering matrix to determine the solution for a more **general** circuit—one where the ports are **not** terminated in matched loads!



Q: *I'm not understanding the importance scattering parameters. How are they useful to us microwave engineers?*

A: Since the device is **linear**, we can apply **superposition**. The output at any port due to **all** the incident waves is simply the coherent **sum** of the output at that port due to **each** wave!

For example, the **output** wave at port 3 can be determined by (assuming $z_{nP} = 0$):

$$V_{03}^- = S_{34} V_{04}^+ + S_{33} V_{03}^+ + S_{32} V_{02}^+ + S_{31} V_{01}^+$$

More **generally**, the output at port m of an N -port device is:

$$V_{0m}^- = \sum_{n=1}^N S_{mn} V_{0n}^+ \quad (z_{nP} = 0)$$

This expression can be written in **matrix** form as:

$$\mathbf{V}^- = \mathbf{S} \mathbf{V}^+$$

Where \mathbf{V}^- is the vector:

$$\mathbf{V}^- = [V_{01}^-, V_{02}^-, V_{03}^-, \dots, V_{0N}^-]^T$$

and \mathbf{V}^+ is the vector:

$$\mathbf{V}^+ = [V_{01}^+, V_{02}^+, V_{03}^+, \dots, V_{0N}^+]^T$$

Therefore \mathcal{S} is the **scattering matrix**:

$$\mathcal{S} = \begin{bmatrix} S_{11} & \dots & S_{1n} \\ \vdots & \ddots & \vdots \\ S_{m1} & \dots & S_{mn} \end{bmatrix}$$

The scattering matrix is a N by N matrix that **completely characterizes** a linear, N -port device. Effectively, the scattering matrix describes a multi-port device the way that Γ_L describes a single-port device (e.g., a load)!



But **beware!** The values of the scattering matrix for a particular device or network, just like Γ_L , are **frequency dependent!** Thus, it may be more instructive to **explicitly** write:

$$\mathcal{S}(\omega) = \begin{bmatrix} \mathcal{S}_{11}(\omega) & \cdots & \mathcal{S}_{1n}(\omega) \\ \vdots & \ddots & \vdots \\ \mathcal{S}_{m1}(\omega) & \cdots & \mathcal{S}_{mn}(\omega) \end{bmatrix}$$

Also realize that—also just like Γ_L —the scattering matrix is dependent on **both the device/network** and the Z_0 value of the **transmission lines connected** to it.


Thus, a device connected to transmission lines with $Z_0 = 50\Omega$ will have a **completely different scattering matrix** than that same device connected to transmission lines with $Z_0 = 100\Omega$!!!

Example: The Scattering Matrix

Say we have a 3-port network that is completely characterized at some frequency ω by the **scattering matrix**:

$$\mathcal{S} = \begin{bmatrix} 0.0 & 0.2 & 0.5 \\ 0.5 & 0.0 & 0.2 \\ 0.5 & 0.5 & 0.0 \end{bmatrix}$$

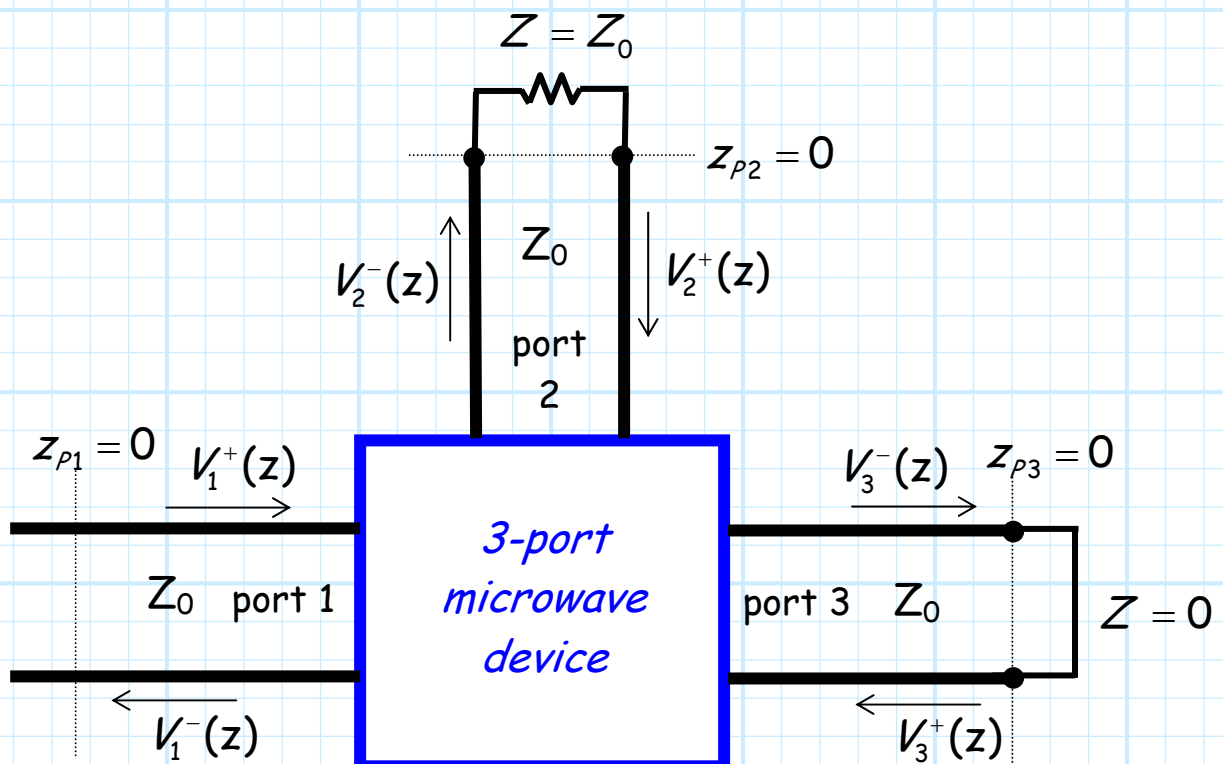A **matched load** is attached to port 2, while a **short circuit** has been placed at port 3:



a) Find the **reflection** coefficient at port 1, i.e.:

$$\Gamma_1 \doteq \frac{V_{01}^-}{V_{01}^+}$$

b) Find the **transmission** coefficient from port 1 to port 2, i.e.,

$$T_{21} \doteq \frac{V_{02}^-}{V_{01}^+}$$

*I am amused by the trivial problems that **you** apparently find so difficult. **I** know that:*

$$\Gamma_1 = \frac{V_{01}^-}{V_{01}^+} = S_{11} = 0.0$$

and

$$T_{21} = \frac{V_{02}^-}{V_{01}^+} = S_{21} = 0.5$$



NO!!! The above statement is **not correct!**



Remember, $V_{01}^-/V_{01}^+ = S_{11}$ **only** if ports 2 and 3 are terminated in **matched** loads! In this problem port 3 is terminated with a **short circuit**.

Therefore:

$$\Gamma_1 = \frac{V_{01}^-}{V_{01}^+} \neq S_{11}$$

and similarly:

$$T_{21} = \frac{V_{02}^-}{V_{01}^+} \neq S_{21}$$

To determine the values T_{21} and Γ_1 , we must start with the **three** equations provided by the **scattering matrix**:

$$V_{01}^- = 0.2 V_{02}^+ + 0.5 V_{03}^+$$

$$V_{02}^- = 0.5 V_{01}^+ + 0.2 V_{03}^+$$

$$V_{03}^- = 0.5 V_{01}^+ + 0.5 V_{02}^+$$

and the **two** equations provided by the **attached loads**:

$$\Gamma_{L2} = 0 \Rightarrow V_{02}^+ = 0$$

$$\Gamma_{L3} = -1 \Rightarrow V_{03}^+ = -V_{03}^-$$



You've made a terrible mistake! Fortunately, I was here to correct it for you—since $\Gamma_L = 0$, the constant V_{02}^- (not V_{02}^+) is equal to zero.

NO!! Remember, the signal $V_2^-(z)$ is **incident** on the matched load, and $V_2^+(z)$ is the **reflected** wave from the load (i.e., $V_2^+(z)$ is incident on **port 2**). Therefore, $V_{02}^+ = 0$ is **correct!**

Likewise, because of the **short** circuit at port 3 ($\Gamma_L = -1$):

$$\frac{V_3^+(z_3 = 0)}{V_3^-(z_3 = 0)} = \frac{V_{03}^+}{V_{03}^-} = -1$$

and therefore:

$$V_{03}^+ = -V_{03}^-$$

We can divide all of these equations by V_{01}^+ , resulting in:

$$\Gamma_1 = \frac{V_{01}^-}{V_{01}^+} = 0.2 \frac{V_{02}^+}{V_{01}^+} + 0.5 \frac{V_{03}^+}{V_{01}^+}$$

$$\mathcal{T}_{21} = \frac{V_{02}^-}{V_{01}^+} = 0.5 + 0.2 \frac{V_{03}^+}{V_{01}^+}$$

$$\frac{V_{03}^-}{V_{01}^+} = 0.5 + 0.5 \frac{V_{02}^+}{V_{01}^+}$$

$$\frac{V_{02}^+}{V_{01}^+} = 0$$

$$\frac{V_{03}^+}{V_{01}^+} = -\frac{V_{03}^-}{V_{01}^+}$$

Look what we have—**5** equations and **5** unknowns! Inserting equations 4 and 5 into equations 1 through 3, we get:

$$\Gamma_1 = \frac{V_{01}^-}{V_{01}^+} = -0.5 \frac{V_{03}^+}{V_{01}^+}$$

$$T_{21} = \frac{V_{02}^-}{V_{01}^+} = 0.5 - 0.2 \frac{V_{03}^+}{V_{01}^+}$$

$$\frac{V_{03}^-}{V_{01}^+} = 0.5$$

Solving, we find:

$$\Gamma_1 = -0.5(0.5) = -0.25$$

$$T_{21} = 0.5 - 0.2(0.5) = 0.4$$

Example: Scattering Parameters

Consider a **two-port device** with a scattering matrix (at some specific frequency ω_0):

$$\mathcal{S}(\omega = \omega_0) = \begin{bmatrix} 0.1 & j0.7 \\ j0.7 & -0.2 \end{bmatrix}$$

and $Z_0 = 50\Omega$.

Say that the transmission line connected to **port 2** of this device is terminated in a **matched load**, and that the wave **incident on port 1** is:

$$V_1^+(z_1) = -j2 e^{-j\beta z_1}$$

where $z_{1p} = z_{2p} = 0$.

Determine:

1. the port voltages $V_1(z_1 = z_{1p})$ and $V_2(z_2 = z_{2p})$.
2. the port currents $I_1(z_1 = z_{1p})$ and $I_2(z_2 = z_{2p})$.
3. the net power flowing into port 1

1. Since the **incident** wave on port 1 is:

$$V_1^+(z_1) = -j2 e^{-j\beta z_1}$$

we can conclude (since $z_{1\rho} = 0$):

$$\begin{aligned} V_1^+(z_1 = z_{1\rho}) &= -j2 e^{-j\beta z_{1\rho}} \\ &= -j2 e^{-j\beta(0)} \\ &= -j2 \end{aligned}$$

and since port 2 is **matched** (and **only** because its matched!), we find:

$$\begin{aligned} V_1^-(z_1 = z_{1\rho}) &= S_{11} V_1^+(z_1 = z_{1\rho}) \\ &= 0.1(-j2) \\ &= -j0.2 \end{aligned}$$

The voltage at port 1 is thus:

$$\begin{aligned} V_1(z_1 = z_{1\rho}) &= V_1^+(z_1 = z_{1\rho}) + V_1^-(z_1 = z_{1\rho}) \\ &= -j2.0 - j0.2 \\ &= -j2.2 \\ &= 2.2 e^{-j\pi/2} \end{aligned}$$

Likewise, since port 2 is **matched**:

$$V_2^+(z_2 = z_{2\rho}) = 0$$

And also:

$$\begin{aligned} V_2^-(z_2 = z_{2P}) &= S_{21} V_1^+(z_1 = z_{1P}) \\ &= j0.7 (-j2) \\ &= 1.4 \end{aligned}$$

Therefore:

$$\begin{aligned} V_2(z_2 = z_{2P}) &= V_2^+(z_2 = z_{2P}) + V_2^-(z_2 = z_{2P}) \\ &= 0 + 1.4 \\ &= 1.4 \\ &= 1.4 e^{-j0} \end{aligned}$$

2. The port **currents** can be easily determined from the results of the previous section.

$$\begin{aligned} I_1(z_1 = z_{1P}) &= I_1^+(z_1 = z_{1P}) - I_1^-(z_1 = z_{1P}) \\ &= \frac{V_1^+(z_1 = z_{1P})}{Z_0} - \frac{V_1^-(z_1 = z_{1P})}{Z_0} \\ &= -j \frac{2.0}{50} + j \frac{0.2}{50} \\ &= -j \frac{1.8}{50} \\ &= -j0.036 \\ &= 0.036 e^{-j\pi/2} \end{aligned}$$

and:

$$\begin{aligned}
 I_2(z_2 = z_{2P}) &= I_2^+(z_2 = z_{2P}) - I_2^-(z_2 = z_{2P}) \\
 &= \frac{V_2^+(z_2 = z_{2P})}{Z_0} - \frac{V_2^-(z_2 = z_{2P})}{Z_0} \\
 &= \frac{0}{50} - \frac{1.4}{50} \\
 &= -0.028 \\
 &= 0.028 e^{+j\pi}
 \end{aligned}$$

3. The net power flowing into port 1 is:

$$\begin{aligned}
 \Delta P_1 &= P_1^+ - P_1^- \\
 &= \frac{|V_{01}^+|^2}{2Z_0} - \frac{|V_{01}^-|^2}{2Z_0} \\
 &= \frac{(2)^2 - (0.2)^2}{2(50)} \\
 &= 0.0396 \text{ Watts}
 \end{aligned}$$

Matched, Lossless, Reciprocal Devices

A microwave device can be **lossless** or **reciprocal**. In addition, we can likewise classify it as being **matched**.

Let's examine **each** of these three characteristics, and how they relate to the **scattering matrix**.

Matched

A matched device is another way of saying that the **input impedance** at each port is **equal to Z_0** when **all other** ports are terminated in **matched loads**. For this condition, the **reflection coefficient** of each port is **zero**—no signal will be come out of a port if a signal is incident on that port (but **only** that port!).

In other words, we want:

$$V_m^- = S_{mm} V_m^+ = 0 \quad \text{for all } m$$

a result that occurs when:

$$S_{mm} = 0 \quad \text{for all } m \text{ if matched}$$

We find therefore that a matched device will exhibit a scattering matrix where all **diagonal elements** are zero.

Therefore:

$$\mathbf{S} = \begin{bmatrix} 0 & 0.1 & j0.2 \\ 0.1 & 0 & 0.3 \\ j0.2 & 0.3 & 0 \end{bmatrix}$$

is an example of a scattering matrix for a **matched**, three port device.

Lossless

For a lossless device, all of the power that delivered to each device port must eventually find its way **out!**

In other words, power is not **absorbed** by the network—no power to be **converted to heat!**

Recall the **power incident** on some port m is related to the amplitude of the **incident wave** (V_{0m}^+) as:

$$P_m^+ = \frac{|V_{0m}^+|^2}{2Z_0}$$

While power of the **wave exiting** the port is:

$$P_m^- = \frac{|V_{0m}^-|^2}{2Z_0}$$

Thus, the power **delivered** to (absorbed by) that port is the **difference** of the two:

$$\Delta P_m = P_m^+ - P_m^- = \frac{|V_{0m}^+|^2}{2Z_0} - \frac{|V_{0m}^-|^2}{2Z_0}$$

Thus, the **total power incident** on an N -port device is:

$$P^+ = \sum_{m=1}^N P_m^+ = \frac{1}{2Z_0} \sum_{m=1}^N |V_{0m}^+|^2$$

Note that:

$$\sum_{m=1}^N |V_{0m}^+|^2 = (\mathbf{V}^+)^H \mathbf{V}^+$$

where operator H indicates the **conjugate transpose** (i.e., Hermetian transpose) operation, so that $(\mathbf{V}^+)^H \mathbf{V}^+$ is the **inner product** (i.e., dot product, or scalar product) of complex vector \mathbf{V}^+ with itself.

Thus, we can write the **total power incident** on the device as:

$$P^+ = \frac{1}{2Z_0} \sum_{m=1}^N |V_{0m}^+|^2 = \frac{(\mathbf{V}^+)^H \mathbf{V}^+}{2Z_0}$$

Similarly, we can express the **total power of the waves exiting** our M -port network to be:

$$P^- = \frac{1}{2Z_0} \sum_{m=1}^N |V_{0m}^-|^2 = \frac{(\mathbf{V}^-)^H \mathbf{V}^-}{2Z_0}$$

Now, recalling that the incident and exiting wave amplitudes are **related** by the **scattering matrix** of the device:

$$\mathbf{V}^- = \mathbf{S} \mathbf{V}^+$$

Thus we find:

$$P^- = \frac{(\mathbf{V}^-)^H \mathbf{V}^-}{2Z_0} = \frac{(\mathbf{V}^+)^H \mathbf{S}^H \mathbf{S} \mathbf{V}^+}{2Z_0}$$

Now, the **total power delivered** to the network is:

$$\Delta P = \sum_{m=1}^M \Delta P = P^+ - P^-$$

Or explicitly:

$$\begin{aligned} \Delta P &= P^+ - P^- \\ &= \frac{(\mathbf{V}^+)^H \mathbf{V}^+}{2Z_0} - \frac{(\mathbf{V}^+)^H \mathbf{S}^H \mathbf{S} \mathbf{V}^+}{2Z_0} \\ &= \frac{1}{2Z_0} (\mathbf{V}^+)^H (\mathbf{I} - \mathbf{S}^H \mathbf{S}) \mathbf{V}^+ \end{aligned}$$

where \mathbf{I} is the **identity matrix**.

Q: *Is there actually some **point** to this long, rambling, complex presentation?*

A: Absolutely! If our M-port device is lossless then the total power exiting the device must **always** be equal to the total power incident on it.

If network is **lossless**, then $P^+ = P^-$.

Or stated another way, the total **power delivered** to the device (i.e., the power absorbed by the device) must always be **zero** if the device is lossless!

If network is **lossless**, then $\Delta P = 0$

Thus, we can conclude from our math that for a **lossless device**:

$$\Delta P = \frac{1}{2Z_0} (\mathbf{V}^+)^H (\mathbf{I} - \mathbf{S}^H \mathbf{S}) \mathbf{V}^+ = 0 \quad \text{for all } \mathbf{V}^+$$

This is true **only** if:

$$\mathbf{I} - \mathbf{S}^H \mathbf{S} = 0 \quad \Rightarrow \quad \mathbf{S}^H \mathbf{S} = \mathbf{I}$$

Thus, we can conclude that the **scattering matrix** of a **lossless** device has the **characteristic**:

If a network is **lossless**, then $\mathbf{S}^H \mathbf{S} = \mathbf{I}$

Q: *Huh? What exactly is this supposed to tell us?*

A: A matrix that satisfies $\mathbf{S}^H \mathbf{S} = \mathbf{I}$ is a special kind of matrix known as a **unitary matrix**.

If a network is **lossless**, then its scattering matrix S is **unitary**.

Q: How do I recognize a unitary matrix if I see one?

A: The **columns** of a unitary matrix form an **orthonormal set!**

$$S = \begin{bmatrix} S_{11} & S_{12} & S_{13} & S_{14} \\ S_{21} & S_{22} & S_{23} & S_{24} \\ S_{31} & S_{32} & S_{33} & S_{34} \\ S_{41} & S_{42} & S_{43} & S_{44} \end{bmatrix}$$

**matrix
columns**

In other words, each **column** of the scattering matrix will have a **magnitude equal to one**:

$$\sum_{m=1}^N |S_{mn}|^2 = 1 \quad \text{for all } n$$

while the inner product (i.e., dot product) of **dissimilar columns** must be **zero**.

$$\sum_{n=1}^N S_{ni} S_{nj}^* = S_{1i} S_{1j}^* + S_{2i} S_{2j}^* + \cdots + S_{Ni} S_{Nj}^* = 0 \quad \text{for all } i \neq j$$

In other words, dissimilar columns are **orthogonal**.

Consider, for example, a lossless **three-port** device. Say a signal is incident on port 1, and that **all other ports are terminated**. The power **incident** on port 1 is therefore:

$$P_1^+ = \frac{|V_{01}^+|^2}{2Z_0}$$

while the power **exiting** the device at each port is:

$$P_m^- = \frac{|V_{0m}^-|^2}{2Z_0} = \frac{|S_{m1}V_{01}^-|^2}{2Z_0} = |S_{m1}|^2 P_1^+$$

The **total** power exiting the device is therefore:

$$\begin{aligned} P^- &= P_1^- + P_2^- + P_3^- \\ &= |S_{11}|^2 P_1^+ + |S_{21}|^2 P_1^+ + |S_{31}|^2 P_1^+ \\ &= (|S_{11}|^2 + |S_{21}|^2 + |S_{31}|^2) P_1^+ \end{aligned}$$

Since this device is **lossless**, then the incident power (**only** on port 1) is **equal** to exiting power (i.e, $P^- = P_1^+$). This is true **only** if:

$$|S_{11}|^2 + |S_{21}|^2 + |S_{31}|^2 = 1$$

Of course, this will likewise be true if the incident wave is placed on **any** of the **other** ports of this lossless device:

$$\begin{aligned} |S_{12}|^2 + |S_{22}|^2 + |S_{32}|^2 &= 1 \\ |S_{13}|^2 + |S_{23}|^2 + |S_{33}|^2 &= 1 \end{aligned}$$

We can state in general then that:

$$\sum_{m=1}^3 |S_{mn}|^2 = 1 \quad \text{for all } n$$

In other words, the columns of the scattering matrix must have **unit magnitude** (a requirement of all **unitary** matrices). It is apparent that this must be true for energy to be conserved.

An **example** of a (unitary) scattering matrix for a **lossless** device is:

$$\mathbf{S} = \begin{bmatrix} 0 & 1/2 & j\sqrt{3}/2 & 0 \\ 1/2 & 0 & 0 & j\sqrt{3}/2 \\ j\sqrt{3}/2 & 0 & 0 & 1/2 \\ 0 & j\sqrt{3}/2 & 1/2 & 0 \end{bmatrix}$$

Reciprocal

Recall **reciprocity** results when we build a **passive** (i.e., unpowered) device with **simple** materials.

For a reciprocal network, we find that the elements of the scattering matrix are **related** as:

$$S_{mn} = S_{nm}$$

For example, a **reciprocal** device will have $S_{21} = S_{12}$ or $S_{32} = S_{23}$. We can write reciprocity in matrix form as:

$$\mathbf{S}^T = \mathbf{S} \quad \text{if reciprocal}$$

where T indicates (non-conjugate) transpose.

An **example** of a scattering matrix describing a **reciprocal**, but **lossy** and **non-matched** device is:

$$\underline{\underline{\mathbf{S}}} = \begin{bmatrix} 0.10 & -0.40 & -j0.20 & 0.05 \\ -0.40 & j0.20 & 0 & j0.10 \\ -j0.20 & 0 & 0.10 - j0.30 & -0.12 \\ 0.05 & j0.10 & -0.12 & 0 \end{bmatrix}$$