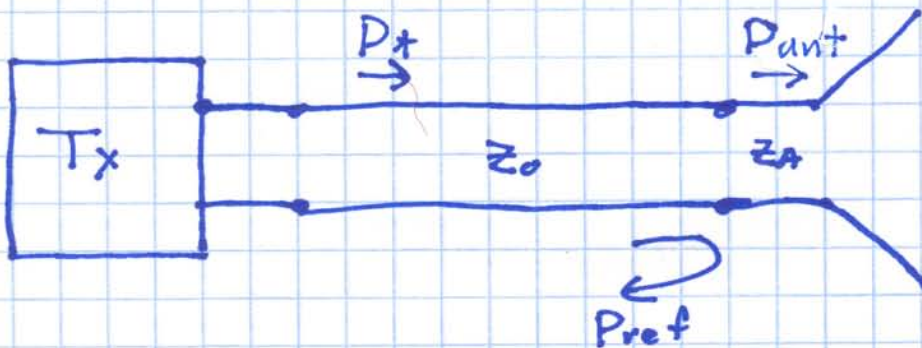


# Antenna Impedance

To transfer all available transmitter power to the antenna, we must make the reflected power = 0.



i.e.  $P_t = P_{ant} + P_{ref}$

∴ make  $P_{ref} = 0$ , so that ∴

$$P_{ant} = P_t$$

To accomplish this,  $Z_A$  must be matched ∴

$$\underline{\underline{Z_A = Z_0}}$$

Q: Huh??  $Z_0$  is a real value, ∴  
 $Z_A = Z_0$  is a resistor !?!



⇒ It would seem that a resistor would make a lousy antenna!

- But, think about this. A resistor does not reflect power because it can absorb power. Reactive elements cannot absorb power, so power is reflected entirely.
- Antennas absorb power as well; the difference is that antennas radiate this absorbed power, while a resistor converts it to heat.

Q: Does this mean that antennas reflect no power??


A: No! In general, antennas both reflect and absorb power.

i.e.  $Z_A$  has both a real (resistive) and imaginary (reactive) component.

$$\Rightarrow Z_A = R_A + jX_A$$



∞ Circuit model is:

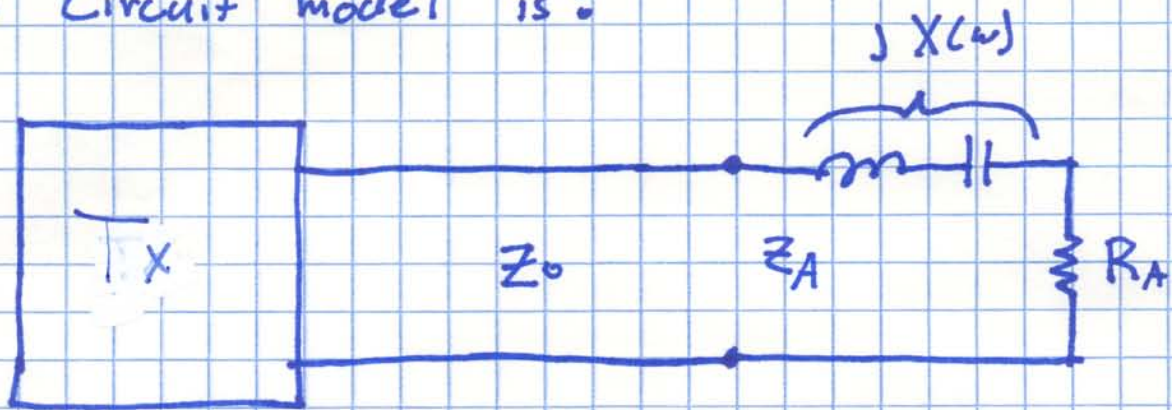

Note antenna input impedance, like other antenna parameters, is generally frequency dependent.

**Q:** So how do we eliminate (or, at least minimize) the reflected power??

**A1:** Design the antenna such that  $R_A = Z_0$  (e.g.  $50\ \Omega$ ,  $75\ \Omega$ ,  $300\ \Omega$ ), and operate at frequency  $\omega$  such that  $X(\omega) \approx 0 \Rightarrow Z_A = Z_0$

**A2:** Implement a matching network!

