

# Example: CMOS Logic Gate Synthesis

**Problem:** Design a CMOS digital circuit that realizes the Boolean function:

$$Y = \overline{A + B + \overline{A} \overline{C}}$$

**Solution:** Follow the steps of the **design synthesis** handout!

**Step1:** Design the PDN

First, we must **rewrite** the Boolean function as:

$$\overline{Y} = f(A, B, C)$$

In other words, write the **complemented output** in terms of **un-complemented inputs**.



*Time to recall our  
Boolean algebra skills!*

We must first complement this equation, and then apply **DeMorgan's Theorem** (several times!).


$$\begin{aligned}
 Y &= \overline{A+B} + \overline{A} \overline{C} \\
 \overline{Y} &= \overline{\overline{A+B} + \overline{A} \overline{C}} \\
 &= \overline{(\overline{A+B})} \overline{(\overline{A} \overline{C})} \\
 &= (A+B) (\overline{\overline{A}} + \overline{\overline{C}}) \\
 &= (A+B) (A+C) \\
 &= AA + AC + BA + BC \\
 &= A(A+B+C) + BC \\
 &= A + BC
 \end{aligned}$$

Logically, this result says:



*Y is low if A is high, **OR** if both B **AND** C are high.*

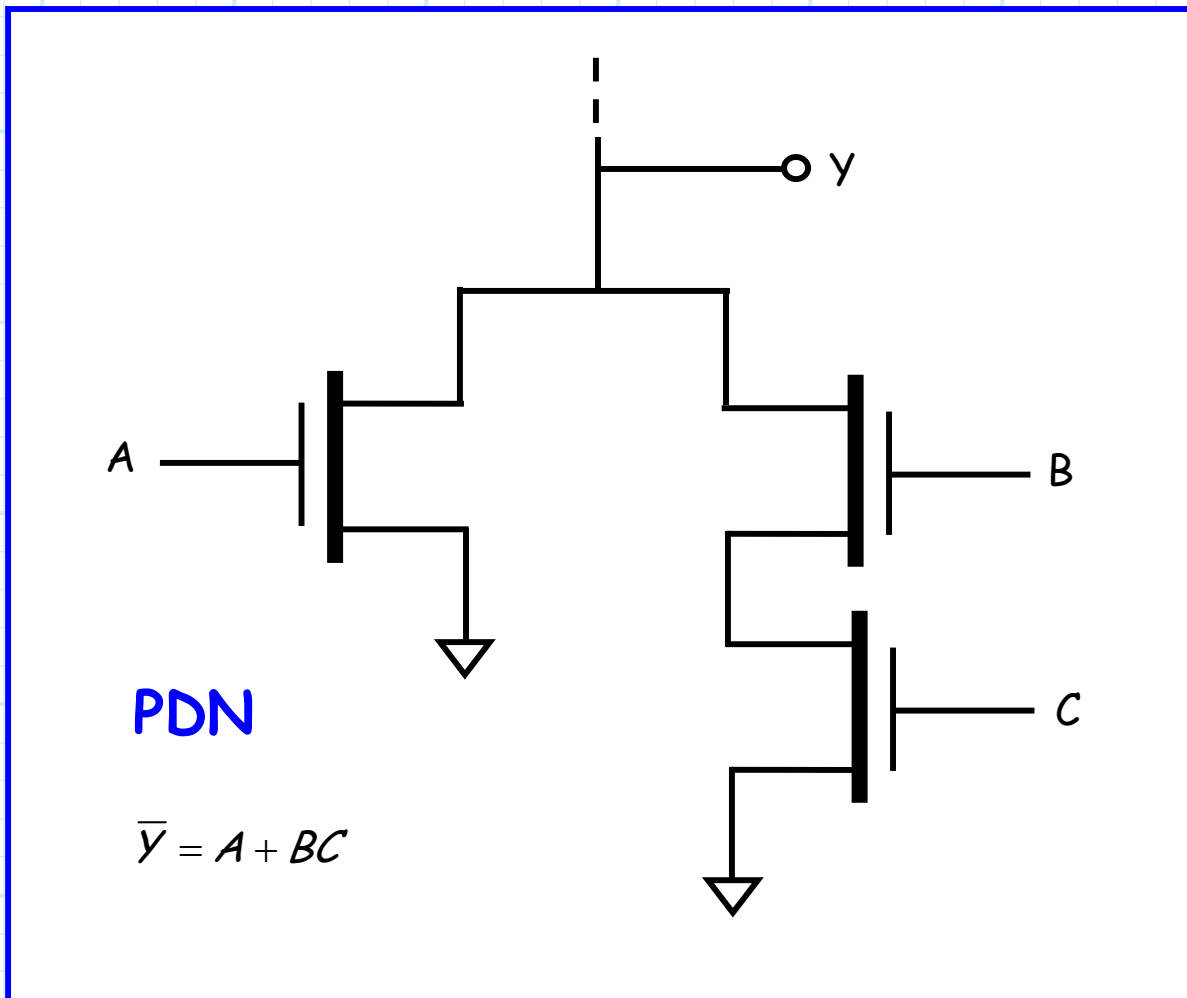We can thus realize this logic with the following **NMOS PDN**:



**Step2:** Design the PUN

First, we must **rewrite** the Boolean function as:


$$Y = f(\bar{A}, \bar{B}, \bar{C})$$

In other words, write the **un-complemented output** in terms of **complemented inputs**.


Again, using DeMorgan's Theorem:

$$\begin{aligned} Y &= \overline{A + B + \overline{A} \overline{C}} \\ &= \overline{A} \overline{B} + \overline{A} \overline{C} \\ &= \overline{A} (\overline{B} + \overline{C}) \end{aligned}$$

Logically, this result says:

 

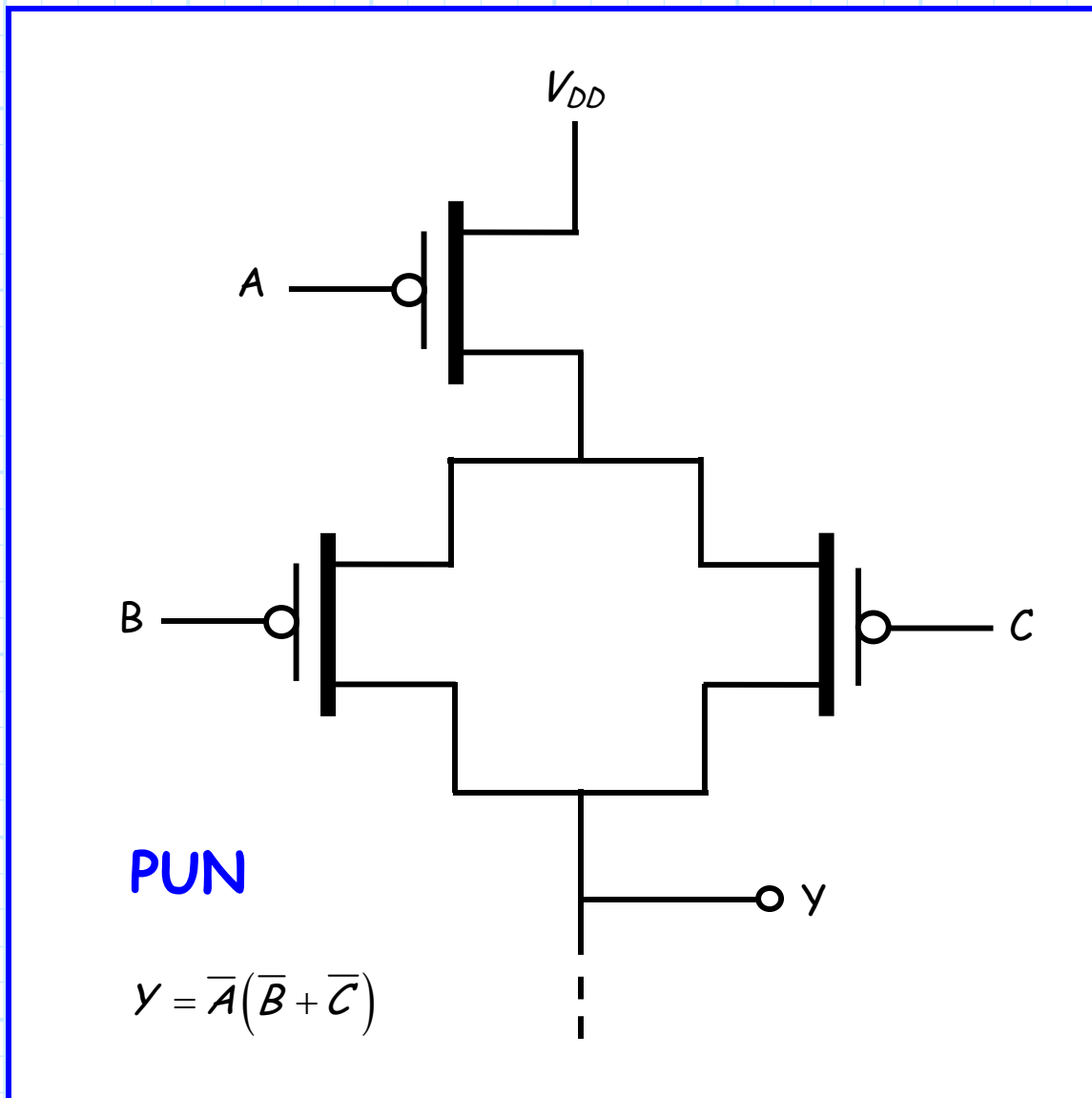We can thus realize this logic with the following **PMOS PUN**:



Thus, the **entire** CMOS realization is:

