

## 3.6 Limiting and Clamping Circuits

Reading Assignment: pp. 184-187 (i.e., neglect section 3.6.2)

Another application of junction diodes →

Q: *What is a limiter?*

A: A 2-port device that **restricts** (i.e., limits) the voltage across a device to some specified region.

→

HO: Diode Limiters

Q:

A: HO: Steps for Analyzing Limiter Circuits

Example: A Diode Limiter



# Diode Limiters

Often, a voltage source (either DC or AC) is used to supply an electronic device that is very **expensive** and/or very **sensitive**.

In this case, we may choose to insert a **diode limiter** between the source and the device—this limiter will provide **over-voltage protection**!



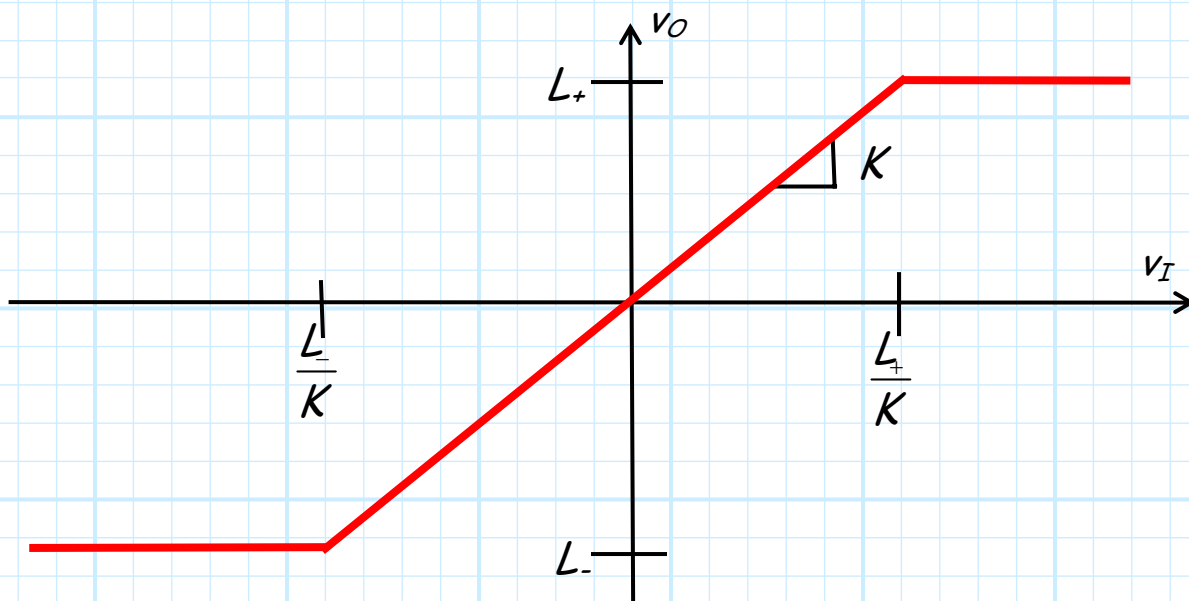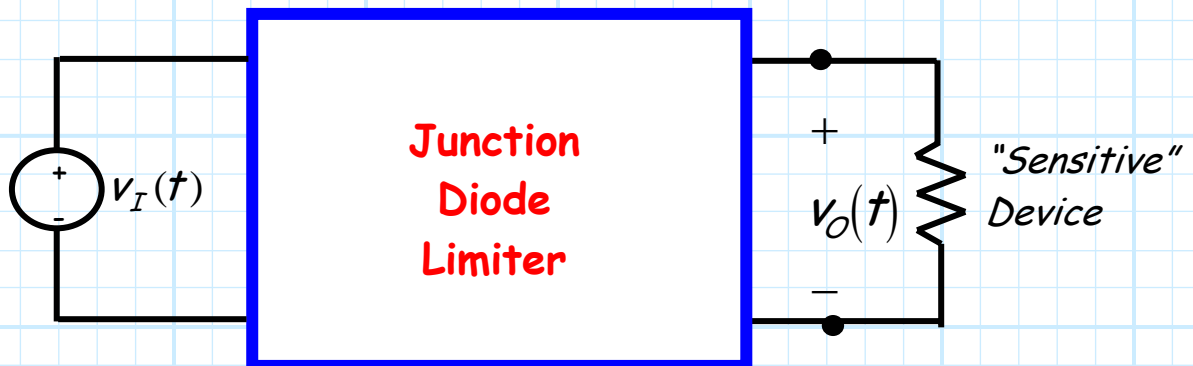To see how, we should first consider a typical **transfer function** for a junction diode limiter:



Note that this transfer function indicates that the **output** voltage  $v_o$  can **never** be more than a **maximum** voltage  $L_+$ , nor less than a **minimum** voltage  $L_-$ .

\* Thus, the device places some **limits** on the value of the **output** voltage:

$$L_- < v_o < L_+ \quad \text{for any } v_I$$

\* The limits  $L_-$  and  $L_+$  provide a **safe** operating value for  $v_o$ , the voltage across our "sensitive" electronic device.


\* Presumably, if **no limiter** were present, we might find that  $v_o > L_+$  or  $v_o < L_-$ , resulting in **damage** to the device!

\* Note although  $L_+ > L_-$ , the values of  $L_-$  and  $L_+$  may be both **positive**, both **negative**, or even **zero**.

For example, a limiter with  $L_- = 0$  ( $L_+ > 0$ ) would prevent the voltage from ever becoming **negative** (positive). We find that for many devices, the **wrong** voltage **polarity** can be **destructive!**

To illustrate, let's consider an **example** input voltage  $v_I(t)$ , and the resulting output voltage when passed through a **limiter** with values  $L_- = 0$  and  $L_+ = 20$  V ( $K=1$ ). I.E.:
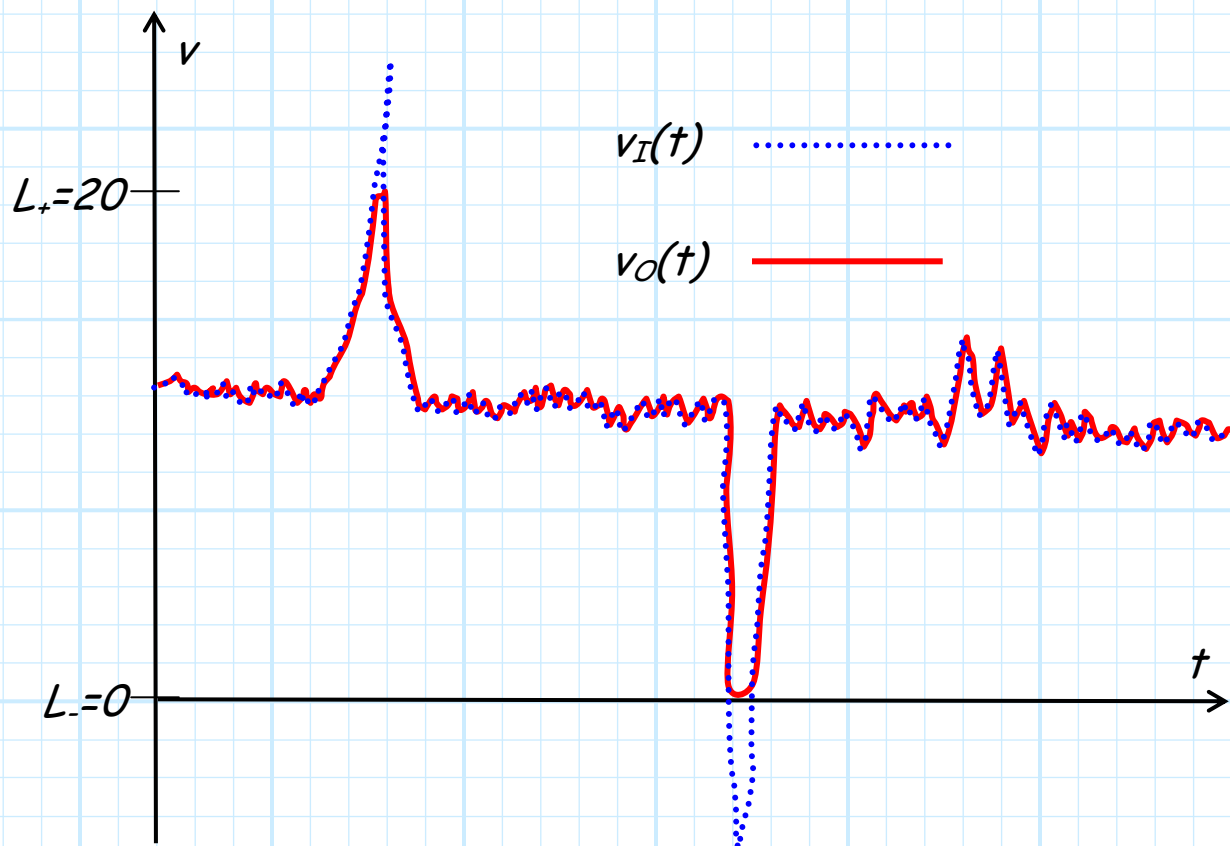
$$v_o = \begin{cases} 0 & \text{if } v_I < 0 \\ v_I & \text{if } 0 < v_I < 20 \\ 20 & \text{if } v_I > 20 \end{cases}$$



Note there are a couple of "hiccups" in the **input** voltage that take the voltage value **outside** the "safety" range of the sensitive device. However, the limiter does in fact **limit** these excursions, such that the voltage across the sensitive device **always** remains between 0 and 20 Volts.

**Q:** *Why would these "hiccups" occur?*

**A:** There are **many** possible reasons, including:


1. A power **surge** (e.g., lightning strike)
2. **Static** discharge
3. **Switching** transients (e.g., at power up or down).

Perhaps the most **prevalent** reason, however, is **operator error**.

→ Someone connects the **wrong** source to the sensitive device!

Thus, limiters are often used on expensive/sensitive devices to make them "**fool-proof**".

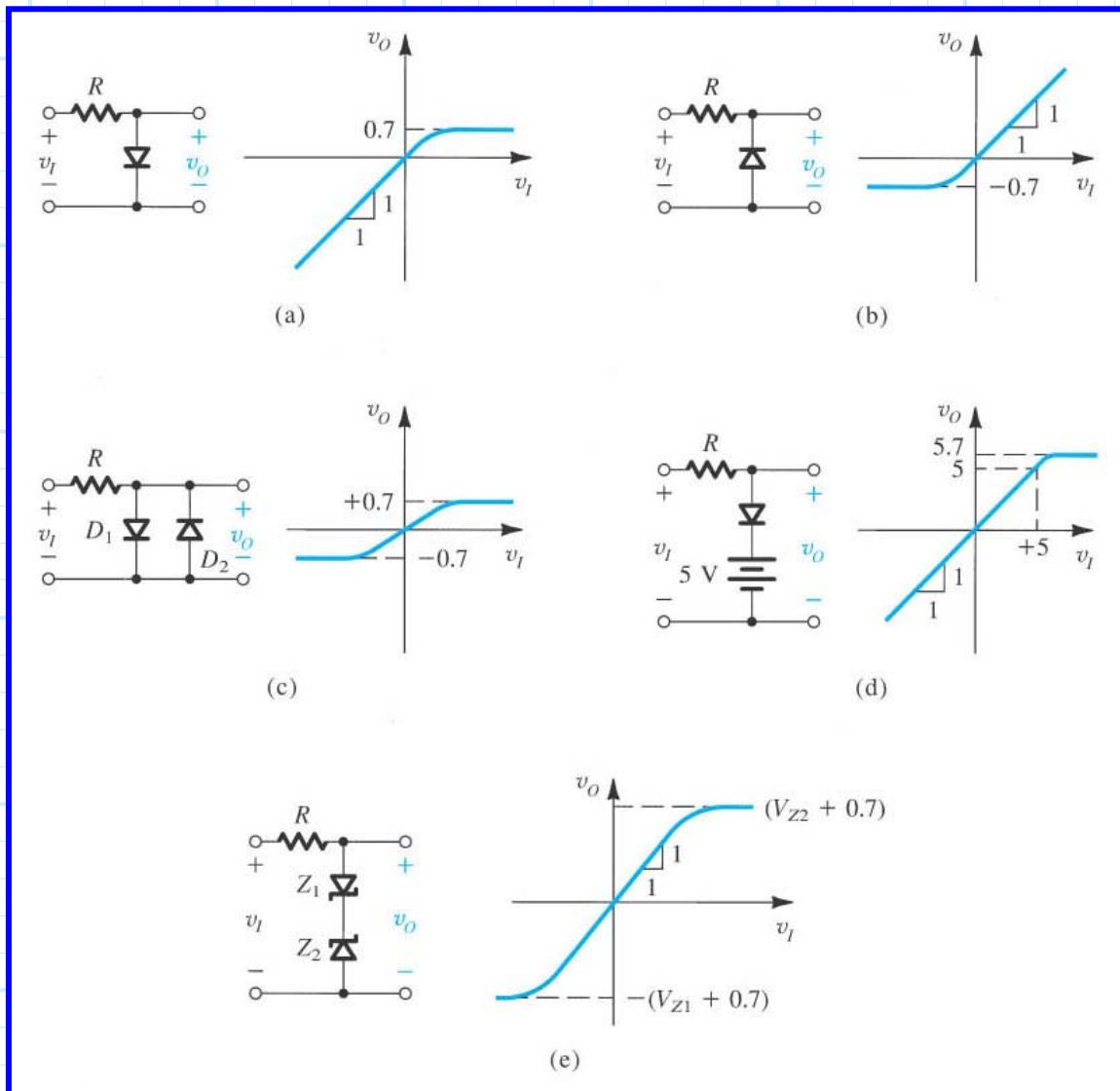Your book has many **examples** of limiter circuits, including:



# Steps for Analyzing Limiter Circuits

The junction diodes in most limiter circuits can/will be in forward bias, or reverse bias, or breakdown modes! Thus, the distinction between a Zener diode and a "normal" junction diode is essentially **meaningless**.

But, this presents us with a **big problem**—what diode **model** do we use to analyze a limiter? Recall that **none** of the diode models that we studied will provide accurate estimates for **all three** junction diode modes!

The **solution** we will use is to **change** the diode model we implement, as we consider **each** of the possible junction diode modes. Specifically:

## Junction Diode Mode

**Forward Bias**

**Reverse Bias**

**Breakdown**

## Junction Diode Model


**CVD model** with ideal diode f.b.

**Ideal diode** model with ideal diode r.b


**Zener CVD model** with ideal diode f.b.

Step 1:

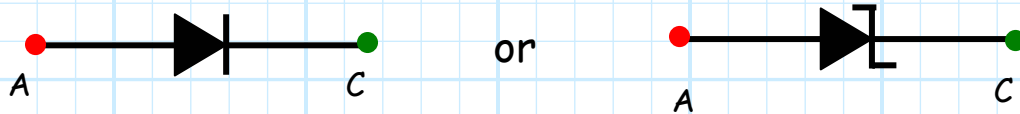Assume that the limiter diode is **forward biased**, so replace



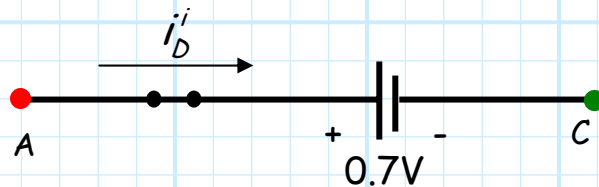with a **CVD model**, where the **ideal diode is forward biased**:




Now, using this model, **determine**:

1. The **output voltage**  $v_O$  in terms of input voltage  $v_I$ .
2. The **ideal diode current**  $i_D^i$  in terms of input voltage  $v_I$ .


Finally, we solve the **inequality**  $i_D^i > 0$  for  $v_I$ , thus determining **when** (i.e., for what values of  $v_I$ ) this assumption, and thus the derived expression for output voltage  $v_O$ , is true.

Step 2:

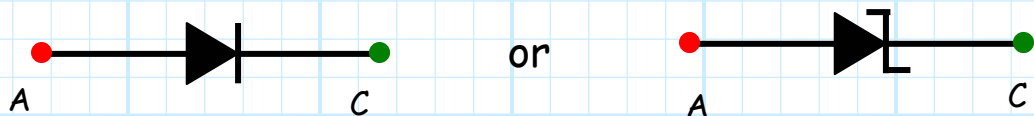Assume that the limiter diode is in **breakdown**, so replace



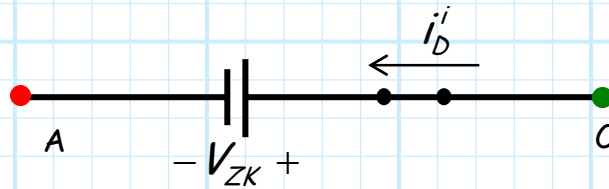with a **Zener CVD model**, where the **ideal diode is forward biased**:




Now, using this model, **determine**:

1. The **output voltage**  $v_O$  in terms of input voltage  $v_I$ .
2. The **ideal diode current**  $i_D^i$  in terms of input voltage  $v_I$ .


Finally, we solve the **inequality**  $i_D^i > 0$  for  $v_I$ , thus determining **when** (i.e., for what values of  $v_I$ ) this assumption, and thus the derived expression for output voltage  $v_O$ , is true.
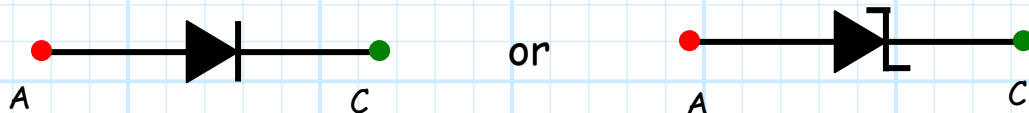
### Step 3:

Assume that the limiter diode is **reverse biased**, so replace



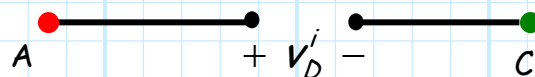with an **Ideal Diode model**, where the ideal diode is **reversed biased**:





Now, using this model, determine the **output voltage**  $v_O$  in terms of input voltage  $v_I$ .

**Q:** *What about  $v_D'$ ? Don't we need to likewise determine its value, and then determine **when**  $v_D' < 0$ ?*

**A:** Actually, **no**. If the junction diode is **not** forward biased and it is **not** in breakdown, then it **must** be reverse biased! As **obvious** as this statement is, we can use it determine **when** the junction diode is reverse biased—it's **when** the junction diode is **not** in forward bias **and when** it is **not** in reverse bias.

For **example**, say that we find that the junction diode is **forward biased** when:

$$v_I > 20 \text{ V},$$

and that the junction diode is in **breakdown** when:

$$v_I < -15 \text{ V}.$$

We can thus **conclude** that the junction diode is **reverse biased** when:


$$-15 \text{ V} < v_I < 20 \text{ V}$$

#### Step 4:

We take the result of the **previous 3 steps** and form a continuous, piecewise linear **transfer function** (make sure it's **continuous**, and that it's a **function!**).

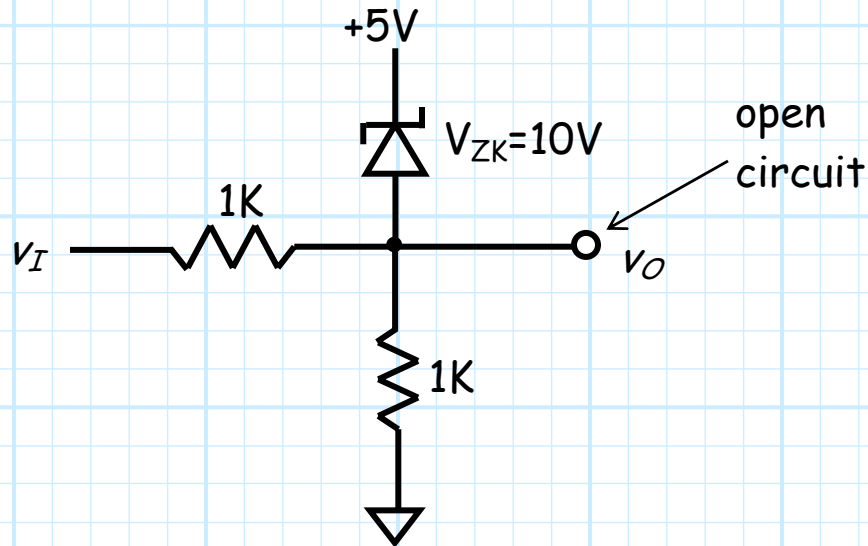
# Example: A Diode Limiter

Consider the following **junction diode circuit**:



This circuit is a **junction diode limiter**!

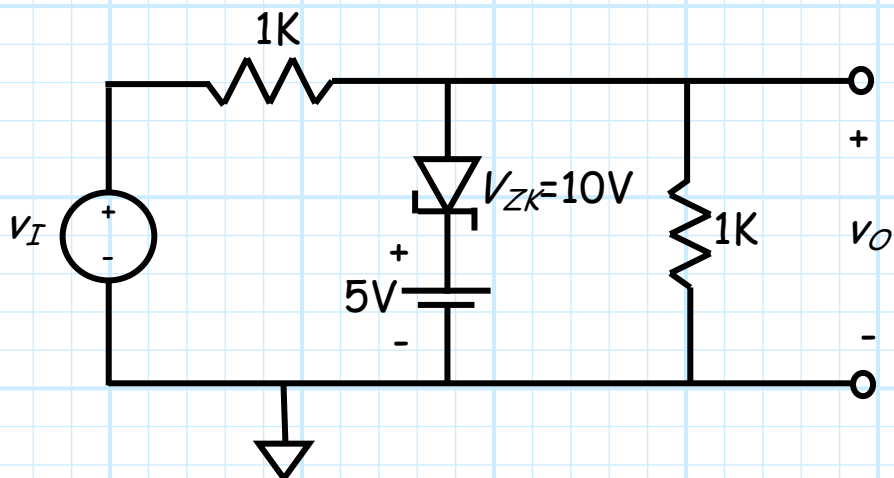Perhaps that would be clearer if we **redrew** this circuit as:




This is the **same** circuit as above!

Now, let's determine the **transfer function** of this limiter. To do this, we must follow the **4 steps** detailed in the previous handout!

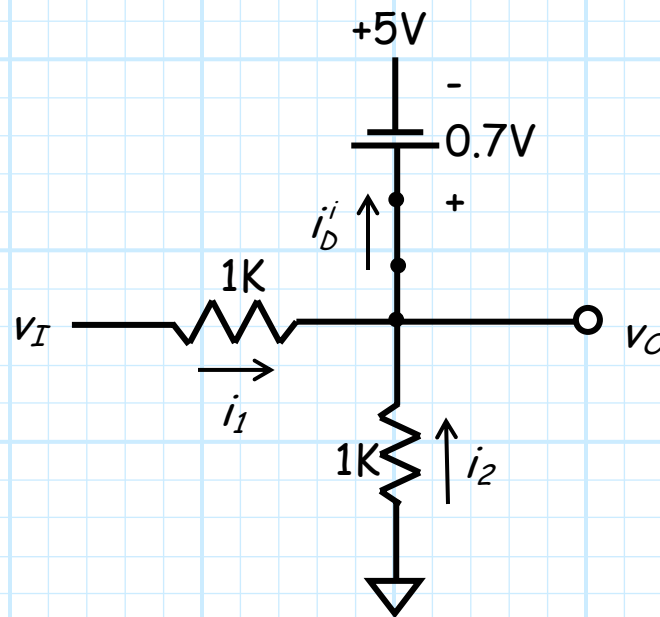**Step 1:** Assume junction diode is **forward biased**

Replace the junction diode with a **CVD model**. ASSUME the **ideal diode** is forward biased, ENFORCE  $v_D' = 0$ .



We find that the **output voltage** is simply:

$$v_o = 5.0 + 0.7 = 5.7 \text{ V}$$

while the **ideal diode current** is more difficult to determine.

From KCL:

$$i_D' = i_1 + i_2$$

where from Ohm's Law:

$$i_1 = \frac{v_I - 5.7}{1} = v_I - 5.7$$

and:

$$i_2 = \frac{0 - 5.7}{1} = -5.7$$

Thus, the **ideal** diode current is:

$$\begin{aligned} i_D^i &= i_1 + i_2 \\ &= v_I - 5.7 - 5.7 \\ &= v_I - 11.4 \end{aligned}$$

Now, for our assumption to be correct, this current must be **positive** (i.e.,  $i_D^i > 0$ ). Thus, we solve this **inequality** to determine **when** our assumption is true:


$$\begin{aligned} v_I - 11.4 &> 0 \\ v_I &> 11.4 \text{ V} \end{aligned}$$

So, from this step we find:

$$v_O = 5.7 \text{ V} \quad \text{when} \quad v_I > 11.4 \text{ V}$$

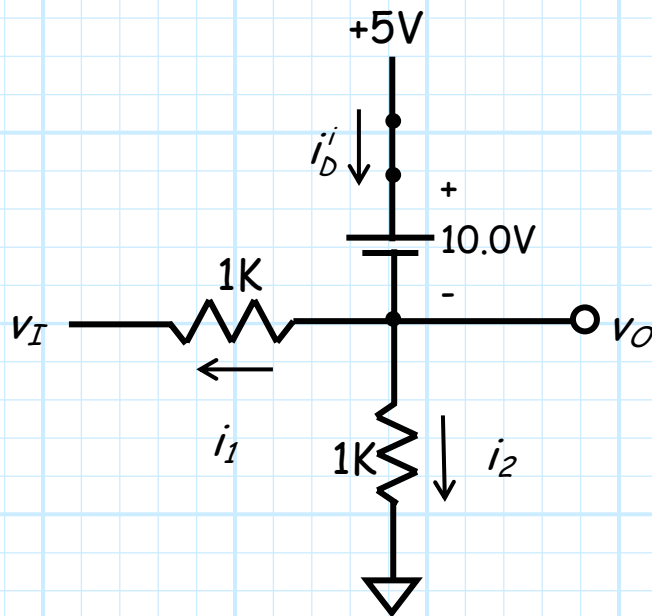**Step2:** Assume the **junction diode** is in **breakdown**

Replace the junction diode with a **Zener CVD** model. **ASSUME** the **ideal** diode is forward biased, **ENFORCE**  $v_D^i = 0$ .



We find that the **output voltage** is simply:

$$v_O = 5 - 10 = -5.0V$$

while the **ideal** diode current is more difficult to determine.

From KCL:

$$i_D' = i_1 + i_2$$

where from Ohm's Law:

$$i_1 = \frac{-5 - v_I}{1} = -v_I - 5.0$$

and:

$$i_2 = \frac{0 - 5.0}{1} = -5.0V$$

Thus, the **ideal** diode current is:

$$\begin{aligned}
 i_D^i &= i_1 + i_2 \\
 &= -v_I - 5.0 - 5.0 \\
 &= -v_I - 10.0
 \end{aligned}$$

Now, for our assumption to be correct, this current must be **positive** (i.e.,  $i_D^i > 0$ ). Thus, we solve this **inequality** to determine **when** our assumption is true:


$$\begin{aligned}
 -v_I - 10.0 &> 0 \\
 -v_I &> 10.0 \text{ V} \\
 v_I &< -10.0 \text{ V}
 \end{aligned}$$

So, from this step we find:

$$v_O = -5.0 \text{ V} \quad \text{when} \quad v_I < -10.0 \text{ V}$$

**Step 3:** Assume the junction diode is **reverse** biased

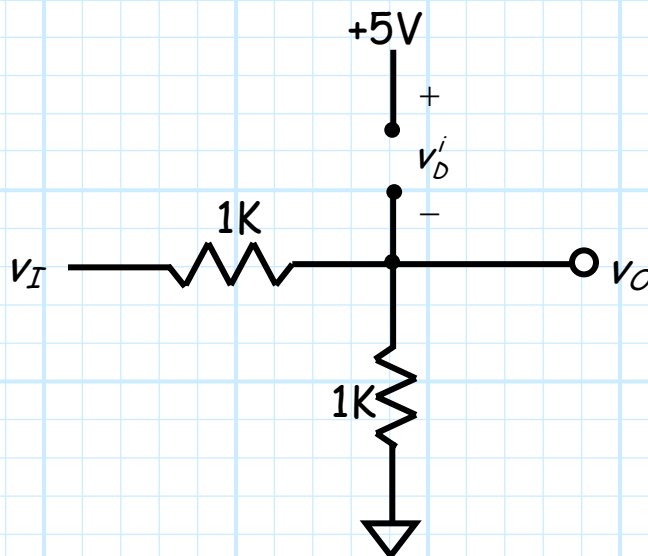Replace the junction diode with the **Ideal Diode** model.  
**ASSUME** the **ideal** diode is **reverse** biased, **ENFORCE**  $i_D^i = 0$ .



**A voltage divider!**

Thus the **output voltage** is:

$$\begin{aligned} v_o &= \frac{v_I(1)}{1+1} \\ &= \frac{v_I}{2} \end{aligned}$$


This output voltage is true **when** the junction diode is neither forward biased nor in breakdown. Thus, using the results from the first two steps, we can **infer** that it is true when:

$$-10.0 < v_I < 11.4$$

**Step 4:** Determine the continuous transfer function

Combining the results of the previous 3 steps, we get the following **continuous, piece-wise linear transfer function**:
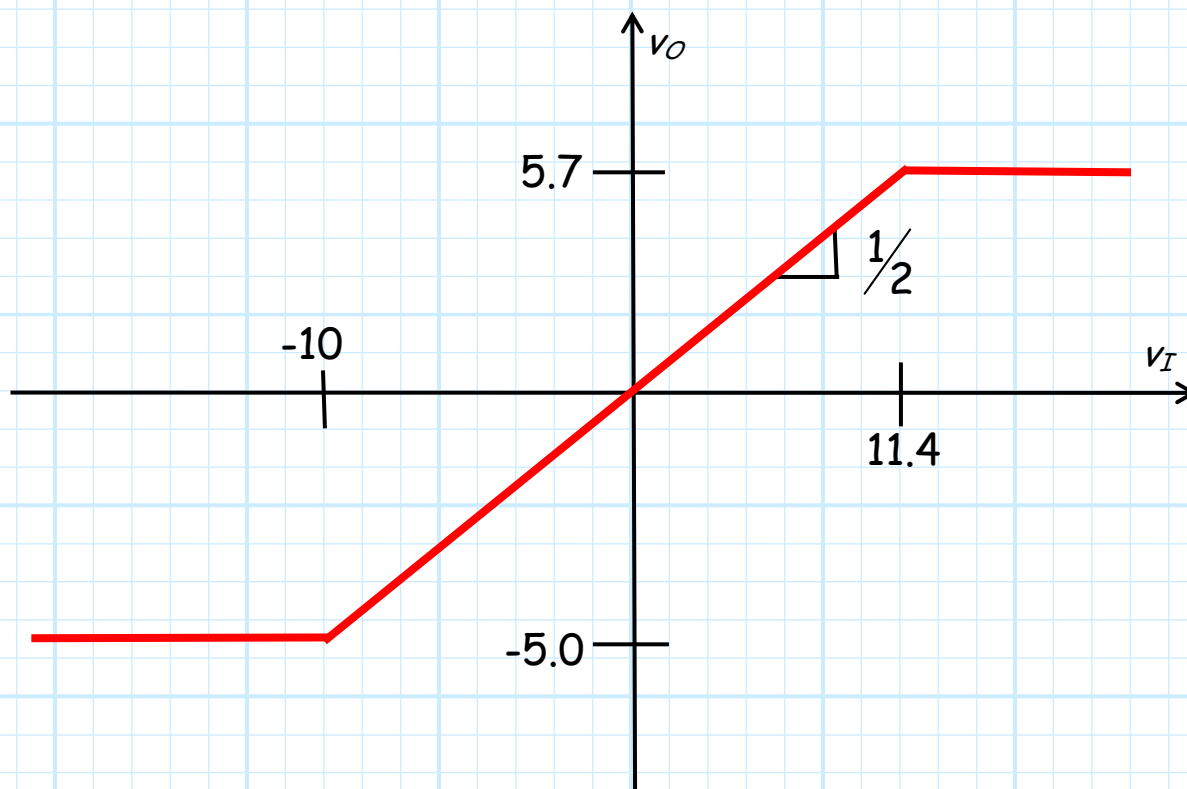
$$v_o = \begin{cases} 5.7 \text{ V} & \text{if } v_I > 11.4 \text{ V} \\ v_I/2 & \text{if } -10.0 < v_I < 11.4 \text{ V} \\ -5.0 \text{ V} & \text{if } v_I < -10.0 \text{ V} \end{cases}$$



Note that at  $v_I = -10$ :

$$v_O = \frac{v_I}{2} = \frac{-10}{2} = -5.0 \text{ V}$$

and at  $v_I = 11.4$ :

$$v_O = \frac{v_I}{2} = \frac{11.4}{2} = 5.7 \text{ V}$$

Thus, this function is continuous!