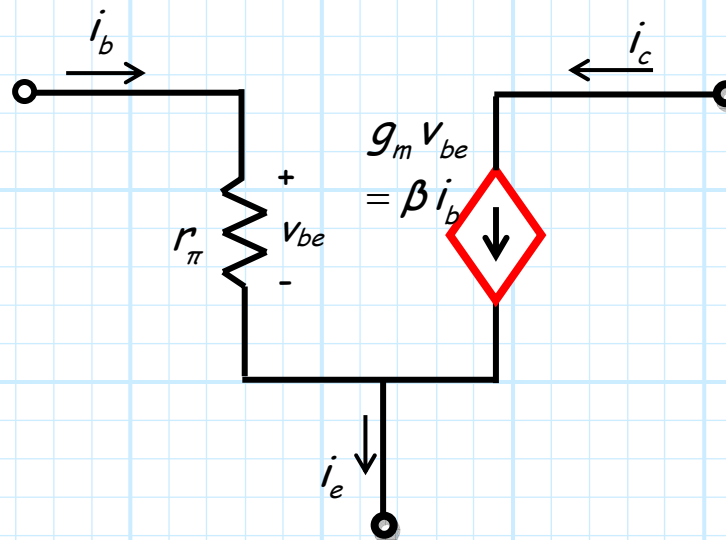


The Hybrid- Π and T Models

Consider again the small-signal equations for an npn BJT biased in the active mode:

$$i_b = \frac{v_{be}}{r_\pi} \quad i_c = g_m v_{be} = \beta i_b \quad i_e = i_b + i_c \quad (\text{KCL})$$

Now, analyze **this** circuit:



Do these equations look familiar?

From Ohm's Law:


$$i_b = \frac{v_{be}}{r_\pi}$$

From KCL:

$$i_c = g_m v_{be} = \beta i_b$$

And also from KCL:

$$i_e = i_b + i_c \quad (KCL)$$

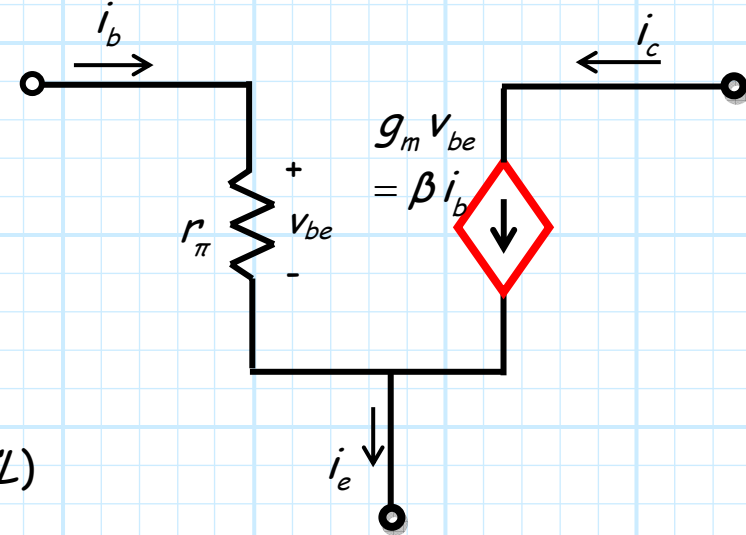

Q: Hey! Aren't these the *same* three equations as the *npn BJT small-signal equations*?

A: They *are* indeed!


With respect to the small-signal currents and voltages in a circuit (but **only** small-signal voltages and currents), an *npn* BJT in active mode might as well be **this** circuit.

Two equivalent circuits

Thus, this circuit can be used as an **equivalent circuit** for BJT small-signal analysis (but **only** for small signal analysis!).

This equivalent circuit is called the Hybrid-II model for a BJT biased in the **active mode**:


npn Hybrid-II Model

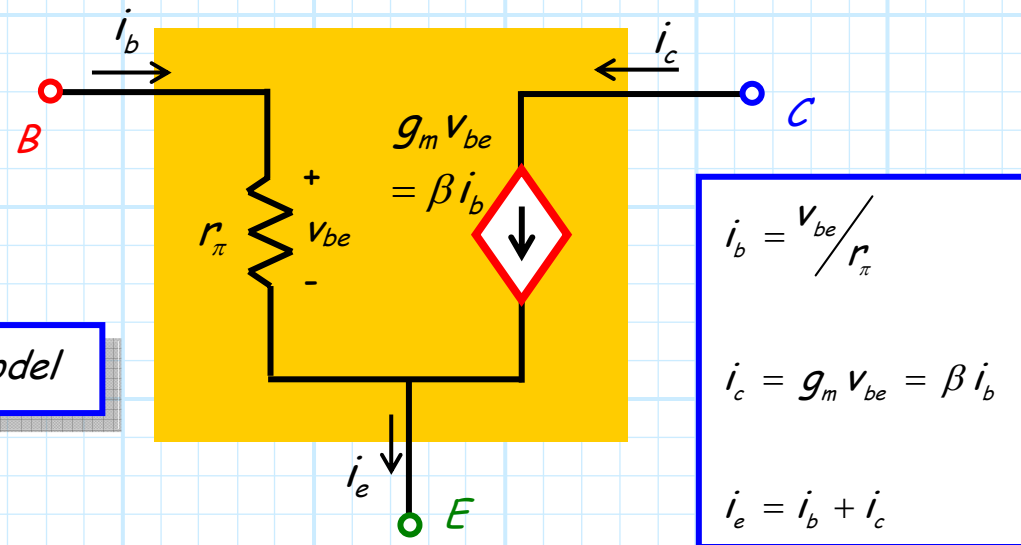

$$i_b = v_{eb} / r_\pi$$

$$i_c = g_m v_{eb} = \beta i_b$$

$$i_e = i_b + i_c$$

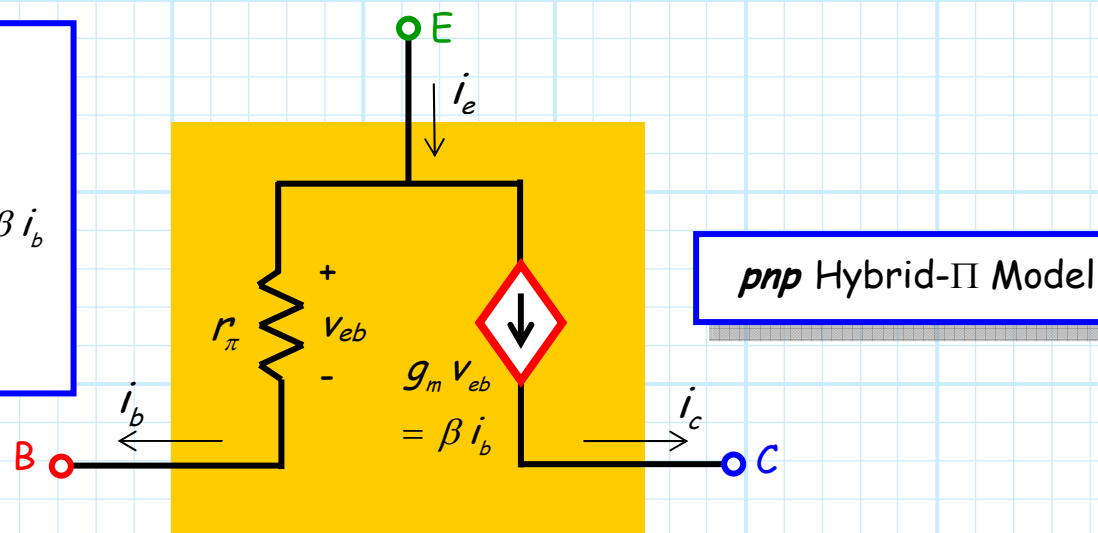


An alternative equivalent circuit


Note however, that we can **alternatively** express the small-signal circuit equations as:

$$i_b = i_e - i_c \quad i_c = g_m v_{be} = \beta i_b \quad i_e = \frac{v_{be}}{r_e}$$

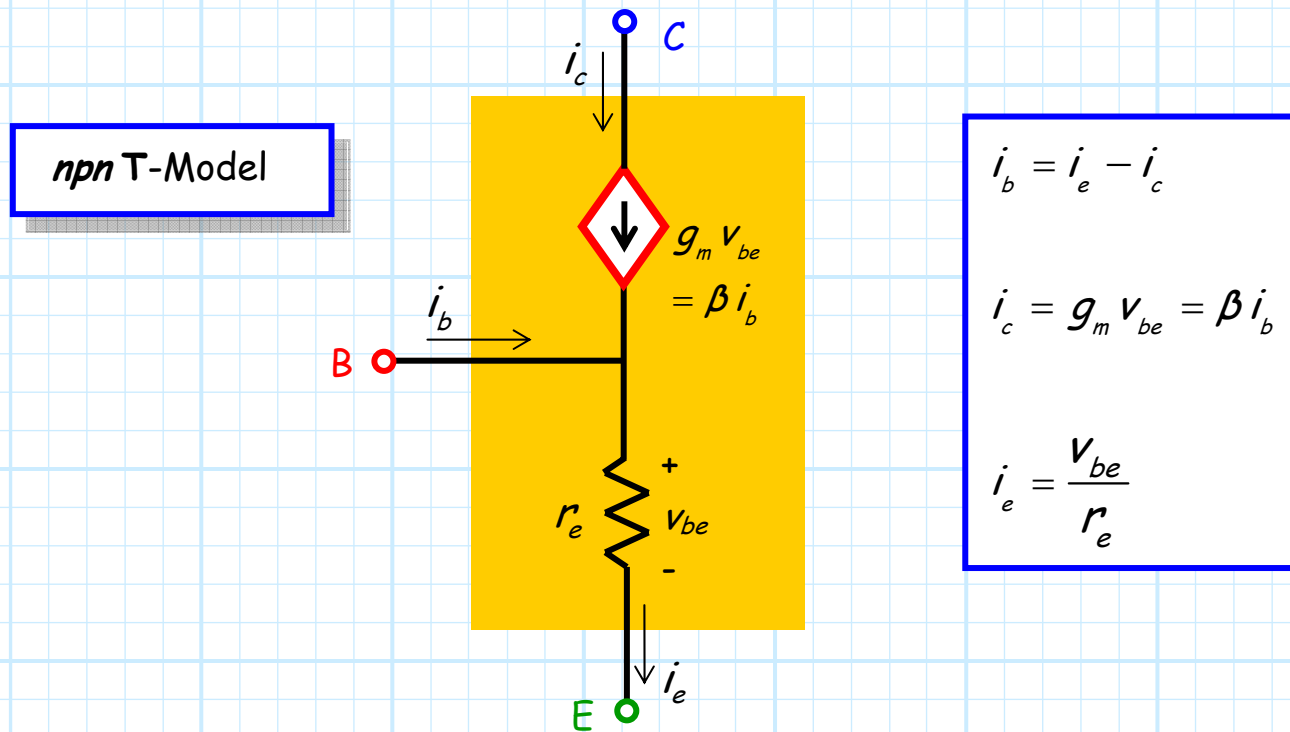These equations likewise describes the **T-Model**—an **alternative but equivalent** model to the Hybrid-II.



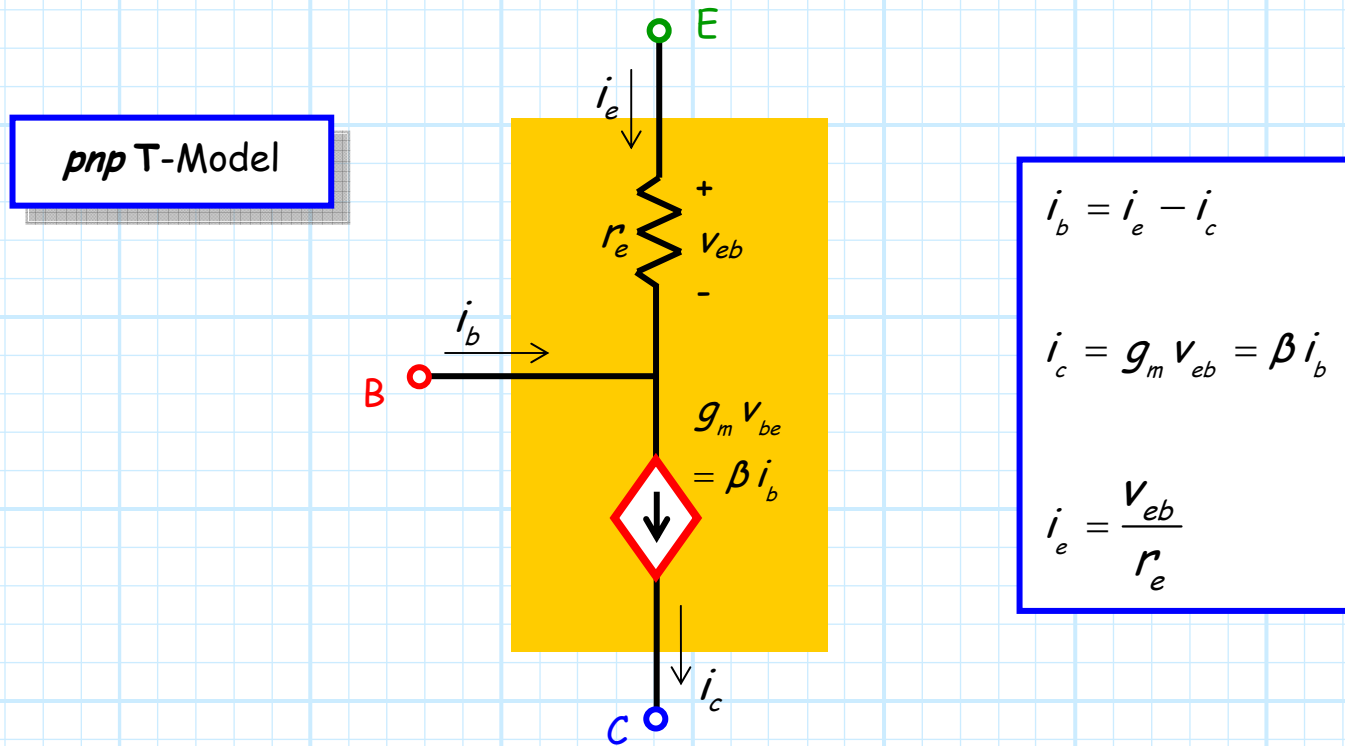I just couldn't fit the *pnp* T-model on the previous page



So many choices; which should I use?

The Hybrid-II and the **T** circuit models are equivalent—they **both** will result in the **same** correct answer!



Therefore, you do **not** need to worry about which one to use for a particular small-signal circuit analysis, **either one** will work.

However, you will find that a particular analysis is **easier** with one model or the other; a result that is dependent **completely** on the type of amplifier being analyzed.

For time being, use the **Hybrid-II model**; later on, we will discuss the types of amplifiers where the **T-model** is simplest to use.