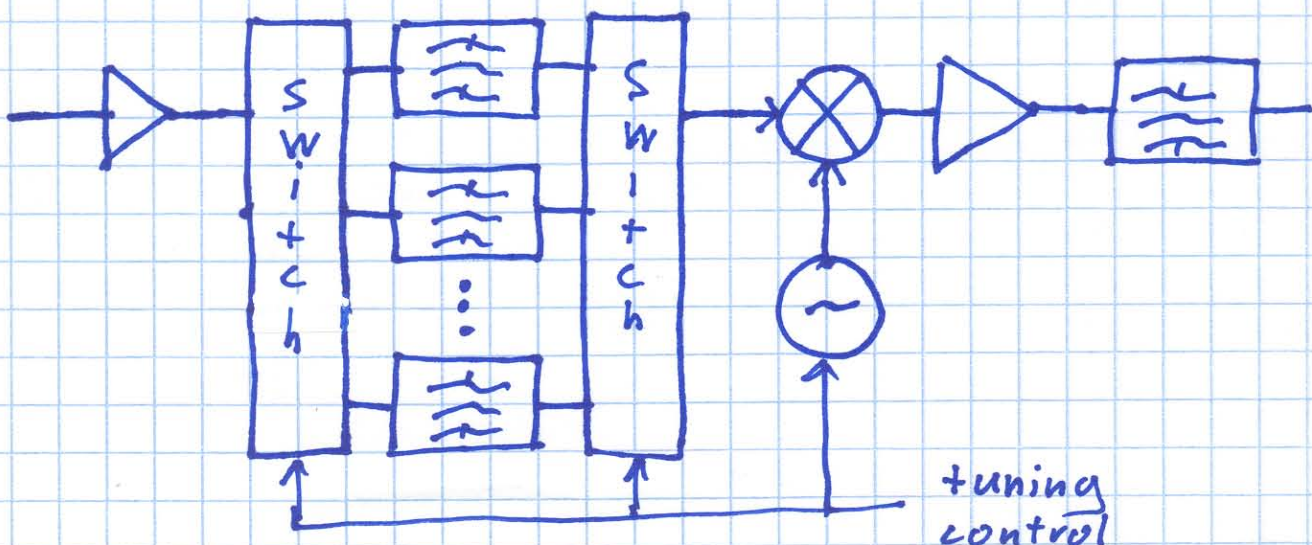


Advanced Rx Designs

To achieve exceptional image/3rd-order product rejection, Rx designers can employ these advanced receiver architectures:

Selectable Preselection

Instead of using a single preselector filter, we can use a bank of selectable preselector filters:



In other words, we use multiple preselector filters to span the Rx bandwidth.

For example, say the Rx bandwidth is 8-12 GHz. Instead of one filter with a 3dB bandwidth of 8 to 12 GHz, we might use 4 filters, with bands:


	bandwidth
filter #1	8-9 GHz
filter #2	9-10 GHz
filter #3	10-11 GHz
filter #4	11-12 GHz

Thus, if we tune the receiver (i.e., the local oscillator) to an RF frequency of 10.3 GHz, we would set the switches so that filter 3 is selected.

This design is particularly effective when the receiver has a wide bandwidth.

Dual Conversion Receivers

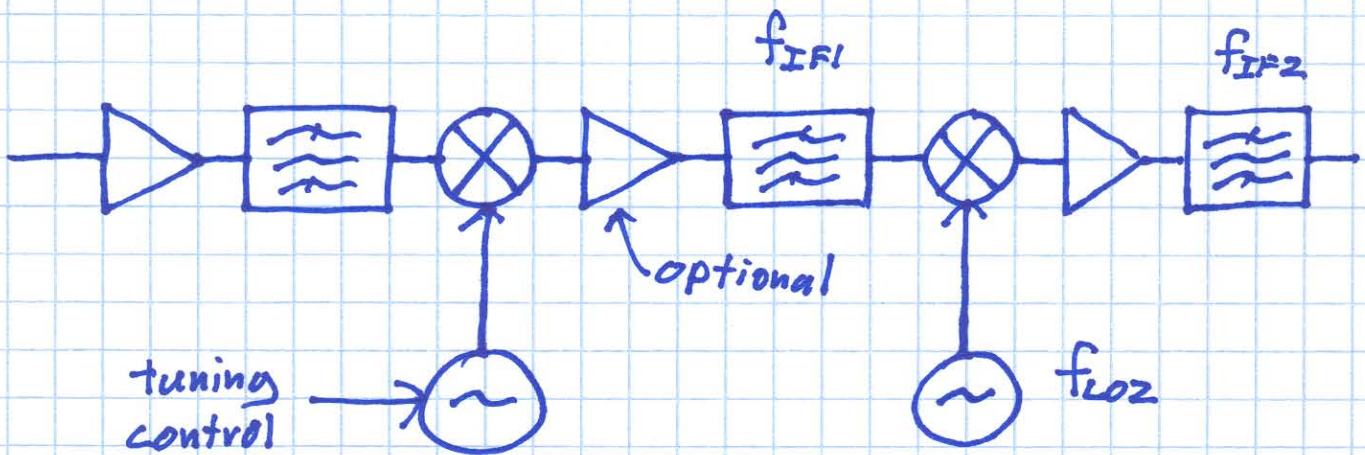Another advanced design is the dual-conversion receiver. With this concept, we employ 2 Intermediate Frequencies!



The idea behind this receiver is that the image/3rd-order rejection generally improves as we increase the IF frequency. It will really get good if we make the IF frequency much

higher than the RF frequencies!
For example, we might use an
IF of 8 GHz for a Rx with RF
bandwidth of 1-2 GHz!

Note that the LO bandwidth for
this design would be either:

6-7 GHz or 9-10 GHz

where for the first case we use
the product $f_{IF} = f_{RF} + f_{LO}$, and for
the second case we use $f_{IF} = f_{LO} - f_{RF}$.

Q: O.K., I see why using an
extremely high IF could
provide excellent image rejection.


But, wouldn't amplifiers/attenuators
at 8 GHz (say) and a demodulator
at 8 GHz be very expensive and/or
perform poorly???

A^o True! This is why we employ
a second IF!

We down convert our signal at
the first IF to a "normal" IF
frequency (e.g. 100 MHz).

Note the local oscillator for this
second mixer is at a fixed frequency:

$$f_{LO2} = |f_{IF1} - f_{IF2}|$$

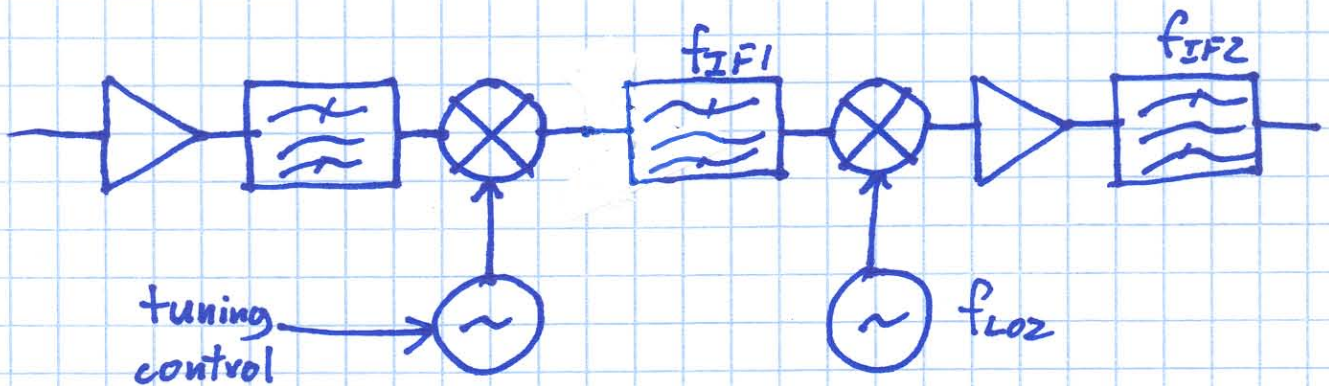

Thus, with this design, we get the
rejection associated with a high frequency
IF, while retaining the cost/performance
of the AGC and demodulator associated
with a low IF.