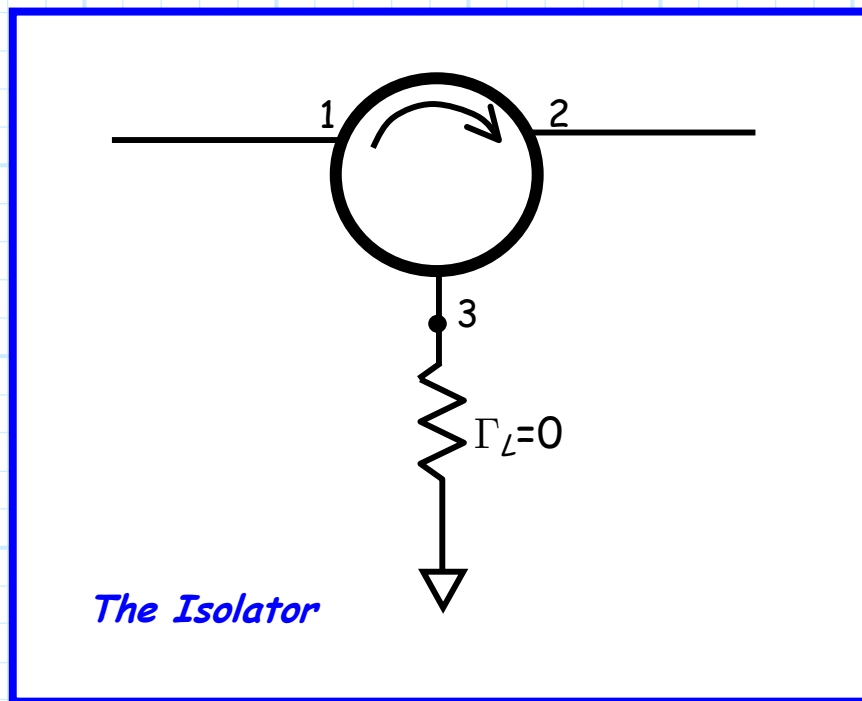


# Isolators

An **isolator** is simply a **circulator**, with port 3 terminated in a **matched load**!




The matched load at port 3 insures that  $P_3^+ = 0$  **always**. As a result we know that  $P_1^- = P_3^+ = 0$  **--always!**

An ideal isolator is thus a **two-port** device with an **odd** looking scattering matrix:

$$\bar{\mathbf{S}} = \begin{bmatrix} 0 & 0 \\ 1 & 0 \end{bmatrix}$$


Therefore,  $P_2^- = P_1^+$ , but  $P_1^- = 0$  regardless of  $P_2^+$  --an ideal isolator is matched, but is also non-reciprocal and **lossy**!

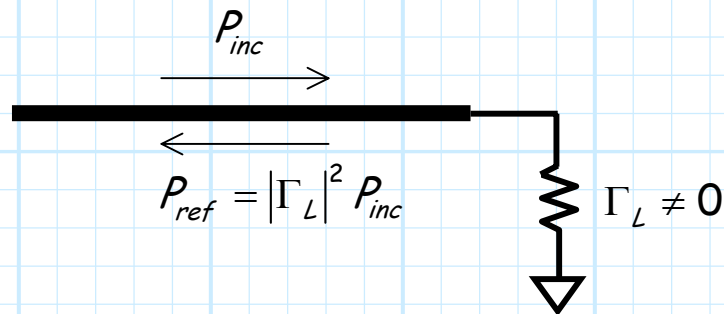An isolator is useful for **isolating** a load from a source. For example, consider an **unmatched** load at the end of a transmission line:



**Plenty** of power is reflected back toward the source!

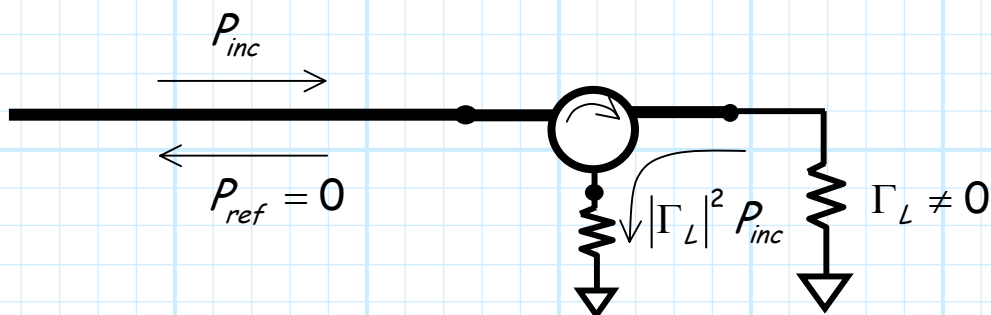Now, let's **insert** an isolator between the source and load:



There is **no power** reflected back to the source! Instead, power reflected by the load is **absorbed** by the isolator.

To the source, the circuit appears **matched**—but it's **not**!

If the isolator was truly a matching network, then the **absence** of reflected power would indicate that **all** the incident power was absorbed by the **load**. Instead, there is no reflected power because this power is instead absorbed by the **isolator**—the isolator is **lossy**!