

The Lossless Transmission Line

Say a transmission line is **lossless** (i.e., $R=G=0$); the transmission line equations are then **significantly** simplified!

Characteristic Impedance

$$\begin{aligned}Z_0 &= \sqrt{\frac{R + j\omega L}{G + j\omega C}} \\ &= \sqrt{\frac{j\omega L}{j\omega C}} \\ &= \sqrt{\frac{L}{C}}\end{aligned}$$

Note the characteristic impedance of a **lossless** transmission line is purely **real** (i.e., $\text{Im}\{Z_0\} = 0$)!

Propagation Constant

$$\begin{aligned}\gamma &= \sqrt{(R + j\omega L)(G + j\omega C)} \\ &= \sqrt{(j\omega L)(j\omega C)} \\ &= \sqrt{-\omega^2 LC} \\ &= j\omega\sqrt{LC}\end{aligned}$$

The wave propagation constant is purely **imaginary**!

In other words, for a **lossless** transmission line:

$$\alpha = 0 \quad \text{and} \quad \beta = \omega\sqrt{LC}$$

Voltage and Current

The **complex functions** describing the magnitude and phase of the voltage/current at every location z along a transmission line are for a **lossless** line are:

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{+j\beta z}$$

Line Impedance

The **complex function** describing the impedance at every point along a **lossless** transmission line is:

$$Z(z) = \frac{V(z)}{I(z)} = Z_0 \frac{V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}}{V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z}}$$

Reflection Coefficient

The **complex function** describing the reflection at every point along a **lossless** transmission line is:


$$\Gamma(z) = \frac{V_0^- e^{+j\beta z}}{V_0^+ e^{-j\beta z}} = \frac{V_0^-}{V_0^+} e^{+j2\beta z}$$

Wavelength and Phase Velocity

We can now **explicitly** write the wavelength and propagation velocity of the two transmission line waves in terms of transmission line parameters L and C :

$$\lambda = \frac{2\pi}{\beta} = \frac{1}{f\sqrt{LC}}$$
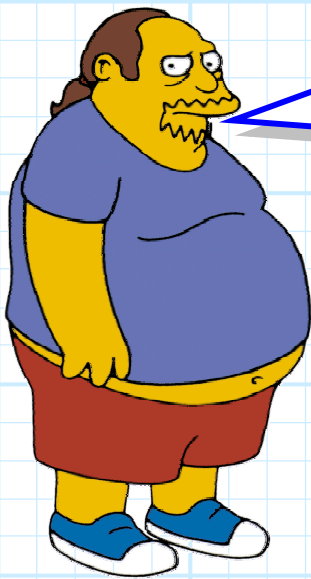
$$v_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$



Q: *Oh please, continue wasting my valuable time. We both know that a **perfectly lossless transmission line** is a physical **impossibility**.*

A: True! However, a **low-loss** line is possible—in fact, it is **typical**! If $R \ll \omega L$ and $G \ll \omega C$, we find that the lossless transmission line equations are excellent **approximations**!

Unless otherwise indicated, we will use the lossless equations to **approximate** the behavior of a **low-loss** transmission line.

The lone **exception** is when determining the attenuation of a long transmission line. For that case we will use the approximation:

$$\alpha \approx \frac{1}{2} \left(\frac{R}{Z_0} + GZ_0 \right)$$

where $Z_0 = \sqrt{L/C}$.

A summary of lossless transmission line equations

$$Z_0 = \sqrt{\frac{L}{C}} \quad \gamma = j\omega\sqrt{LC}$$

$$V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z} \quad I(z) = \frac{V_0^+}{Z_0} e^{-j\beta z} - \frac{V_0^-}{Z_0} e^{+j\beta z}$$

$$Z(z) = Z_0 \frac{V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}}{V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z}}$$

$$V^+(z) = V_0^+ e^{-j\beta z} \quad V^-(z) = V_0^- e^{+j\beta z}$$

$$\Gamma(z) = \frac{V_0^-}{V_0^+} e^{+j2\beta z}$$

$$\beta = \omega\sqrt{LC} \quad \lambda = \frac{1}{f\sqrt{LC}} \quad v_p = \frac{1}{\sqrt{LC}}$$