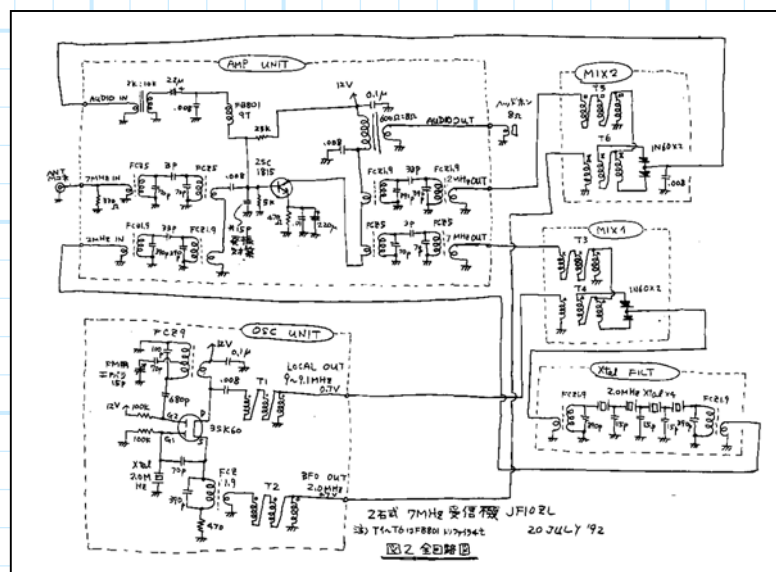


The Radio Receiver

There are 8 basic components in a radio receiver:

- 1) Antenna
- 2) Low-noise Amplifier (LNA)
- 3) Preselection Filter
- 4) Local Oscillator/Mixer
- 5) Intermediate Frequency (IF) Amplifier
- 6) IF Filter
- 7) Detector/Demodulator
- 8) The recovered signal $\hat{a}(t)$




← A receiver design schematic I found on the web.

Note the amplifier (amp), oscillator (osc), mixer (mix), and filter (filt) sections.

Let's examine each component:

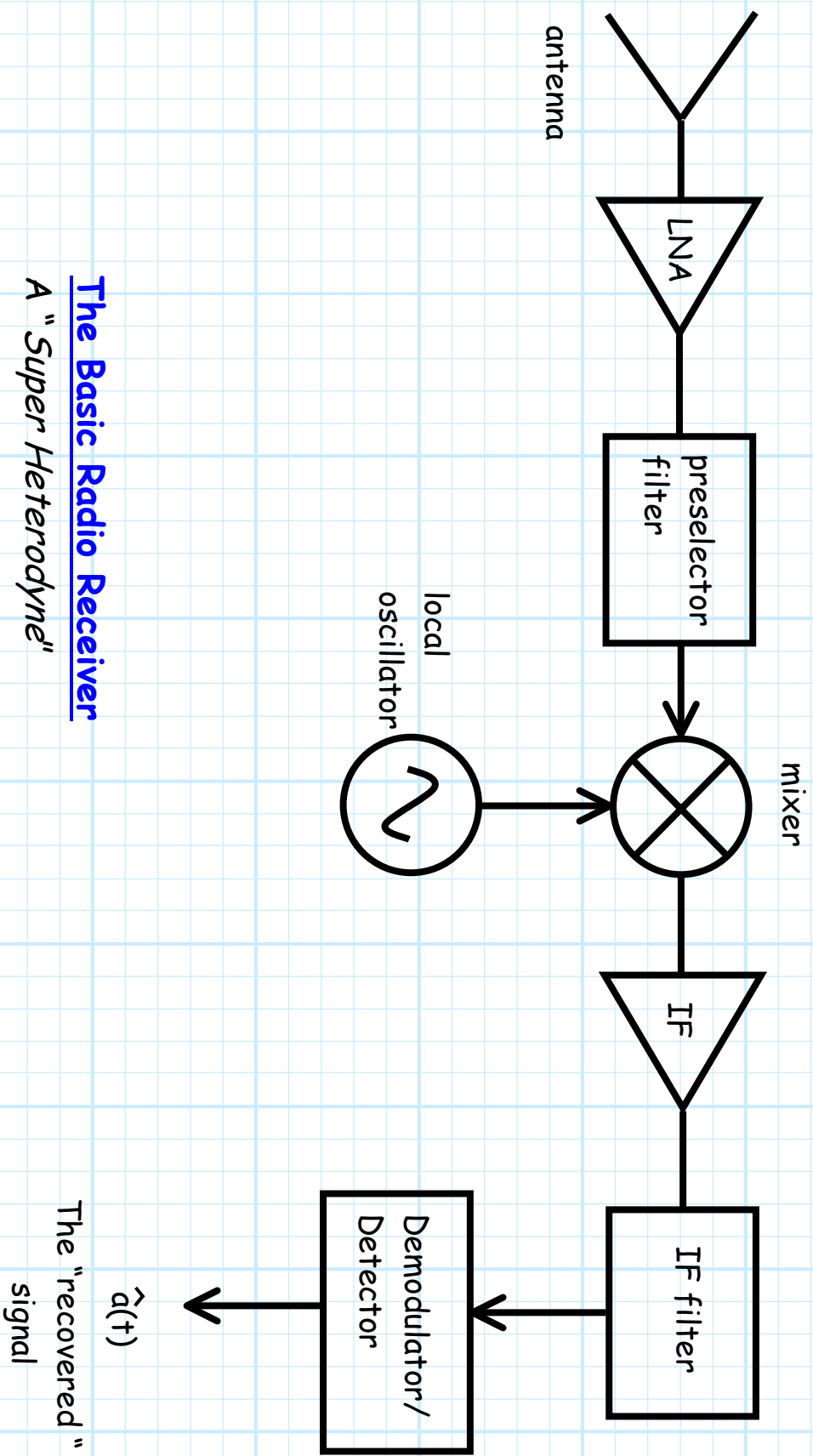- 1) **Antenna** - **Couples** the incoming e.m. propagating wave into the receiver.
- 2) **Low-Noise Amplifier** - **Boosts** the power of the initial signal above the receiver noise.
- 3) **Preselector Filter** - Allows **only** the frequency band of interest to pass into the receiver (e.g., for FM radio 88-108 MHz).
- 4) **Local Oscillator/Mixer** - **Translates** the signal from its propagation frequency to a lower, fixed intermediate frequency (IF).
- 5) **IF Amplifier** - A high-gain amplifier that greatly **increases** signal power (i.e., to a detectable level).
- 6) **IF Filter** - Allows **only** the signal of interest to pass. Bandwidth is typically that of the desired signal. (e.g., 200 kHz for FM radio, 20 kHz for AM radio).
- 7) **Detector/Demodulator** - **Extracts** the signal information (or, at least tries to !) from the IF signal.
- 8) **The Recovered Signal** $\hat{a}(t)$ - The receiver's "**guess**" at what the original signal was. Ideally, $\hat{a}(t) = a(t)$, but channel propagation "uncertainties" and noise make **perfect** reproduction impossible !



The Basic Radio Receiver
A "Super Heterodyne"