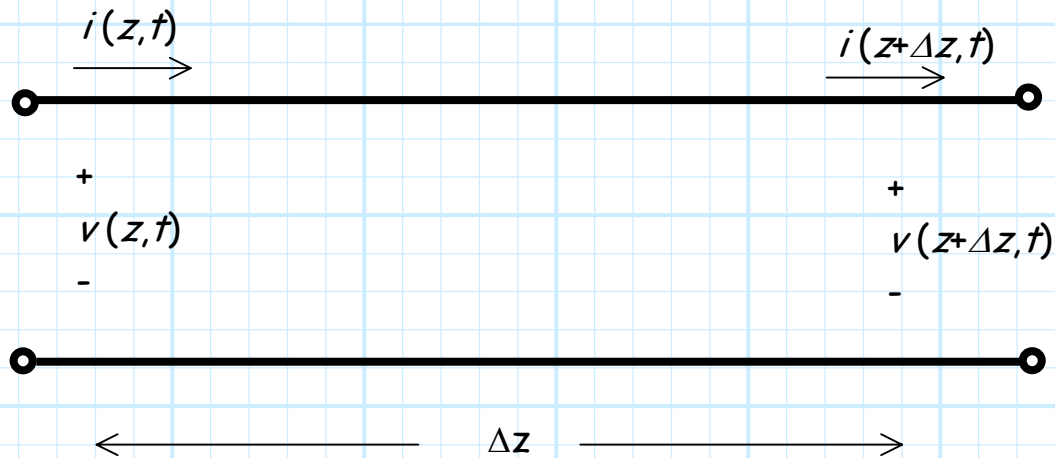


# The Telegrapher Equations

Consider a section of "wire":




**Q:** Huh ?! Current  $i$  and voltage  $v$  are a function of position  $z$  ??  
Shouldn't  $i(z, t) = i(z + \Delta z, t)$  and  $v(z, t) = v(z + \Delta z, t)$  ?

**A:** NO ! Because a wire is never a **perfect** conductor.

A "wire" will have:

- 1) Inductance
- 2) Resistance
- 3) Capacitance
- 4) Conductance

i.e.,

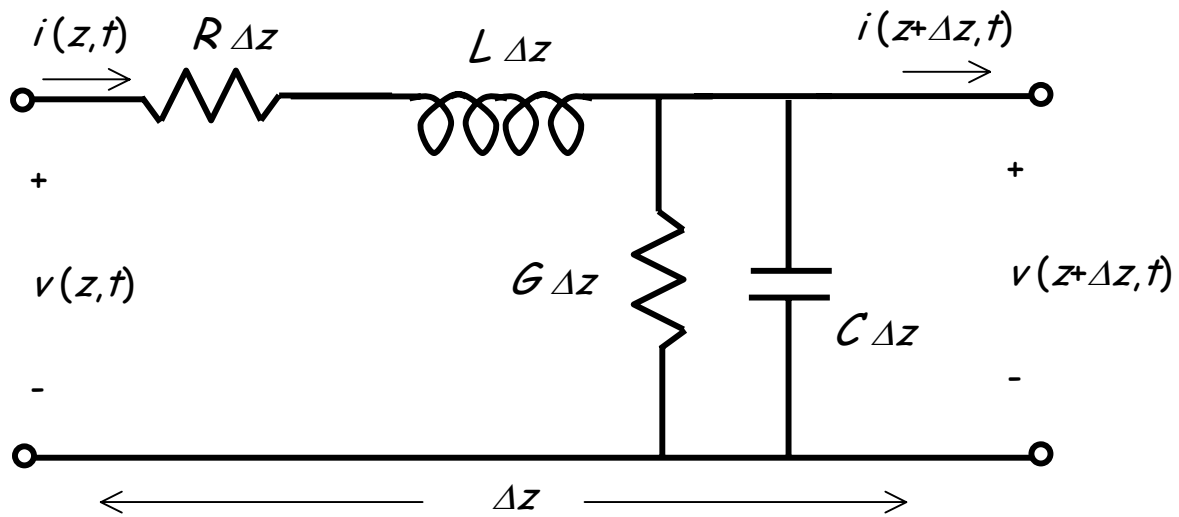

Where:

$R$  = resistance/unit length

$L$  = inductance/unit length

$C$  = capacitance/unit length

$G$  = conductance/unit length

$\therefore$  resistance of wire length  $\Delta z$  is  $R\Delta z$ .

Using KVL, we find:

$$v(z+\Delta z,t) - v(z,t) = -R\Delta z i(z,t) - L\Delta z \frac{\partial i(z,t)}{\partial t}$$

and from KCL:

$$i(z+\Delta z,t) - i(z,t) = -G\Delta z v(z,t) - C\Delta z \frac{\partial v(z,t)}{\partial t}$$

Dividing the first equation by  $\Delta z$ , and then taking the limit as  $\Delta z \rightarrow 0$ :

$$\lim_{\Delta z \rightarrow 0} \frac{v(z + \Delta z, t) - v(z, t)}{\Delta z} = -R i(z, t) - L \frac{\partial i(z, t)}{\partial t}$$

which, by definition of the derivative, becomes:

$$\frac{\partial v(z, t)}{\partial z} = -R i(z, t) - L \frac{\partial i(z, t)}{\partial t}$$

Similarly, the KCL equation becomes:

$$\frac{\partial i(z, t)}{\partial z} = -G v(z, t) - C \frac{\partial v(z, t)}{\partial t}$$

If  $v(z, t)$  and  $i(z, t)$  have the form:

$$v(z, t) = \text{Re}\{V(z)e^{j\omega t}\} \quad \text{and} \quad i(z, t) = \text{Re}\{I(z)e^{j\omega t}\}$$

then these equations become:

$$\frac{\partial V(z)}{\partial z} = -(R + j\omega L)I(z)$$

$$\frac{\partial I(z)}{\partial z} = -(G + j\omega C)V(z)$$

These equations are known as the **telegrapher's equations** !

- \* The functions  $I(z)$  and  $V(z)$  are **complex**, where the **magnitude** and **phase** of the complex functions describe the **magnitude** and **phase** of the sinusoidal time function  $e^{j\omega t}$ .
- \* Thus,  $I(z)$  and  $V(z)$  describe the current and voltage along the transmission line, as a function as position  $z$ .
- \* **Remember**, not just **any** function  $I(z)$  and  $V(z)$  can exist on a transmission line, but rather **only** those functions that satisfy the **telegraphers equations**.

Our task, therefore, is to **solve** the telegrapher equations and find **all** solutions  $I(z)$  and  $V(z)$ !

