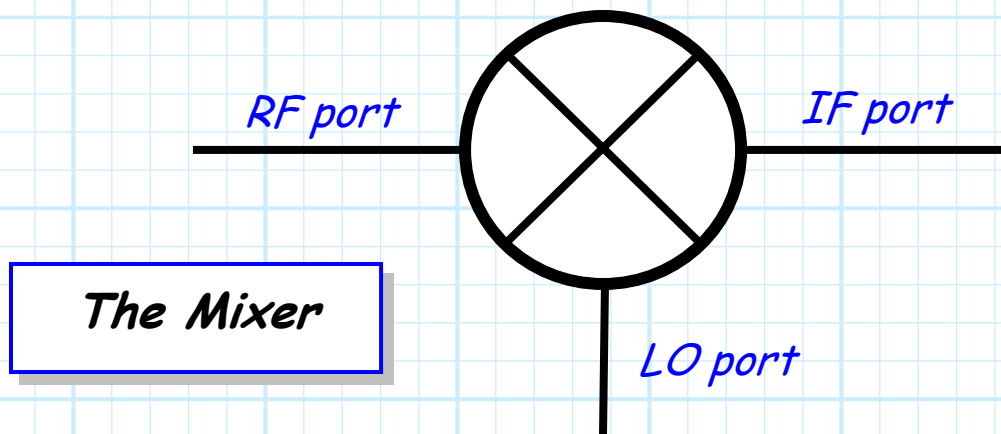


# Mixers

A **mixer** is a three-port, **non-linear** microwave device.



The three ports of a mixer are **distinct** and unique, and are typically referred to as:

- 1) The **RF** (Radio Frequency) port
- 2) The **IF** (Intermediate Frequency) port
- 3) The **LO** (Local Oscillator) port

**Q:** So just what does a mixer **do**??

**A:** A clue is in its symbol:  $\otimes$

→ A mixer is a **multiplier** ( $\times$ ) !!

Say there is a signal  $v_{RF}(t)$  at the RF mixer port, and a signal  $v_{LO}(t)$  at the LO mixer port. An **ideal** mixer would then produce at the IF port, a signal  $v_{IF}(t)$ , where:

$$v_{RF}(t)v_{LO}(t) = v_{IF}(t) \quad (\text{an ideal mixer})$$

To see why this might be **useful**, consider a case where:

$$v_{RF}(t) = \cos \omega_{RF} t$$

$$v_{LO}(t) = \cos \omega_{LO} t$$

Multiplying these signals, we get:


$$\begin{aligned} v_{IF}(t) &= v_{RF}(t)v_{LO}(t) \\ &= \cos(\omega_{RF}t)\cos(\omega_{LO}t) \\ &= \frac{1}{2}\cos(\omega_{RF} - \omega_{LO})t + \frac{1}{2}\cos(\omega_{RF} + \omega_{LO})t \end{aligned}$$

At the IF port we have created **two** signals with **new** frequencies!

One new signal has a frequency that is the **difference** of the LO and RF signal frequencies:

$$\frac{1}{2}\cos(\omega_{RF} - \omega_{LO})t$$

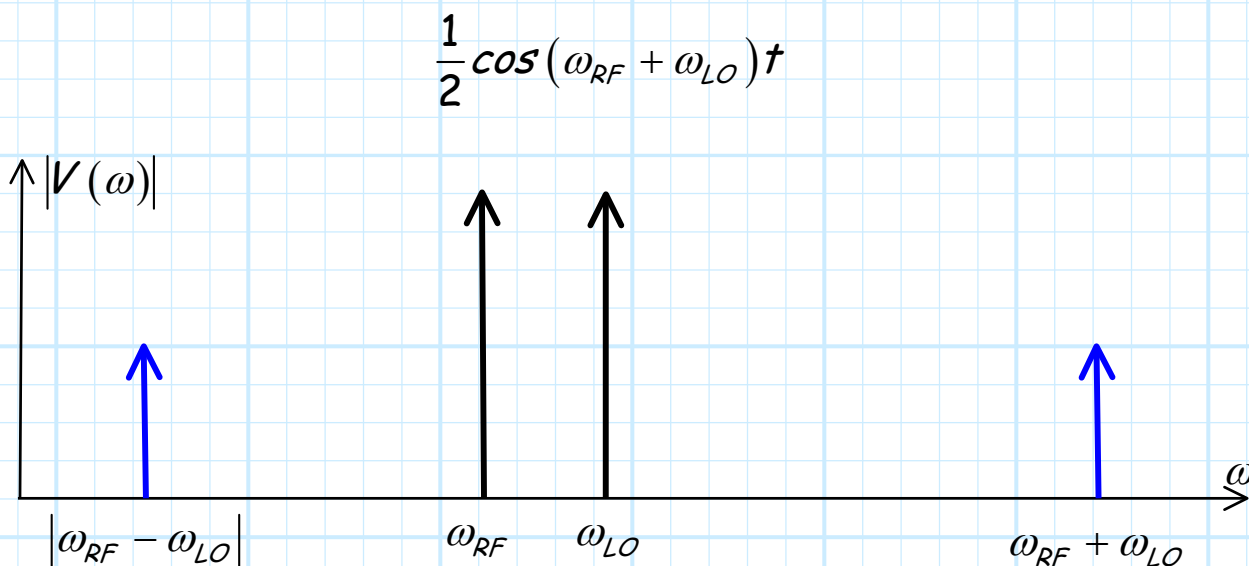While the other new signal has a frequency that is the **sum** of the LO and RF signal frequencies:



But alas, mixers are **not ideal!**

A more **accurate** model of the (non-ideal) relationship between  $v_{RF}(t)$ ,  $v_{LO}(t)$ , and  $v_{IF}(t)$  is:

$$\begin{aligned}
 v_{IF}(t) = & a_1 v_{RF}(t) + a_2 v_{LO}(t) \\
 & + a_3 v_{RF}^2(t) + a_4 v_{RF}(t)v_{LO}(t) + a_5 v_{LO}^2(t) \\
 & + a_6 v_{RF}^3(t) + a_7 v_{RF}^2(t)v_{LO}(t) \\
 & + a_8 v_{RF}(t)v_{LO}^2(t) + a_9 v_{LO}^3(t) \\
 & + \dots
 \end{aligned}$$

where the values  $a_n$  are real-valued **constants**.

Just as with an amplifier, a mixer will produce **1<sup>st</sup>-order**, **2<sup>nd</sup>-order**, **3<sup>rd</sup>-order**, and even **higher order** terms!

As a result, there will be **many** signals created at the IF port. If we did **all** the trigonometry, we would find that the signal **frequencies** created from these terms (in relation to  $\omega_{RF}$  and  $\omega_{LO}$ ) are:

**1<sup>st</sup> order:**  $\omega_{RF}, \omega_{LO}$

**2<sup>nd</sup> order:**  $|\omega_{RF} - \omega_{LO}|, 2\omega_{RF}, 2\omega_{LO}, \omega_{RF} + \omega_{LO}$

**3<sup>rd</sup> order:**  $|2\omega_{RF} - \omega_{LO}|, |2\omega_{LO} - \omega_{RF}|, 3\omega_{RF},$   
 $3\omega_{LO}, 2\omega_{RF} + \omega_{LO}, \omega_{RF} + 2\omega_{LO}$

**examples of higher orders:**  $|4\omega_{RF} - 2\omega_{LO}|, 5\omega_{RF},$   
 $7\omega_{LO}, 827\omega_{RF} + 134\omega_{LO}$

Note that the **ideal** mixer (multiplier) occurs when all constants  $a_n$  are zero, **except** for the constant  $a_4$ . The result in this case being:

$$v_{IF}(t) = a_4 v_{RF}(t) v_{LO}(t) \quad (\text{ideal mixer response})$$

and thus the **only** signals created are the **2<sup>nd</sup> order** terms  $|\omega_{RF} - \omega_{LO}|$  and  $\omega_{RF} + \omega_{LO}$ .

Of course for a "real" mixer, all the constants  $a_n$  are **non-zero**, although for good mixers all but  $a_4$  are relatively **small**.

Thus, for good mixers, most of the signals created at the IF output will be of relatively **low** power, with **exception** of the signal at frequencies  $|\omega_{RF} - \omega_{LO}|$  and  $\omega_{RF} + \omega_{LO}$ .

All **other** signals (meaning other than  $|\omega_{RF} - \omega_{LO}|$  and  $\omega_{RF} + \omega_{LO}$ ) at the IF are known as **spurious** signals—or in the vernacular of radio engineers, "**spurs**".


**Q:** *How are mixers constructed?*

**A:** Multiplication is a decidedly **non-linear** operation. As such, it requires **non-linear devices** to implement.

Typically, these non-linear devices are **diodes**, but sometimes transistors are used.

For example, as those of you who aced EECS 312 know, the **junction diode** equation is:
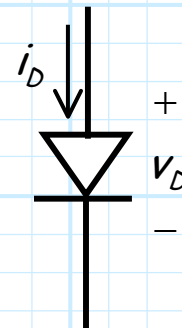
$$i_D = I_s \left( e^{v_D/nV_T} - 1 \right)$$



This **non-linear** function can be expanded using a **Taylor series** as:

$$i_D = I_s \left( e^{v_D/nV_T} - 1 \right) = b_1 v_D + b_2 v_D^2 + b_3 v_D^3 + \dots$$

And if, for example:

$$v_D(t) = v_{RF}(t) + v_{LO}(t)$$

we find that the diode will create **high-order** terms, including  $v_{RF}(t)v_{LO}(t)$ :

$$b_2(v_{RF}(t) + v_{LO}(t))^2 = b_2(v_{RF}^2(t) + 2v_{RF}(t)v_{LO}(t) + v_{LO}^2(t))$$

Basically, generating high-order terms with **any** non-linear device is **not** at all difficult (just try and **keep** it from happening!). The trick is to generate **only** the 2<sup>nd</sup> order term  $v_{RF}(t)v_{LO}(t)$ , while somehow **suppressing** the rest.

Thus, mixer design is as much **art** as it is science! Popular designs include the **balanced mixer** (with 2 junction diodes), and the **double balanced mixer** (with 4 junction diodes).

