

Special Problem 2.C-1

A diode mixer has an LO signal at $f_{LO} = 120$ MHz, and an RF signal at $f_{RF} = 100$ MHz.

Find **all** first, second, and third order output frequencies.