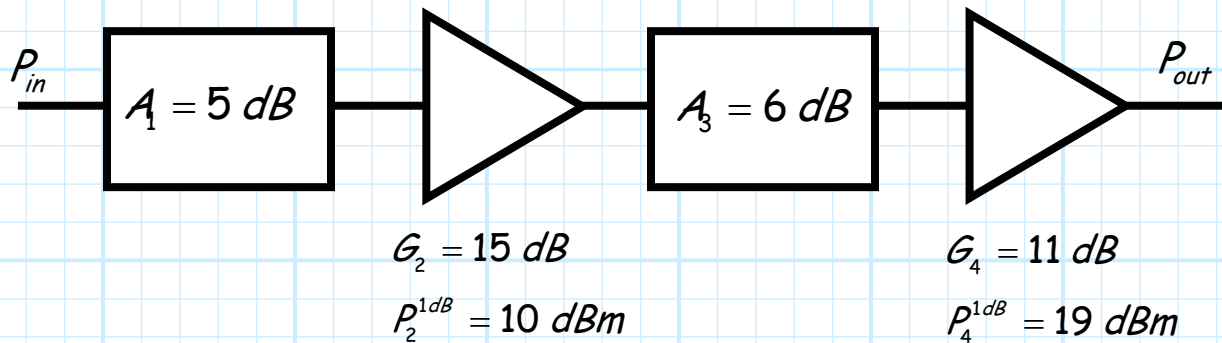


Special Problem 4.D-6

The following microwave network consists of **two amplifiers** and **two attenuators**.



Determine (approximately) the value of **output power** P_{out} when input power P_{in} becomes sufficiently large to cause the network to **saturate**.