

**Special Problem II.A-13**

The voltage along a transmission line connected to **port 1** of a **passive** microwave device is:

$$V(z) = 0.8 e^{-j\beta z} + 0.2 e^{j\beta z}$$

Assuming all other ports of the device are **terminated** in matched loads, **determine  $S_{11}$**  for this device.