

Special Problem - II.A-29

Using **ideal** microwave switches and fixed attenuators, design a **digital attenuator** where we can select any attenuation from 0 dB to 22.5 dB in 1.5 dB steps (i.e., 0 dB, 1.5 dB, 3.0 dB, 4.5 dB,)