

### Special Problem II.A-5

A diode mixer has an LO signal at  $f_{LO} = 120$  MHz, and an RF signal at  $f_{RF} = 100$  MHz.

Find **all** first, second, and third order output frequencies.